

***Analysis and Design of Analog Integrated Circuits***  
***Lecture 10***



***Frequency Response of Amplifiers***

**Michael H. Perrott**  
**February 29, 2012**



**Copyright © 2012 by Michael H. Perrott**  
**All rights reserved.**

# Open Loop Versus Closed Loop Amplifier Topologies

Open Loop

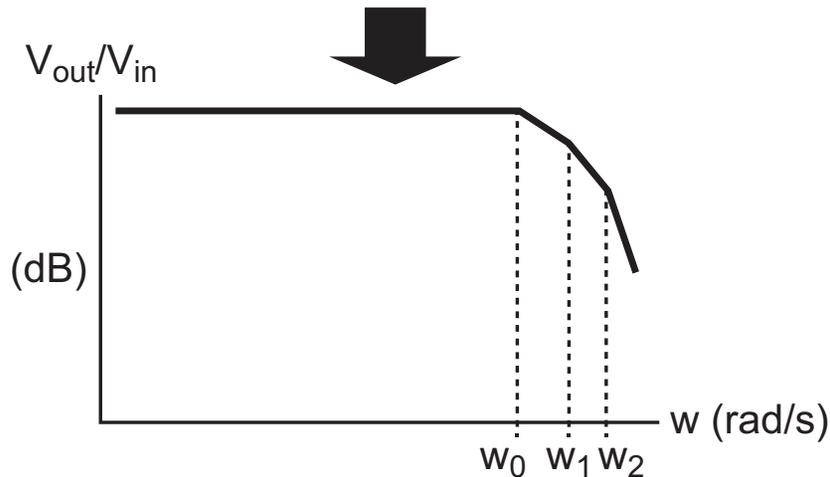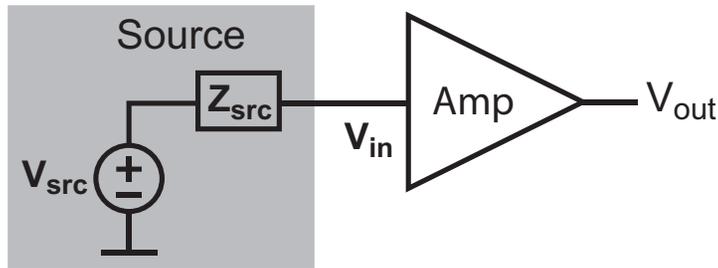


Closed Loop

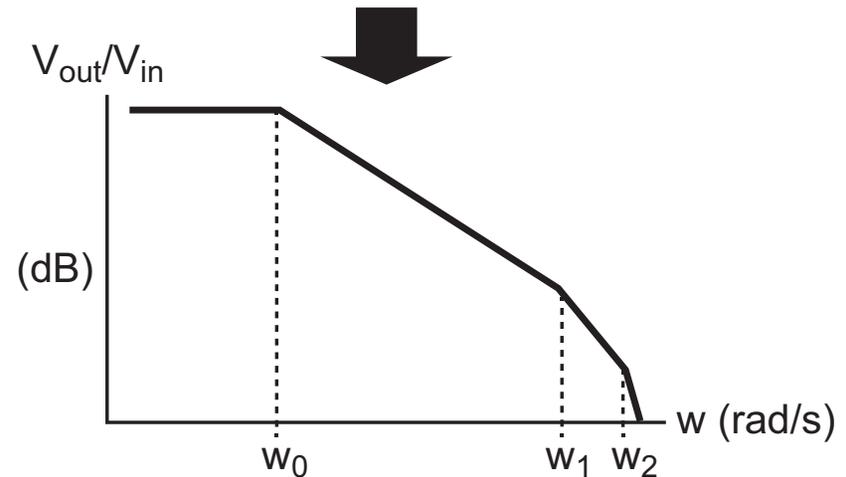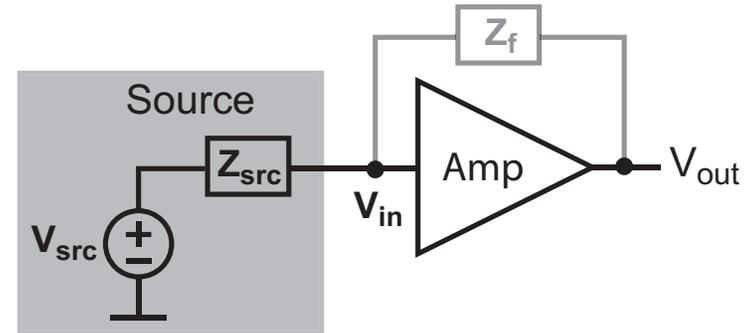

- **Open loop – want all bandwidth limiting poles to be as high in frequency as possible**
- **Closed loop – want one pole to be dominant and all other parasitic poles to be as high in frequency as possible**

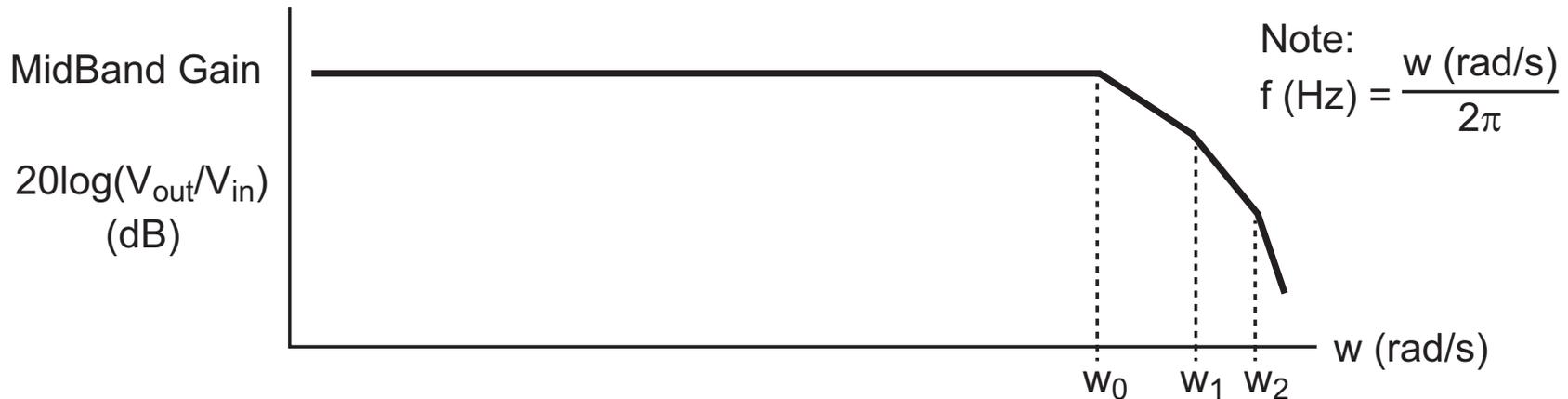
# OCT Method of Estimating Amplifier Bandwidth



- OCT method calculates  $\sum_{i=0}^{n-1} \tau_i$  by the following steps:
  - Compute the effective resistance  $R_{thj}$  seen by each capacitor,  $C_j$ , with other caps as open circuits
    - AC coupling caps are not included – considered as shorts
  - Form the “open circuit” time constant  $T_j = R_{thj}C_j$  for each capacitor  $C_j$
  - Sum all of the “open circuit” time constants

$$\Rightarrow BW \approx \frac{1}{\sum_{j=1}^m R_{thj}C_j} \text{ rad/s}$$
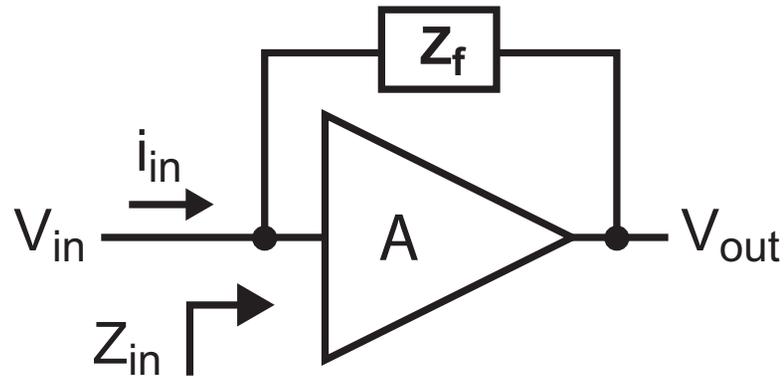
## Another Useful Analysis Tool: Miller Effect



- Derive input impedance (assume gain of amplifier =  $A$ ):


$$Z_{in} = \frac{V_{in}}{i_{in}} = \frac{V_{in}}{(V_{in} - V_{out})/Z_f} = \frac{V_{in}Z_f}{V_{in} - AV_{in}} = \frac{Z_f}{1 - A}$$

- Consider the case where  $Z_f$  is a capacitor

$$Z_f = \frac{1}{sC} \Rightarrow Z_{in} = \frac{1}{s(1 - A)C}$$

- For negative  $A$ , input impedance sees increased cap value
- For  $A = 1$ , input impedance sees no influence from cap
- For  $A > 1$ , input impedance sees negative capacitance!
  - Can be used to create active inductor for a specific frequency

# Key Capacitances for CMOS Devices

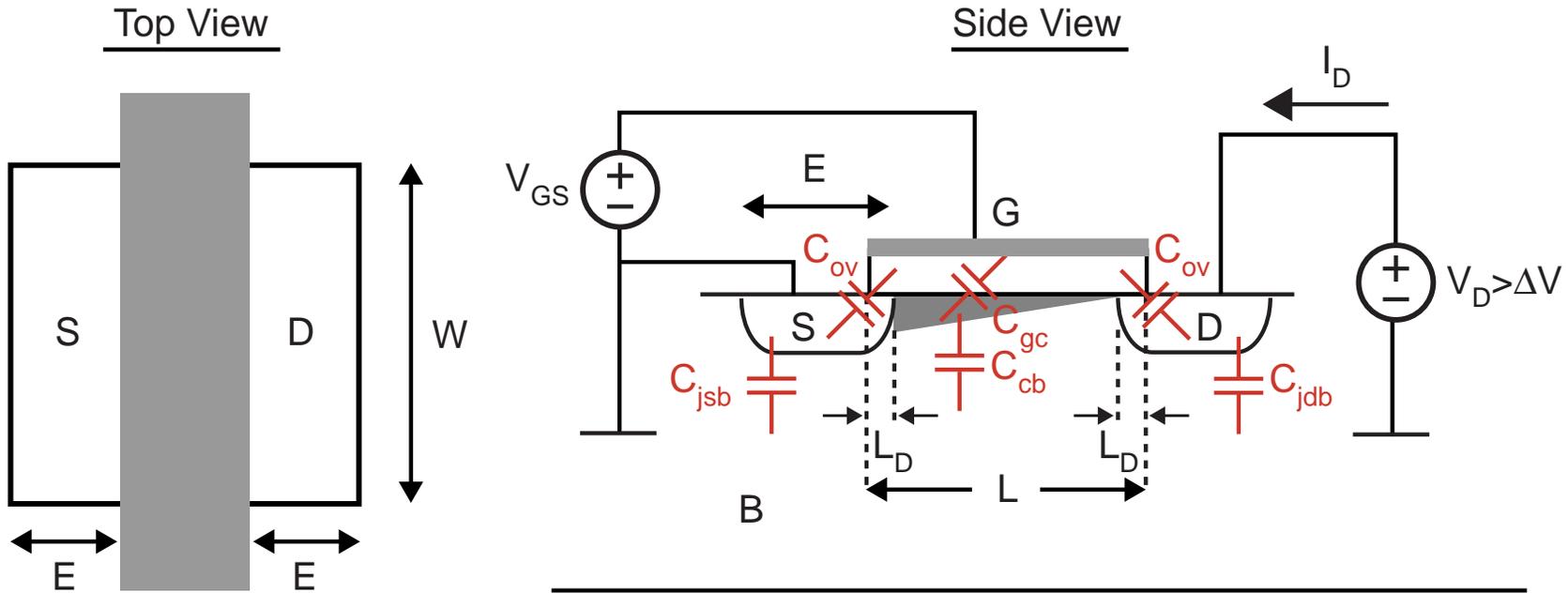

junction bottom wall cap (per area)

junction sidewall cap (per length)

source to bulk cap:  $C_{\text{j\text{sb}}} = \frac{C_{\text{j}}(0)}{\sqrt{1 + V_{\text{SB}}/|\Phi_{\text{B}}|}} WE + \frac{C_{\text{j\text{sw}}}(0)}{\sqrt{1 + V_{\text{SB}}/|\Phi_{\text{B}}|}} (W + 2E)$


drain to bulk cap:  $C_{\text{j\text{sd}}} = \frac{C_{\text{j}}(0)}{\sqrt{1 + V_{\text{DB}}/|\Phi_{\text{B}}|}} WE + \frac{C_{\text{j\text{sw}}}(0)}{\sqrt{1 + V_{\text{DB}}/|\Phi_{\text{B}}|}} (W + 2E)$

(make  $2W$  for "4 sided" perimeter in some cases)

overlap cap:  $C_{\text{ov}} = WL_D C_{\text{ox}} + WC_{\text{fringe}}$       gate to channel cap:  $C_{\text{gc}} = \frac{2}{3} C_{\text{ox}} W(L - 2L_D)$

channel to bulk cap:  $C_{\text{cb}}$  - ignore in this class
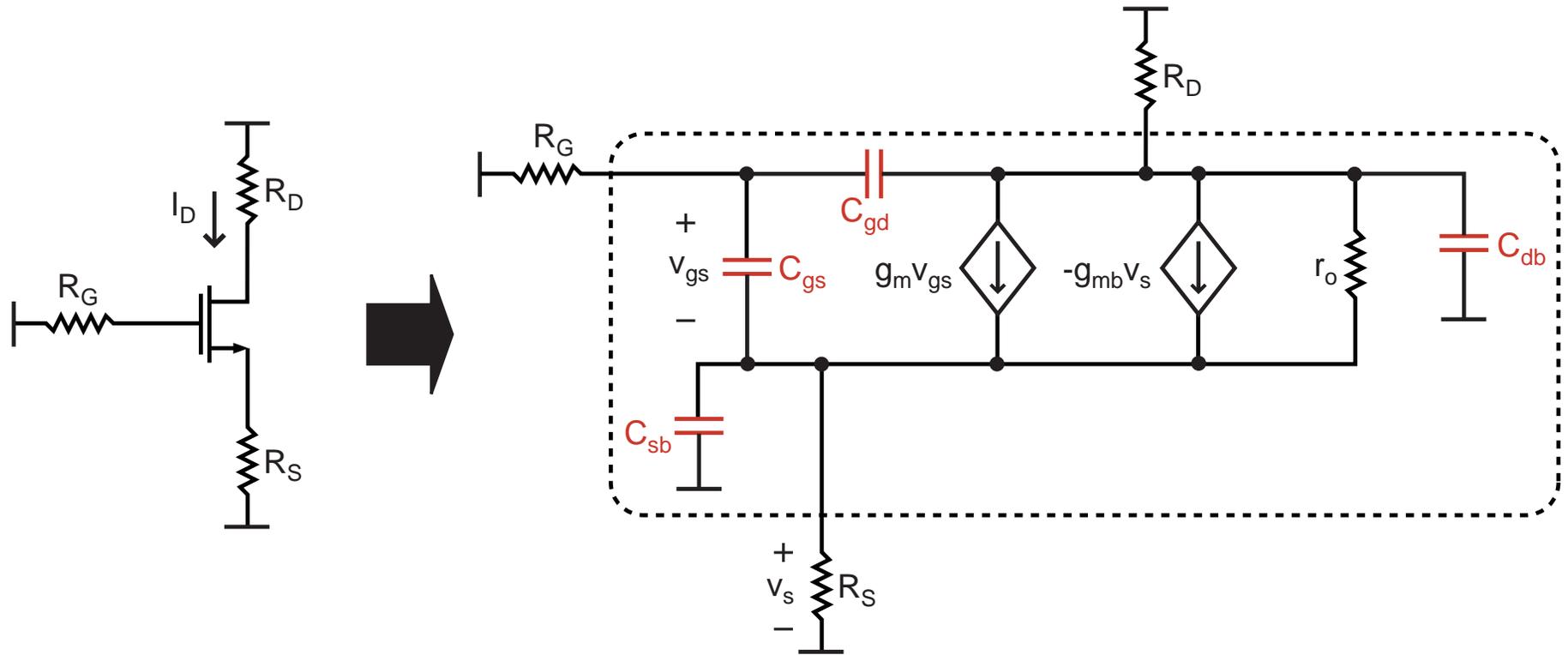
# CMOS Hybrid- $\pi$ Model with Caps (Device in Saturation)




$$C_{gs} = C_{gc} + C_{ov} = \frac{2}{3} C_{ox} W(L-2L_D) + C_{ov}$$

$$C_{gd} = C_{ov}$$

$$C_{sb} = C_{jsb} \quad (\text{area + perimeter junction capacitance})$$

$$C_{db} = C_{jdb} \quad (\text{area + perimeter junction capacitance})$$

# OCT Thevenin Resistance Calculations

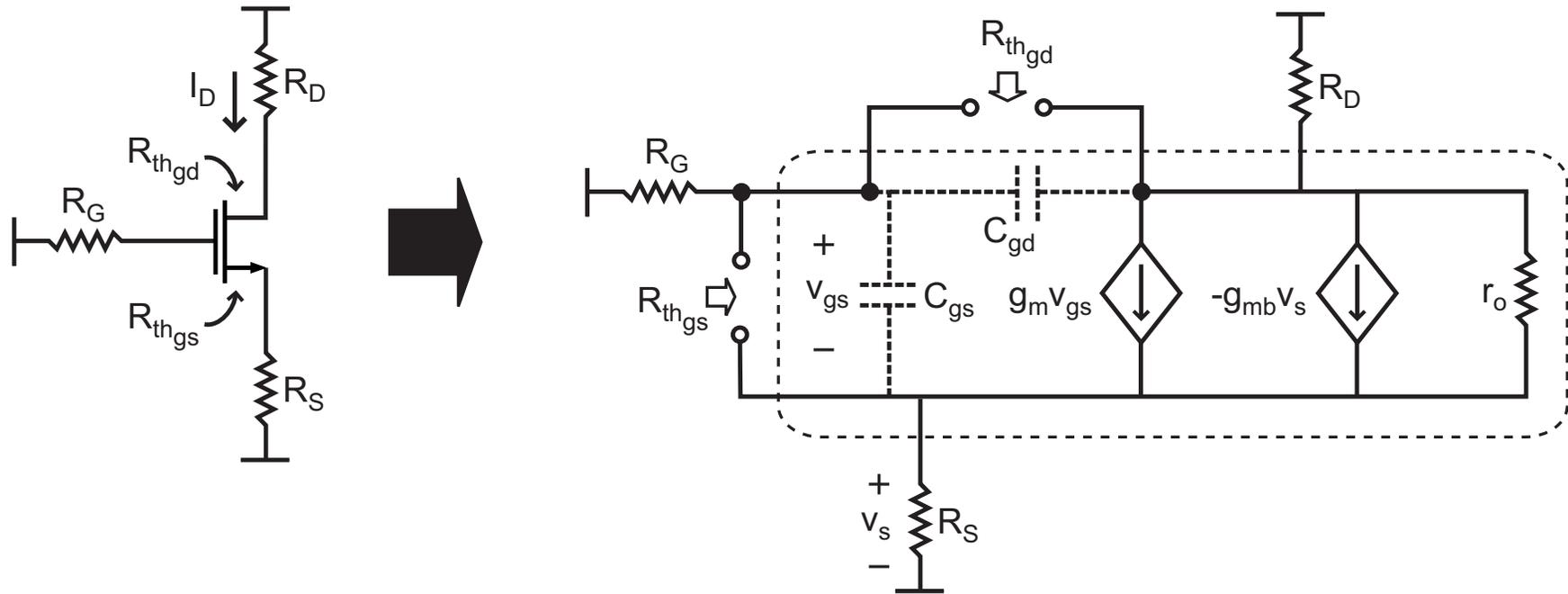

- $C_{gs}$ : Thevenin resistance between gate and source


$$R_{th_{gs}} = \frac{R_S(1 + R_D/r_o) + R_G(1 + (g_{mb} + 1/r_o)R_S + R_D/r_o)}{1 + (g_m + g_{mb})R_S + (R_S + R_D)/r_o}$$

- $C_{gd}$ : Thevenin resistance between gate and drain

$$R_{th_{gd}} = (R_D + R_G)(1 - r_{ods}/r_o) + r_{ods}g_m R_G$$

$$\text{where } r_{ods} = r_o \parallel \frac{R_D}{1 + (g_m + g_{mb})R_S}$$
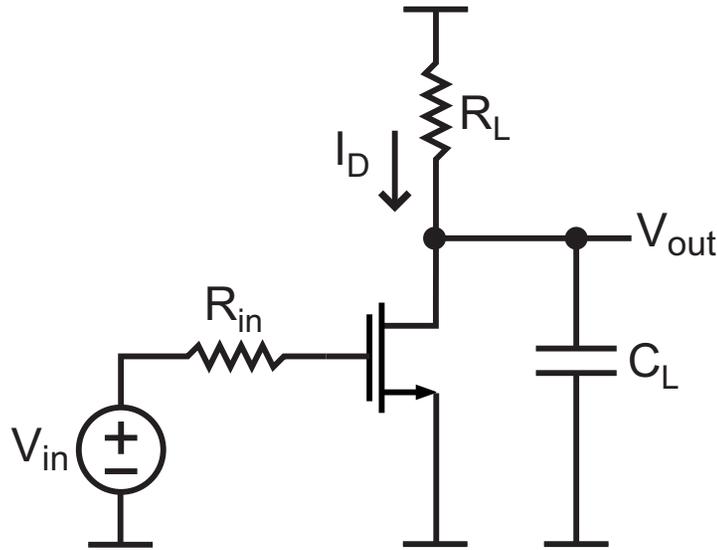
# OCT Example: Design Wide Bandwidth Amplifier



## Assumptions:

$$g_m = 1/(100\Omega), \gamma = 0, \lambda = 0$$

$$C_{gs} = 10\text{fF}, C_{gd} = 3\text{fF}$$

$$C_{sb} = 5\text{fF}, C_{db} = 4\text{fF}$$


$$R_{in} = 4\text{k}\Omega$$

$$R_L = 1\text{k}\Omega$$

$$C_L = 100\text{fF}$$

- **Step 1: identify AC coupling versus OCT capacitors**
  - AC coupling caps will be regarded as shorts
- **Step 2: calculate individual OCT time constants**
- **Step 3: identify long OCT time constants and modify circuit to improve its bandwidth**

## Step 1: Identify OCT Capacitors

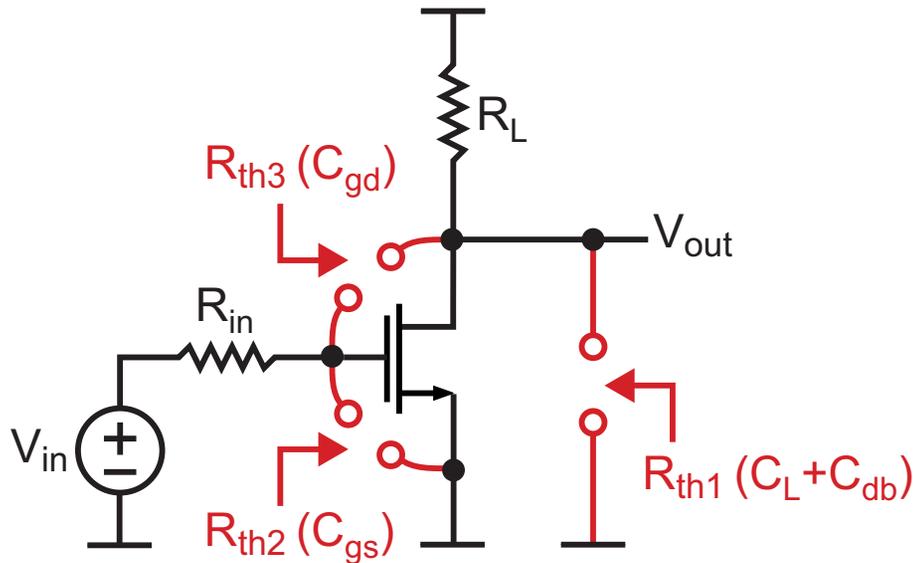

### Assumptions:

$$g_m = 1/(100\Omega), \gamma = 0, \lambda = 0$$

$$C_{gs} = 10\text{fF}, C_{gd} = 3\text{fF}$$

$$C_{sb} = 5\text{fF}, C_{db} = 4\text{fF}$$


$$R_{in} = 4\text{k}\Omega$$

$$R_L = 1\text{k}\Omega$$

$$C_L = 100\text{fF}$$

- Which time constants are easy to calculate?
- How do we efficiently calculate the more difficult cases?
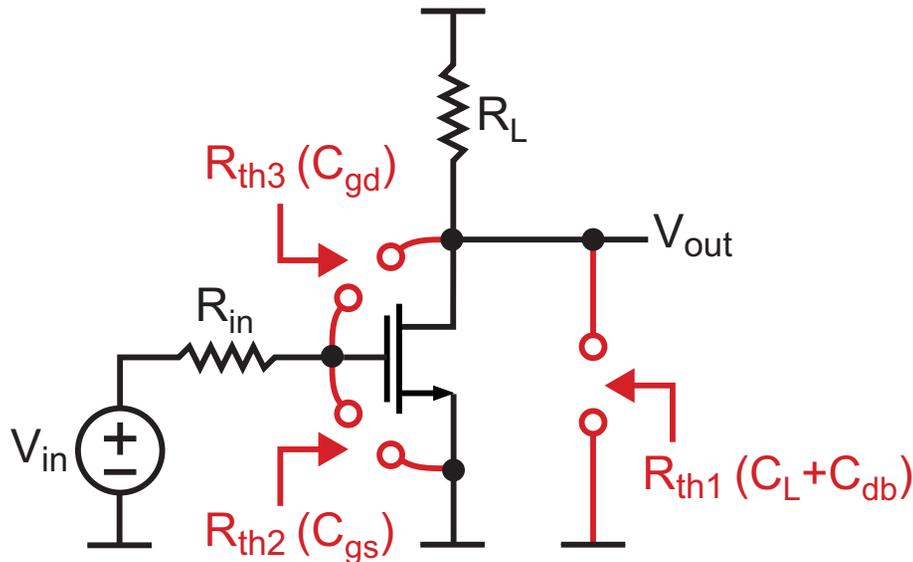
## Step 2: OCT Time Constant Calculations



### Assumptions:

$$g_m = 1/(100\Omega), \gamma = 0, \lambda = 0$$

$$C_{gs} = 10\text{fF}, C_{gd} = 3\text{fF}$$

$$C_{sb} = 5\text{fF}, C_{db} = 4\text{fF}$$

$$R_{in} = 4\text{k}\Omega$$

$$R_L = 1\text{k}\Omega$$

$$C_L = 100\text{fF}$$

### ■ Easy ones:

$$R_{th1} = R_L \parallel R_{th_d} = R_L \parallel \infty = R_L = 1\text{k}\Omega \Rightarrow \tau_1 = 1\text{k}\Omega \cdot 104\text{fF} = \boxed{104\text{ps}}$$

$$R_{th2} = R_{in} \parallel R_{th_g} = R_{in} \parallel \infty = R_{in} = 4\text{k}\Omega \Rightarrow \tau_2 = 4\text{k}\Omega \cdot 10\text{fF} = \boxed{40\text{ps}}$$

### ■ Use formula for $\tau_3$ :


$$R_{th_{ad}} = (R_D + R_G)(1 - r_{ods}/r_o) + r_{ods}g_m R_G$$

$$\text{where } r_{ods} = r_o \parallel \frac{R_D}{1 + (g_m + g_{mb})R_S} = R_D = R_L$$

$$\Rightarrow R_{th3} = (R_L + R_{in})(1 - 0) + R_L g_m R_{in} = 5.5\text{k}\Omega + 40\text{k}\Omega = 45.5\text{k}\Omega$$

$$\Rightarrow \tau_3 = 45.5\text{k}\Omega \cdot 3\text{fF} = \boxed{136.5\text{ps}}$$
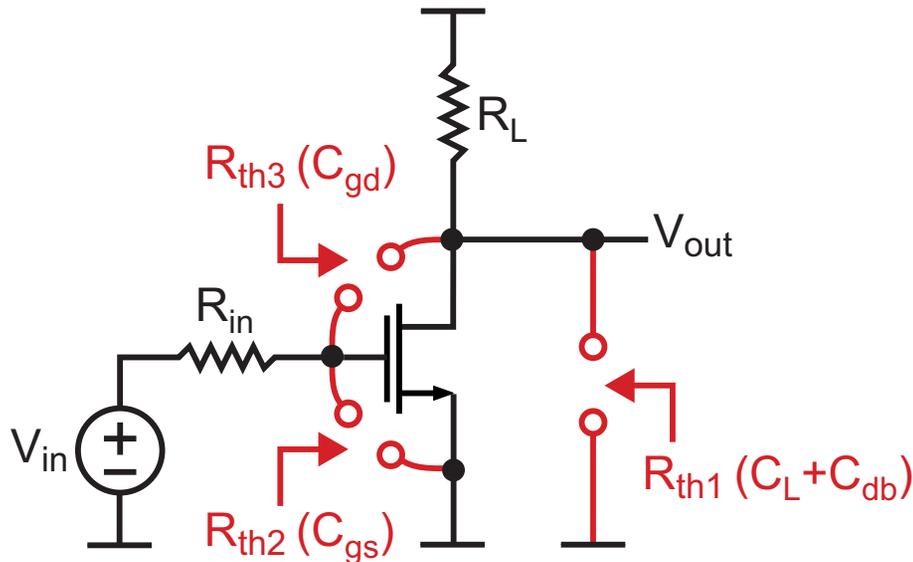
## Step 3: Identify Largest OCT Time Constant



### Assumptions:

$$g_m = 1/(100\Omega), \gamma = 0, \lambda = 0$$

$$C_{gs} = 10\text{fF}, C_{gd} = 3\text{fF}$$

$$C_{sb} = 5\text{fF}, C_{db} = 4\text{fF}$$

$$R_{in} = 4\text{k}\Omega$$

$$R_L = 1\text{k}\Omega$$


$$C_L = 100\text{fF}$$

- Time constant associated with  $C_{gd}$  is the longest:

$$\tau_3 = 45.5\text{k}\Omega \cdot 3\text{fF} = \boxed{136.5\text{ps}}$$

- Why is this time constant so large given that it is associated with the lowest value capacitor?
- How do we change the amplifier topology to reduce this time constant value?
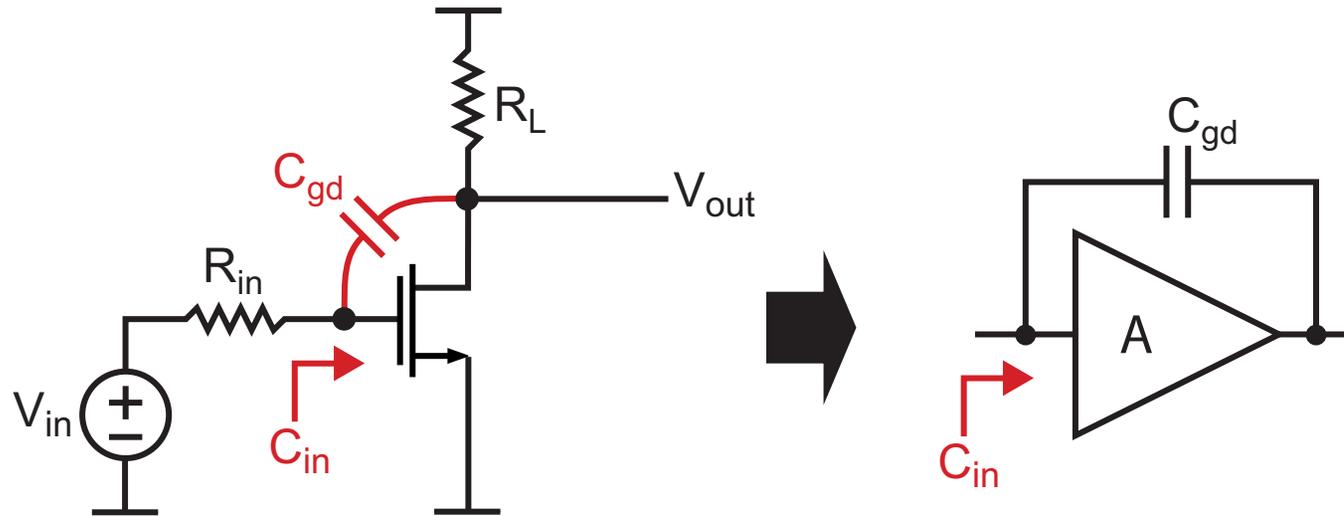
# The Miller Effect Analysis Provides Helpful Intuition



- Notice that  $C_{gd}$  is in the feedback path of the common source amplifier

- Recall Miller effect calculation:  $C_{in} = (1 - A)C_{gd}$

- For this amplifier:


$$A = -g_m R_L \Rightarrow C_{in} = (1 + g_m R_L)C_{gd} = 11 \cdot C_{gd} = 33 \text{ fF}$$

$$\Rightarrow \tau_3 = R_{in} C_{in} = 4 \text{ k}\Omega \cdot 33 \text{ fF} = 132 \text{ ps}$$

- This analysis agrees well with OCT calculation of 136.5ps

**Can we change the amplifier topology to lower this time constant?**

# Consider Adding a Cascode Device

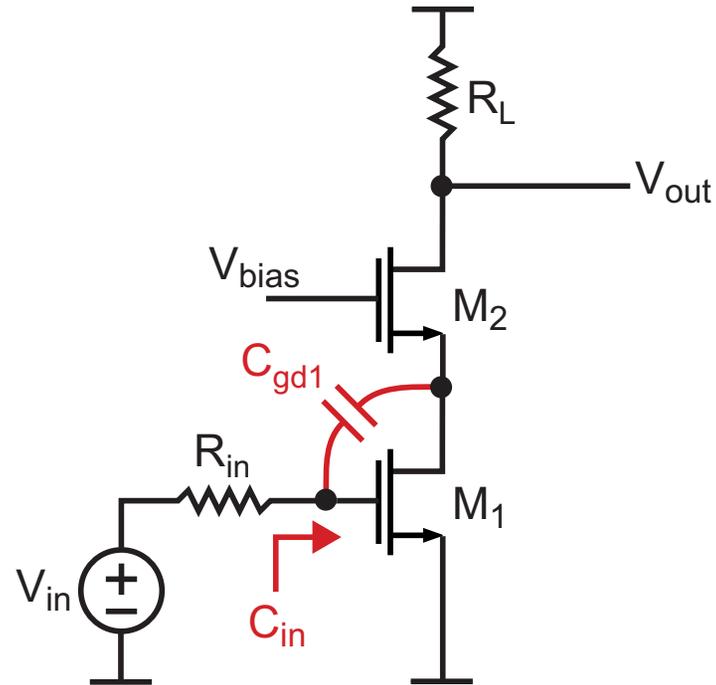


- Examine the impact of this topological change using the Miller Effect analysis

$$A = -g_{m1} \frac{1}{g_{m2}} \approx -1 \Rightarrow C_{in} = (1 + 1)C_{gd1} = 2 \cdot C_{gd1} = 6fF$$

$$\Rightarrow \tau_3 = R_{in} C_{in} = 4k\Omega \cdot 6fF = 24ps$$

**Cascode device dramatically reduces the  $C_{gd1}$  time constant!**
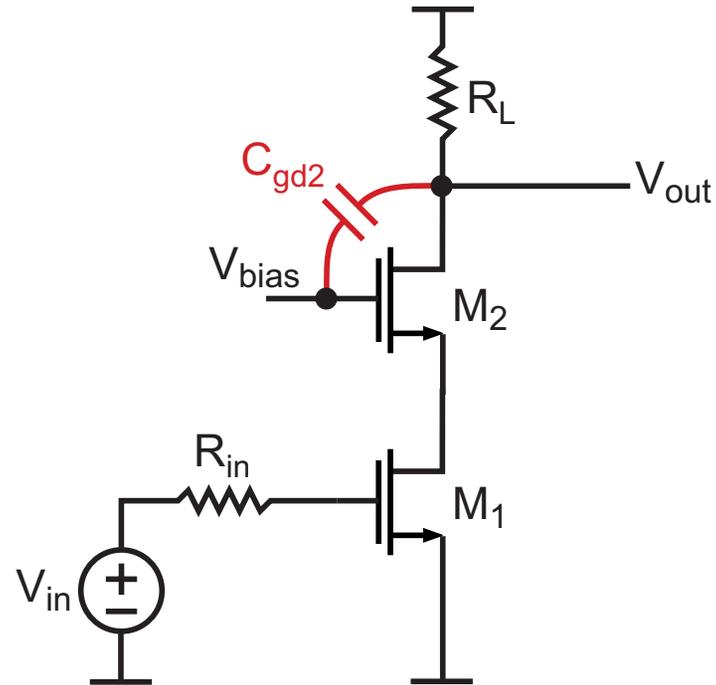
# Does the Miller Effect Impact the Cascode Device?




- Observe that the capacitance seen by  $V_{bias}$  is not of concern since this voltage is not part of the signal path
- The signal path sees the time constant:

$$\tau_4 = R_L || R_{th_{d2}} \cdot C_{gd2} \approx R_L \cdot C_{gd2} = 1k\Omega \cdot 3fF = 3ps$$

- This time constant is much smaller than the other time constants of the amplifier
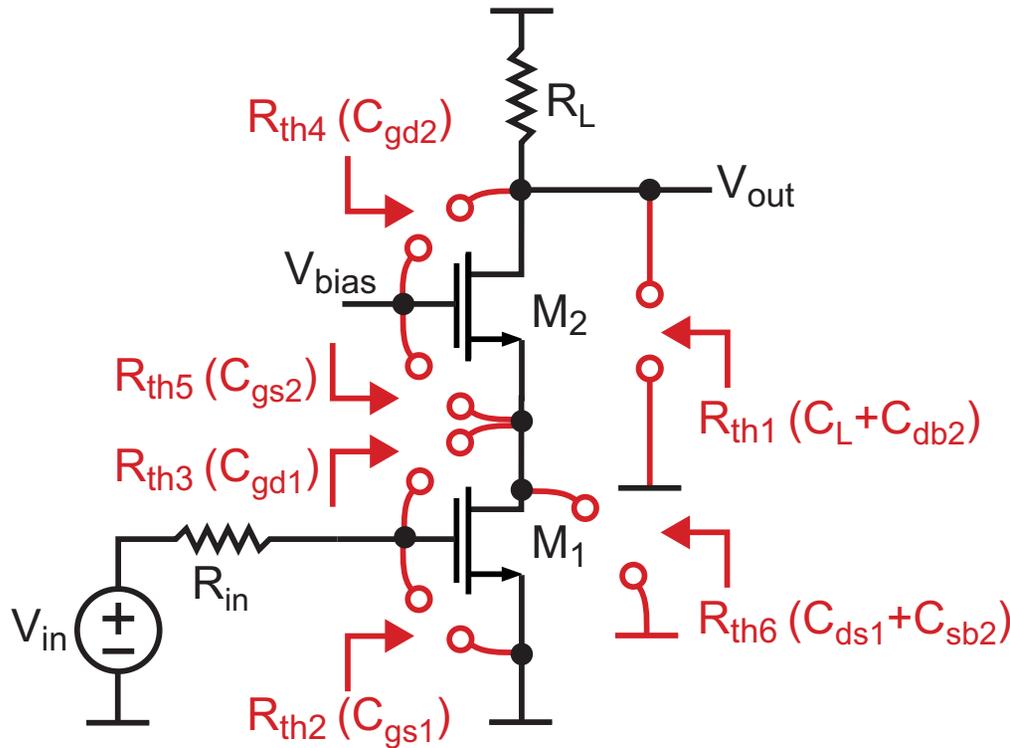
# Perform OCT Calculations for Updated Amplifier



## Assumptions for all devices:

$$g_m = 1/(100\Omega), \gamma = 0, \lambda = 0$$

$$C_{gs} = 10\text{fF}, C_{gd} = 3\text{fF}$$

$$C_{sb} = 5\text{fF}, C_{db} = 4\text{fF}$$

$$R_{in} = 4\text{k}\Omega$$

$$R_L = 1\text{k}\Omega$$

$$C_L = 100\text{fF}$$

$$R_{th1} = R_L || R_{th_{d2}} = R_L = 1\text{k}\Omega \Rightarrow \tau_1 = 1\text{k}\Omega \cdot 104\text{fF} = \boxed{104\text{ps}}$$


$$R_{th2} = R_{in} || R_{th_{g1}} = R_{in} = 4\text{k}\Omega \Rightarrow \tau_2 = 4\text{k}\Omega \cdot 10\text{fF} = \boxed{40\text{ps}}$$

$$R_{th4} = R_L || R_{th_{d2}} \approx R_L = 1\text{k}\Omega \Rightarrow \tau_3 = 1\text{k}\Omega \cdot 3\text{fF} = \boxed{3\text{ps}}$$

$$R_{th5} = R_{th_{s2}} || R_{th_{d1}} \approx 1/g_{m2} || \infty = 100\Omega \Rightarrow \tau_5 = 100\Omega \cdot 10\text{fF} = \boxed{1\text{ps}}$$

$$R_{th6} = R_{th_{d1}} || R_{th_{s2}} = \infty || 1/g_{m2} = 100\Omega \Rightarrow \tau_6 = 100\Omega \cdot 9\text{fF} = \boxed{0.9\text{ps}}$$
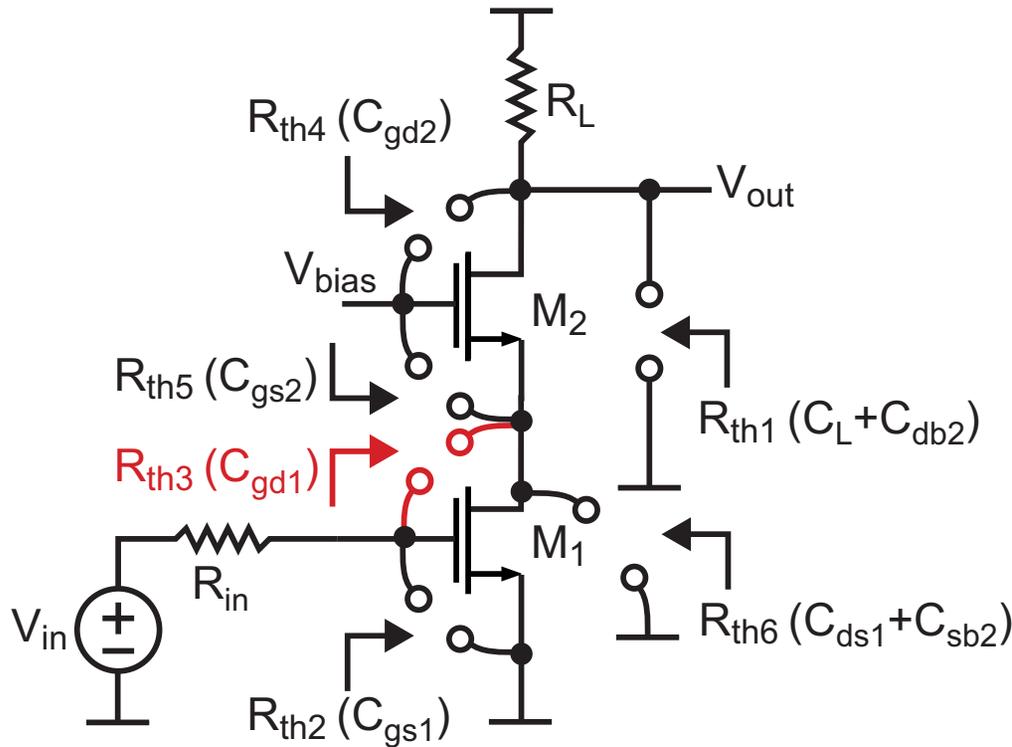
# Perform OCT Calculations for Updated Amplifier



## Assumptions for all devices:

$$g_m = 1/(100\Omega), \gamma = 0, \lambda = 0$$

$$C_{gs} = 10\text{fF}, C_{gd} = 3\text{fF}$$

$$C_{sb} = 5\text{fF}, C_{db} = 4\text{fF}$$

$$R_{in} = 4\text{k}\Omega$$

$$R_L = 1\text{k}\Omega$$

$$C_L = 100\text{fF}$$

## ■ Use Thevenin formula for $C_{gd}$ calculation:


$$R_{th3} = (R_{D1} + R_{G1})(1 - r_{ods}/r_{o1}) + r_{ods}g_{m1}R_{G1}$$

$$\text{where } r_{ods} = r_{o1} \parallel \frac{R_{D1}}{1 + (g_{m1} + g_{mb1})R_{S1}}$$

$$\Rightarrow R_{th3} = \left(\frac{1}{g_{m2}} + R_{in}\right)(1 - 0) + \frac{1}{g_{m2}}g_{m1}R_{in} = 4.1\text{k}\Omega + 4\text{k}\Omega = 8.1\text{k}\Omega$$

$$\Rightarrow \tau_3 = 8.1\text{k}\Omega \cdot 3\text{fF} = \boxed{24.3\text{ps}}$$

## Identify Longest OCT Time Constant

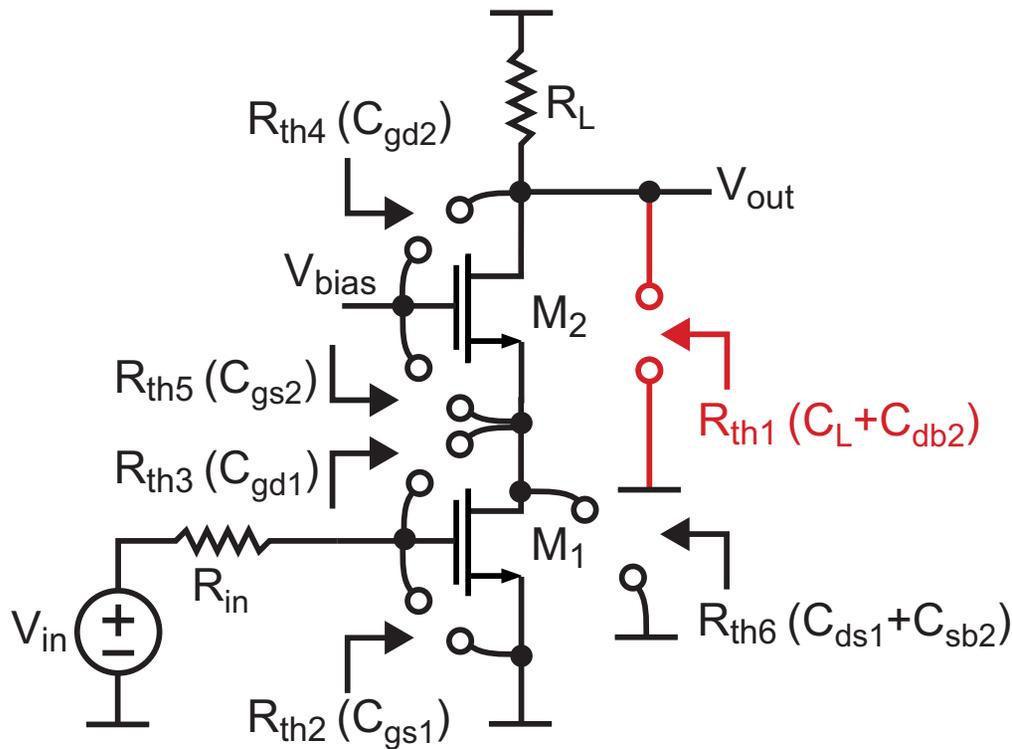

### Assumptions for all devices:

$$g_m = 1/(100\Omega), \gamma = 0, \lambda = 0$$

$$C_{gs} = 10\text{fF}, C_{gd} = 3\text{fF}$$

$$C_{sb} = 5\text{fF}, C_{db} = 4\text{fF}$$

$$R_{in} = 4\text{k}\Omega$$

$$R_L = 1\text{k}\Omega$$


$$C_L = 100\text{fF}$$

- The load capacitance now presents the largest time constant:

$$R_{th1} = R_L || R_{th_{d2}} = R_L = 1\text{k}\Omega \Rightarrow \tau_1 = 1\text{k}\Omega \cdot 104\text{fF} = \boxed{104\text{ps}}$$

Can we change the amplifier topology to lower this time constant?

## Add a Source Follower to the Output

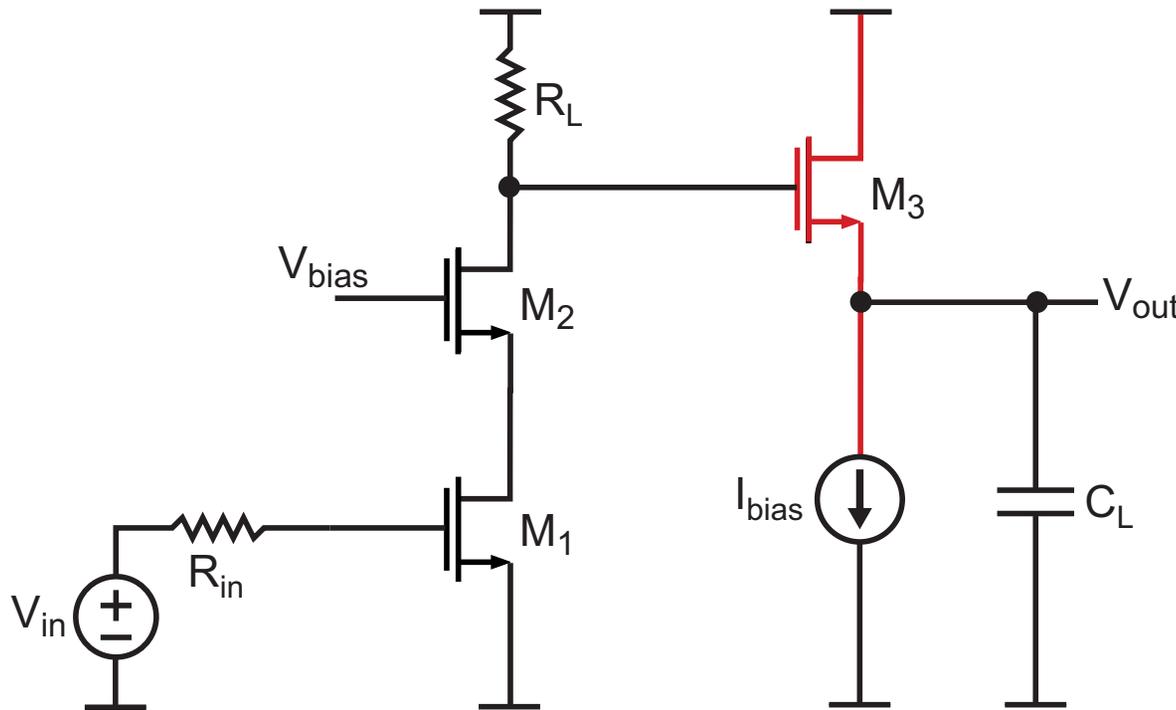

**For all devices:**

$$g_m = 1/(100\Omega), \gamma = 0, \lambda = 0$$

$$C_{gs} = 10\text{fF}, C_{gd} = 3\text{fF}$$

$$C_{sb} = 5\text{fF}, C_{db} = 4\text{fF}$$

$$R_{in} = 4\text{k}\Omega$$


$$R_L = 1\text{k}\Omega$$

$$C_L = 100\text{fF}$$

- **Key idea:** reduce the time constant associated with  $C_L$  by decreasing the Thevenin resistance that it sees
  - Previous design presented  $R_L = 1\text{K}\Omega$  to  $C_L$
  - Source follower presents  $R_{\text{ths3}} = 1/g_{m3} = 100\Omega$  to  $C_L$

**Source follower should reduce  $C_L$  time constant by a factor of ten!**

# Calculation of New $C_L$ Time Constant

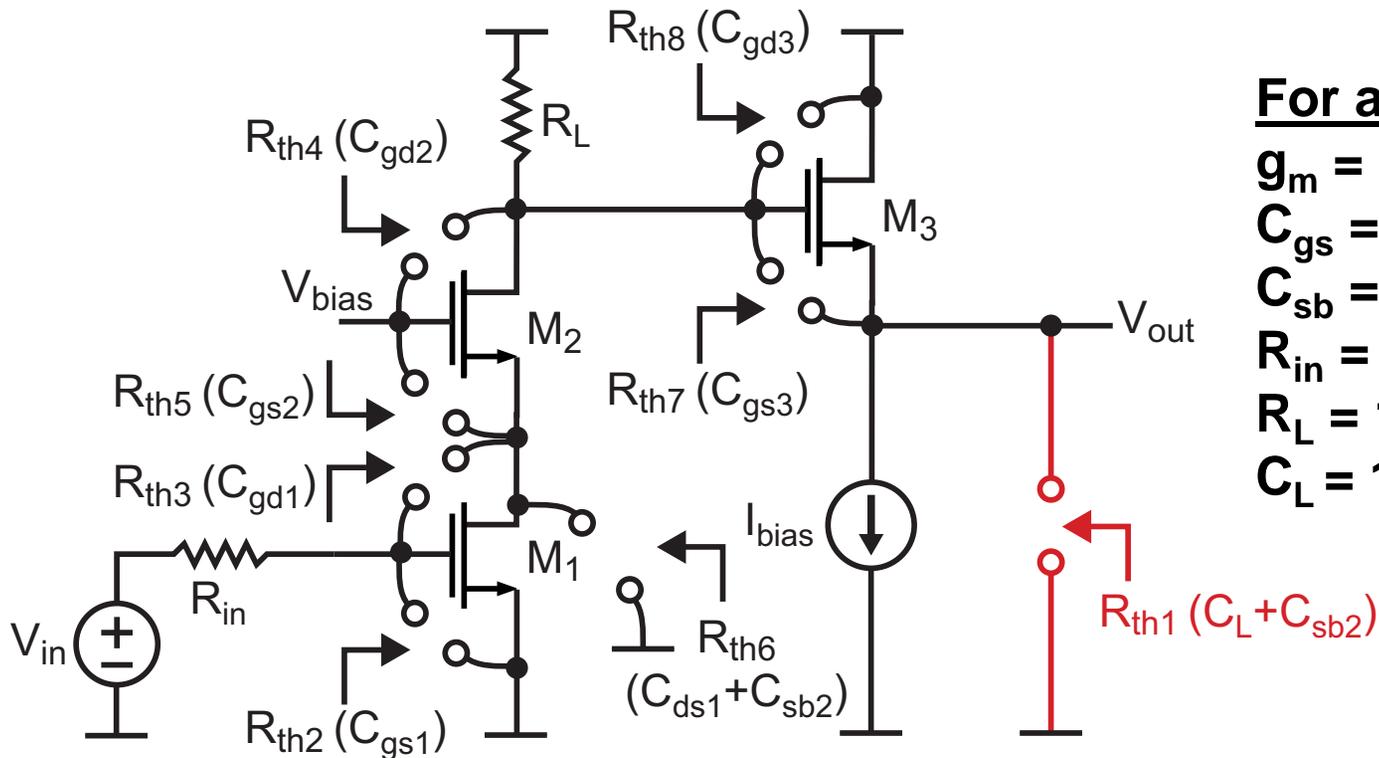

**For all devices:**

$$g_m = 1/(100\Omega), \gamma = 0, \lambda = 0$$

$$C_{gs} = 10\text{fF}, C_{gd} = 3\text{fF}$$

$$C_{sb} = 5\text{fF}, C_{db} = 4\text{fF}$$

$$R_{in} = 4\text{k}\Omega$$

$$R_L = 1\text{k}\Omega$$


$$C_L = 100\text{fF}$$

## Formal calculation:

$$R_{th1} = R_{th_{s3}} = 1/g_{m3} = 100\Omega \Rightarrow \tau_1 = 100\Omega \cdot 104\text{fF} = \boxed{10.4\text{ps}}$$

**How large are the additional time constants created by  $M_3$ ?**
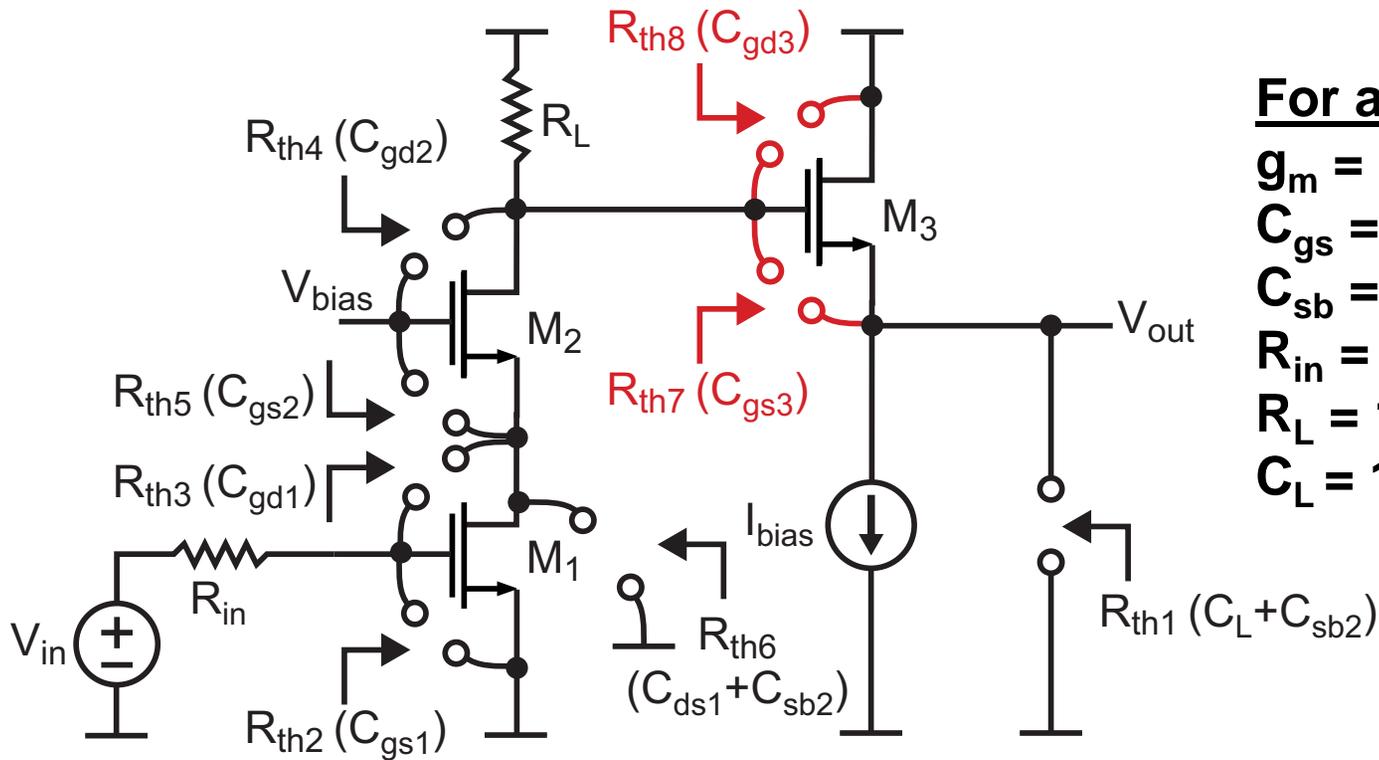
# Calculation of Additional Time Constants from $M_3$



**For all devices:**

$$g_m = 1/(100\Omega), \gamma = 0, \lambda = 0$$

$$C_{gs} = 10\text{fF}, C_{gd} = 3\text{fF}$$

$$C_{sb} = 5\text{fF}, C_{db} = 4\text{fF}$$

$$R_{in} = 4\text{k}\Omega$$

$$R_L = 1\text{k}\Omega$$

$$C_L = 100\text{fF}$$


$$R_{th8} = R_L || R_{th_{d2}} \approx R_L = 1\text{k}\Omega \Rightarrow \tau_8 = 1\text{k}\Omega \cdot 3\text{fF} = \boxed{3\text{ps}}$$

$$R_{th7} = \frac{R_{S3}(1 + R_{D3}/r_{o3}) + R_{G3}(1 + (g_{mb3} + 1/r_{o3})R_{S3} + R_{D3}/r_{o3})}{1 + (g_{m3} + g_{mb3})R_{S3} + (R_{S3} + R_{D3})/r_{o3}}$$

$$\Rightarrow R_{th7} = \frac{1 + R_{D3}/r_{o3} + R_{G3}(g_{mb3} + 1/r_{o3})}{g_{m3} + g_{mb3} + 1/r_{o3}} = \frac{1 + 0 + 0}{g_{m3} + 0 + 0} = 100\Omega$$

$$\Rightarrow \tau_7 = 100\Omega \cdot 10\text{fF} = \boxed{1\text{ps}}$$
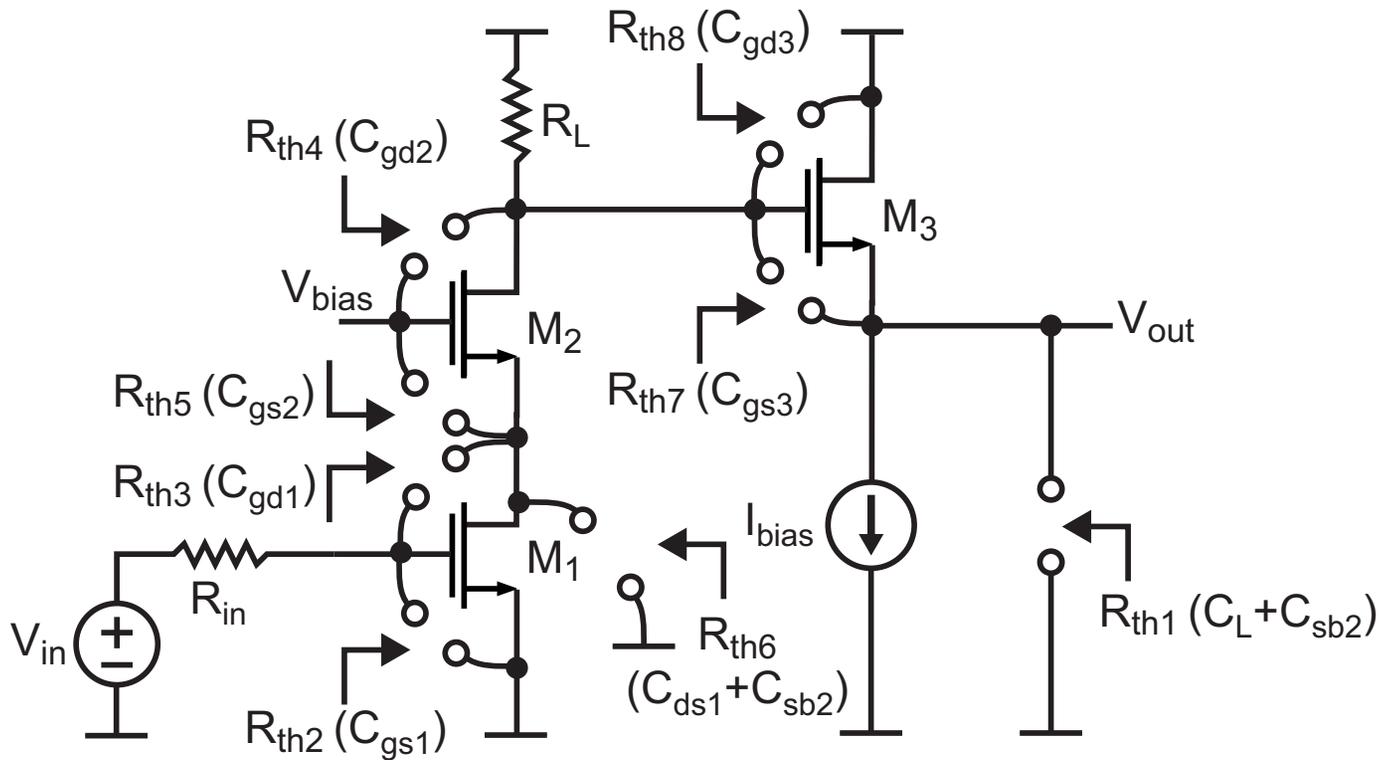
# Estimate Bandwidth Based on OCT Calculations



- $\tau_1 = 10.4ps$
- $\tau_2 = 40ps$
- $\tau_3 = 24.3ps$
- $\tau_4 = 3ps$
- $\tau_5 = 1ps$
- $\tau_6 = 0.9ps$
- $\tau_7 = 1ps$
- $\tau_8 = 3ps$

$$BW \approx \frac{1}{\sum_{j=1}^m R_{thj} C_j} = \frac{1}{83.6ps} = 11.96 \text{ Grad/s}$$

$$\Rightarrow BW \approx \frac{11.96}{2\pi} = \boxed{1.9GHz}$$

# Summary

---

- **Two techniques prove very useful when designing amplifiers for desired frequency response behavior**
  - **Open Circuit Time Constant method**
  - **Miller Effect analysis**
- **Thevenin resistance analysis in combination with the above offers tremendous insight for designing amplifier topologies**
  - **OCT method allows quick discovery of large time constants**
  - **Miller effect provides intuition of the impact of placing capacitors within feedback**
  - **Awareness of impedances presented by various amplifier stages allows intuitive approach to achieve reduction of large time constants**