


MIC511
Analysis and Design of Analog Integrated Circuits
Lecture 11

Examples

Michael H. Perrott
Masdar Institute of Science and Technology
March 4, 2012

Copyright © 2012 by Michael H. Perrott
All rights reserved

Example Analysis Circuit

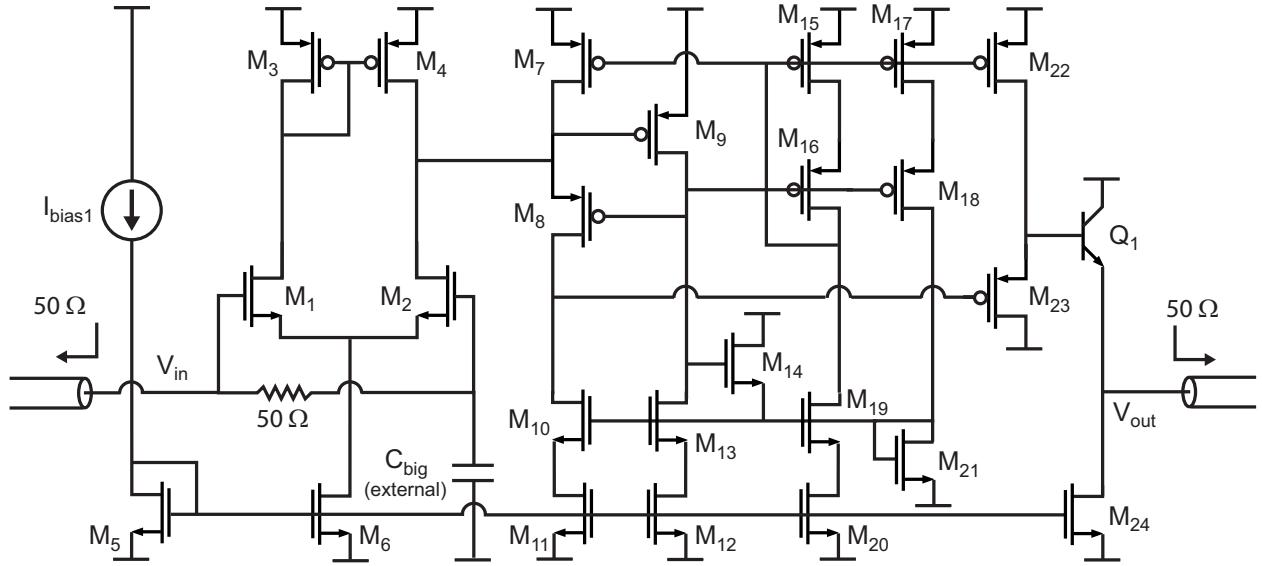

- Assumptions

1. Intrinsic gain of each device $\gg 1$

$$g_m r_o \gg 1 \implies 1/g_m \ll r_o$$



2. Intrinsic gain of devices similar in value
3. Output resistances of devices similar in value

$$r_{o1} \approx r_{o2}$$


- Note:

- Assumption 1 is reasonable in practice
- Assumptions 2 and 3 are invalid in practice
 - * Used here only for pedagogical reasons

Replace Current Sources

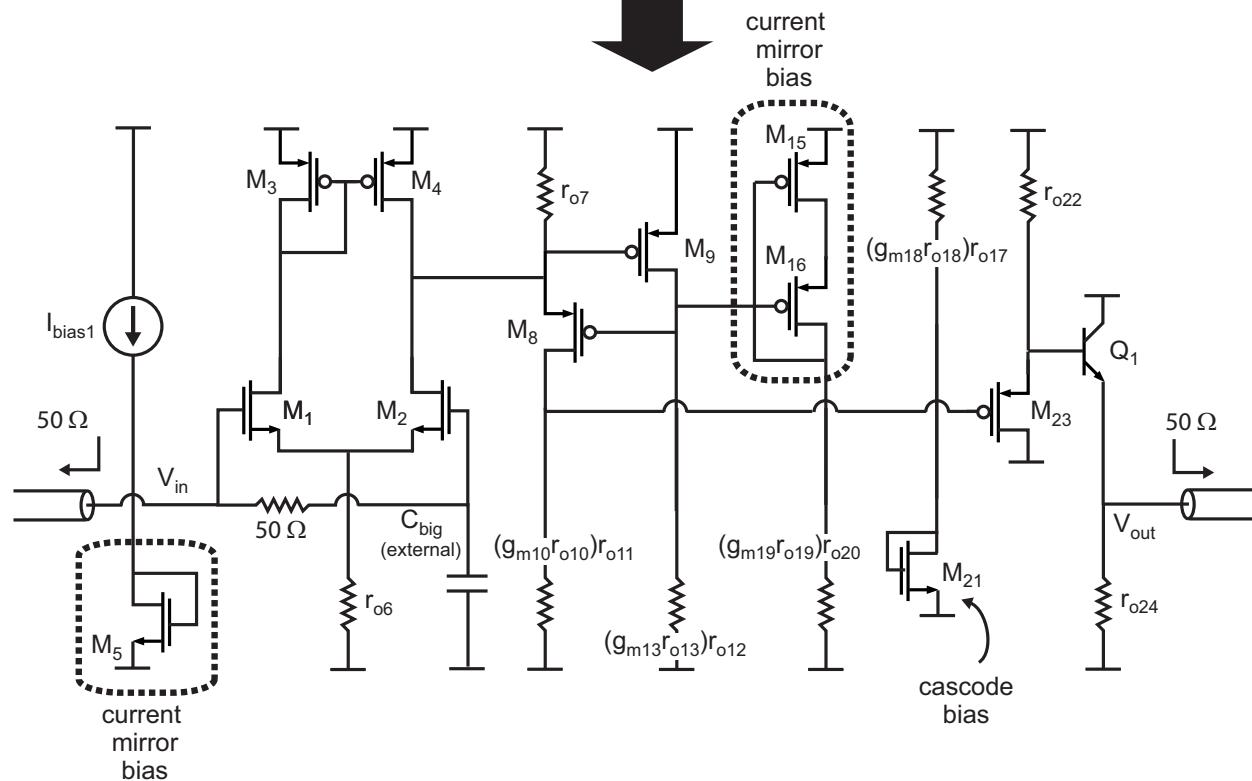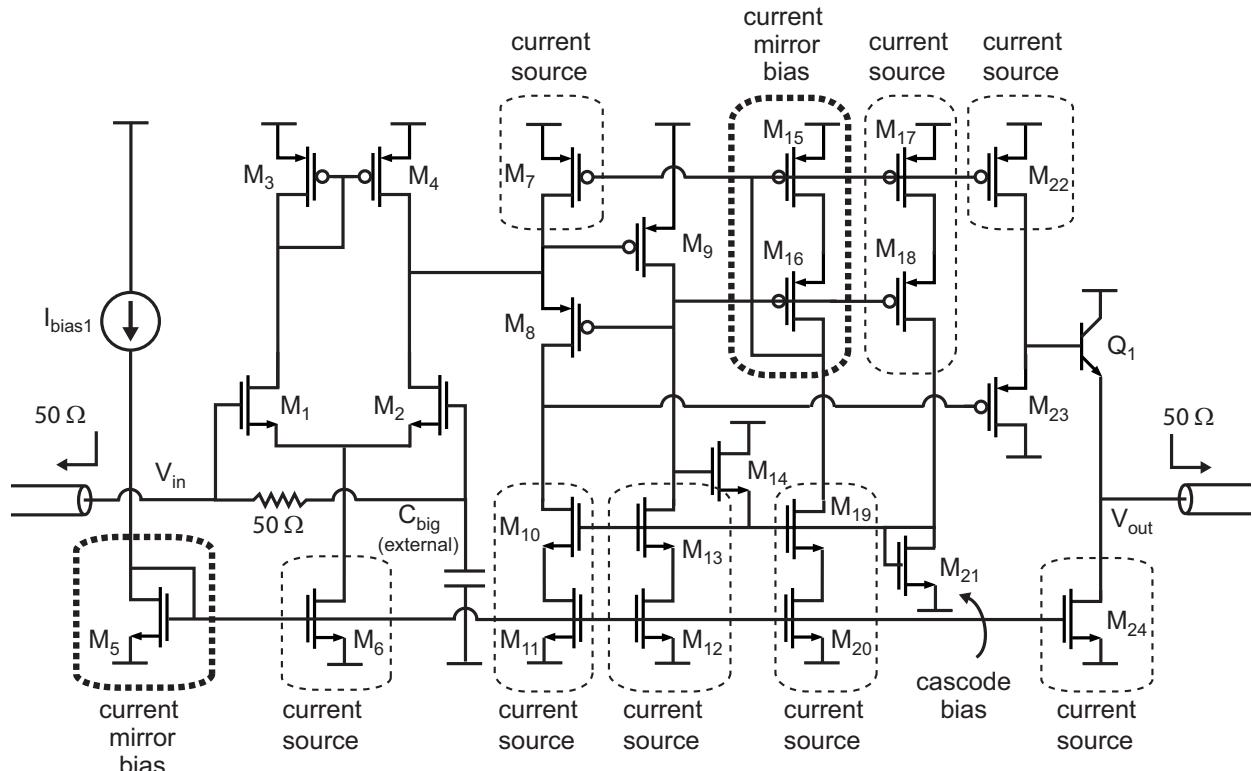


Remove Non-Signal-Path Biasing Circuitry

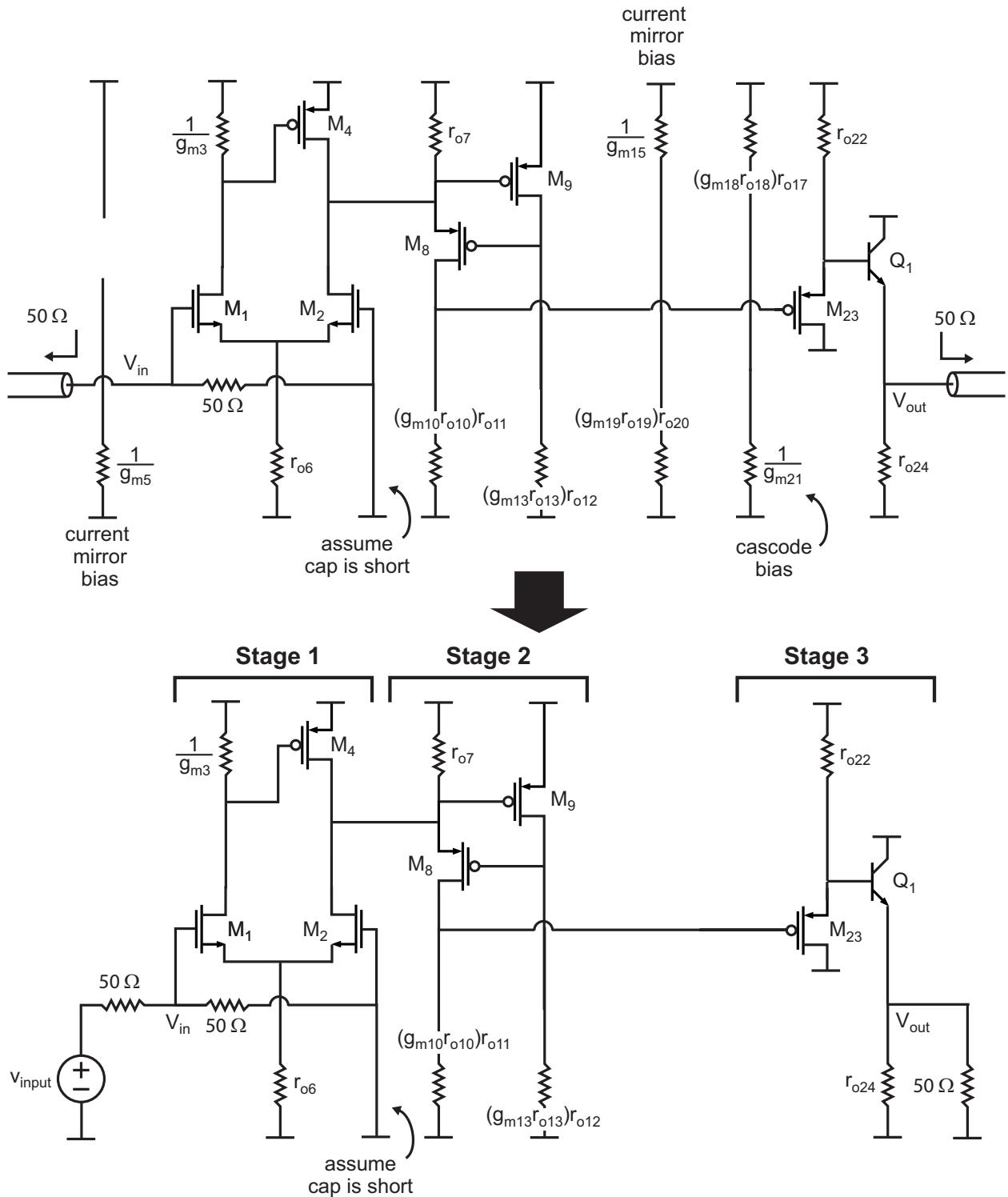


Bipolar Modeling is similar to CMOS

MOSFET	BIPOLAR
<p>Key Small-Signal Parameters</p> $g_m = \mu_n C_{ox} (W/L) (V_{GS} - V_{TH})$ $= \sqrt{2\mu_n C_{ox} (W/L) I_D}$ $g_{mb} \ll g_m$ $r_o = \frac{1}{\lambda I_D}$	<p>Key Small-Signal Parameters</p> $g_m = \frac{I_c}{V_t}, V_t = \frac{kT}{q}$ $V_t \approx 25 \text{ mV at room temp}$ $r_\pi = \frac{\beta_o}{g_m}, \beta_o \approx 100 \text{ to } 200$ $r_o = \frac{V_A}{I_c}, V_A \approx 100 \text{ to } 200 \text{ V}$
<p>Thevenin Resistances</p>	<p>Thevenin Resistances</p>
<p>Approximation</p> $R_{th_d} = r_o (1 + g_m R_S)$ $R_{th_g} = \text{infinite}$ $R_{th_s} = \frac{1 + R_D / r_o}{g_m}$	<p>Assumption</p> $g_{mb} \ll g_m$
<p>Approximation</p> $R_{th_c} = r_o (1 + g_m (r_\pi R_E))$ $R_{th_b} = r_\pi + \beta_o R_E$ $R_{th_e} = 1/g_m + R_B / \beta_o$	<p>Assumption</p> $R_B \ll r_\pi$ $R_C + R_E \ll r_o$ $R_C \ll \beta_o r_o$
<p>General Thevenin Model</p>	<p>General Thevenin Model</p>
<p>Approximation</p> $A_v = 1$ $\alpha = 1$	<p>Assumption</p> $g_{mb} \ll g_m, g_m r_o \gg 1$ $R_d \ll R_{thd}$
<p>Approximation</p> $A_v = 1$ $\alpha = 1$	<p>Assumption</p> $R_C + R_E \ll r_o, R_B \ll r_\pi$ $R_C + R_E \ll \beta_o r_o$


Compute 2-port for Stage 3

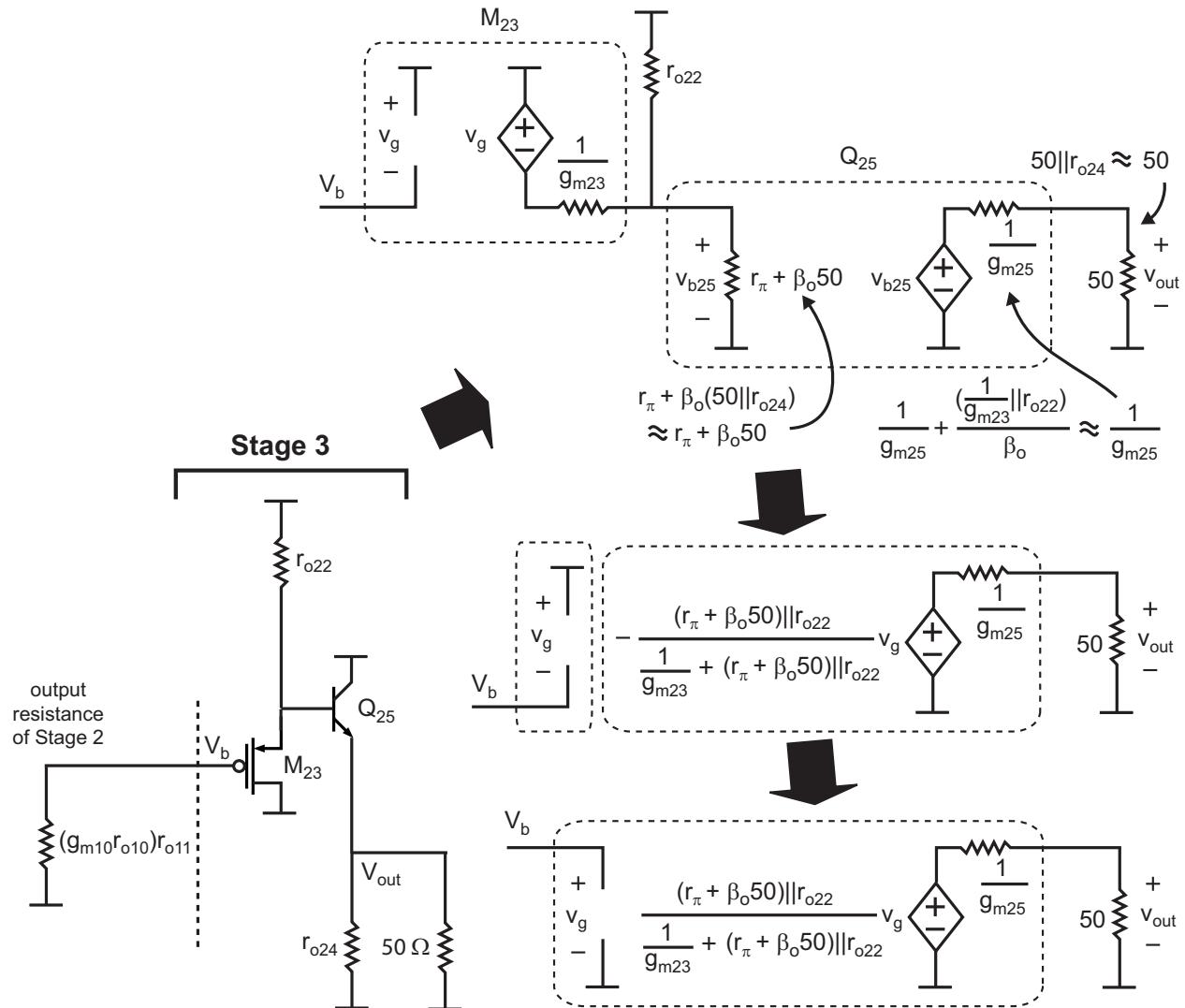

Compute 2-port for Stage 2

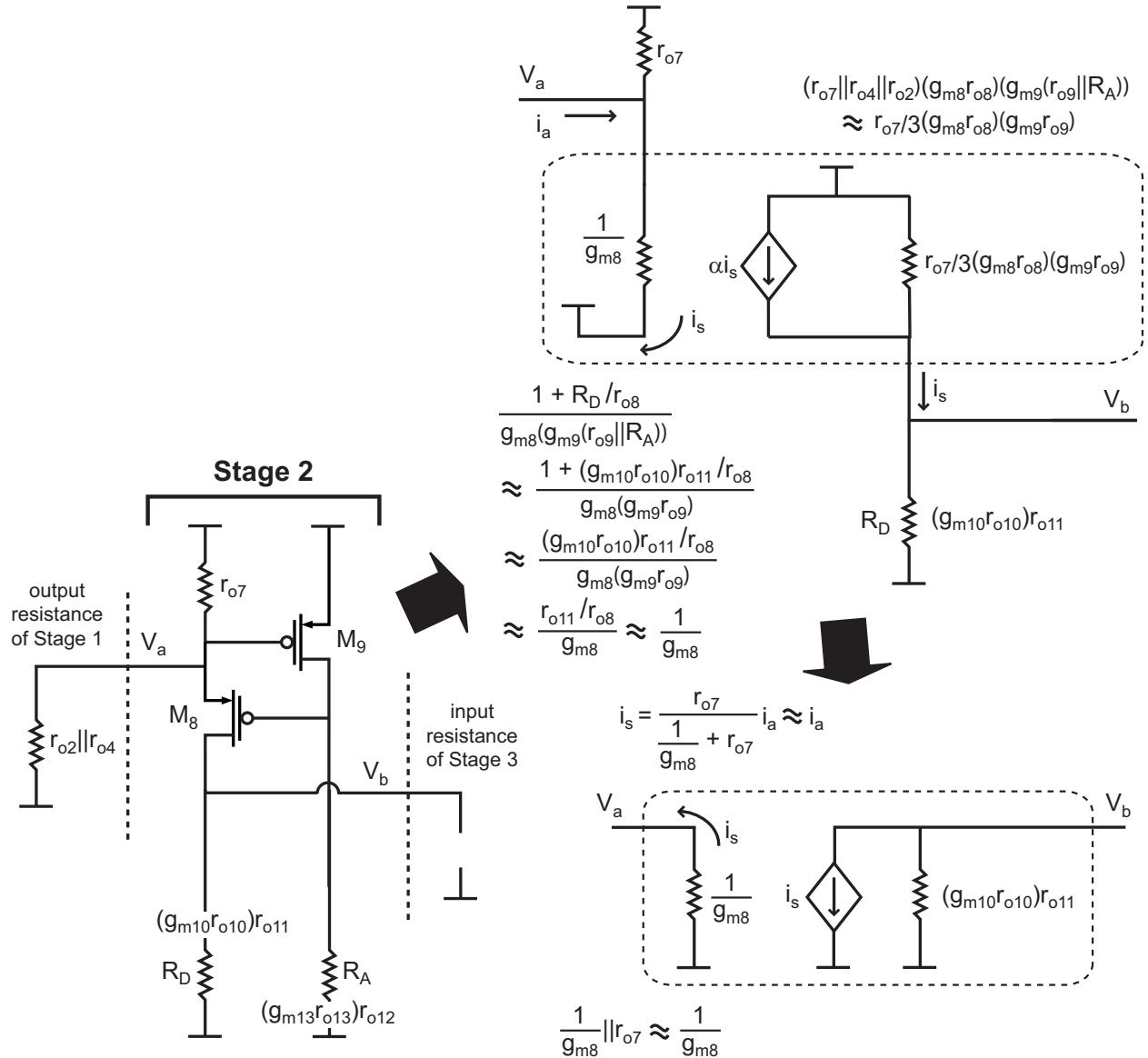


Compute 2-port for Stage 1 (Step 1)

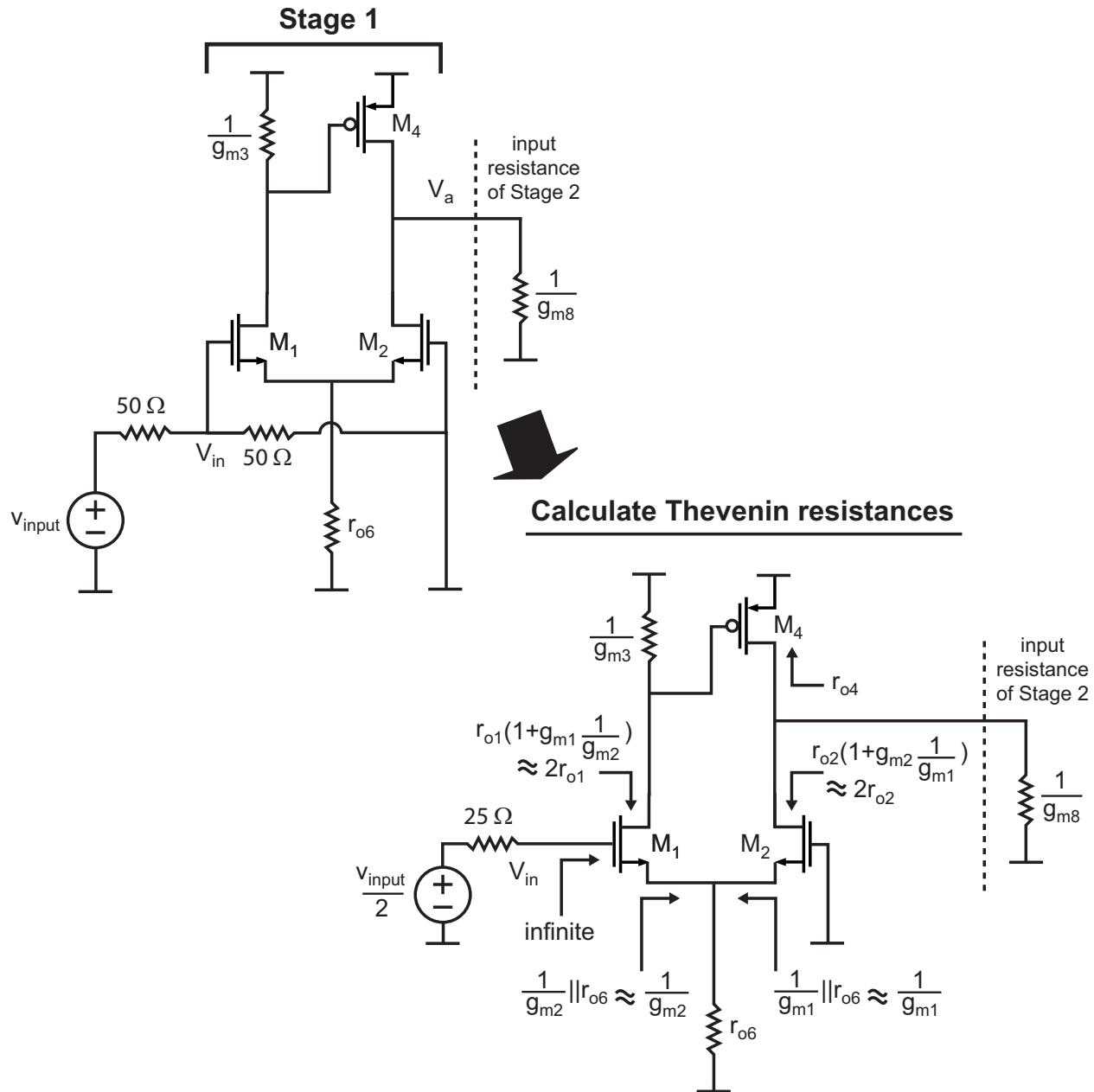


Compute 2-port for Stage 1 (Step 2)

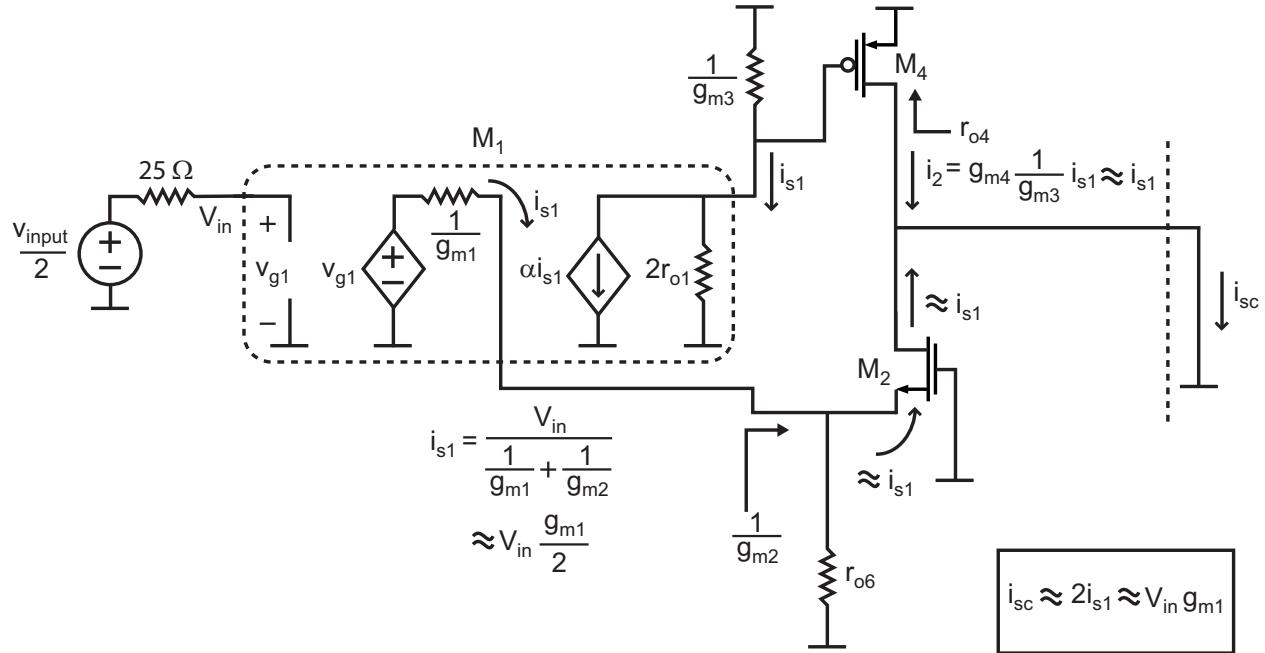
Calculate short circuit current at output




Calculate output resistance

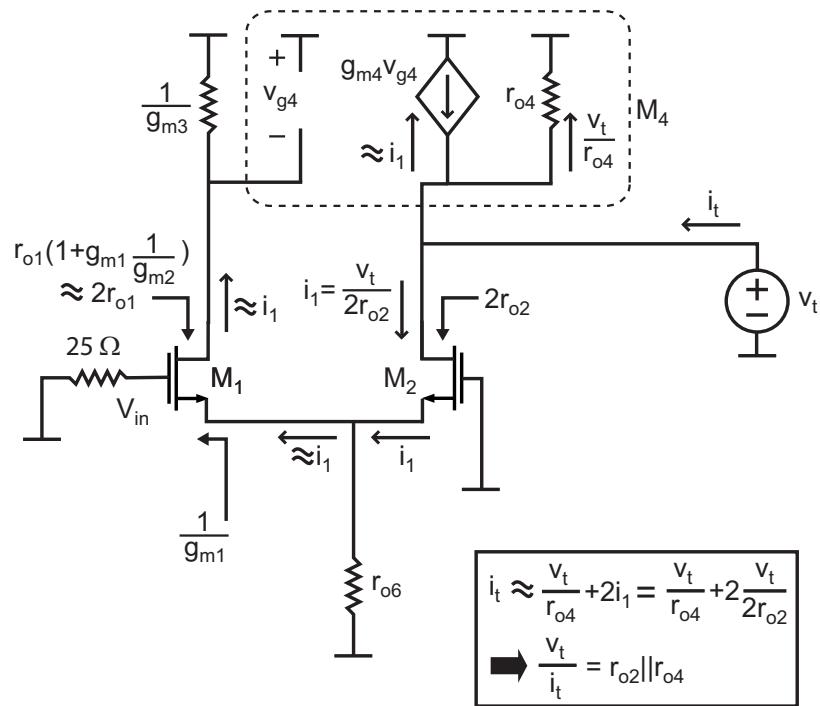

Compute 2-port for Stage 1 (Final Step)

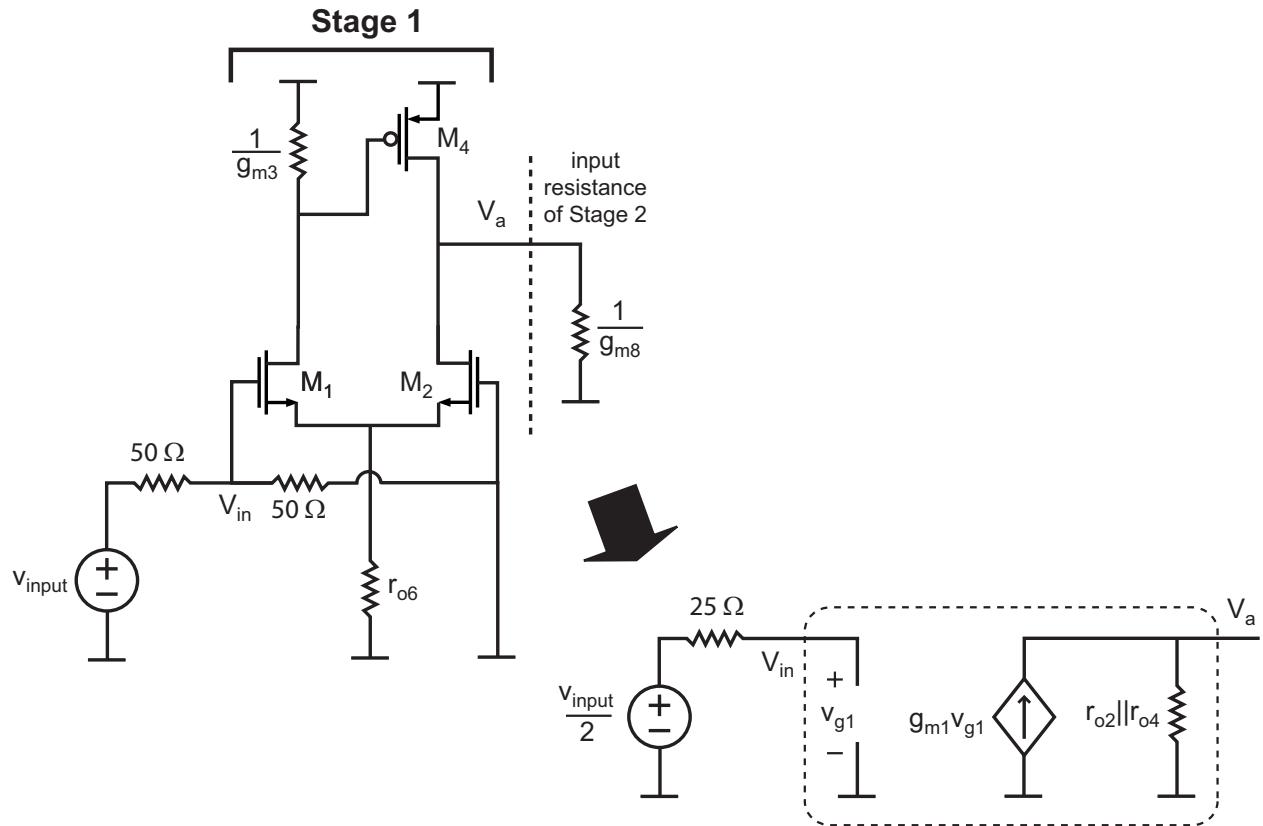

Overall Cascade of 2-ports for Amplifier

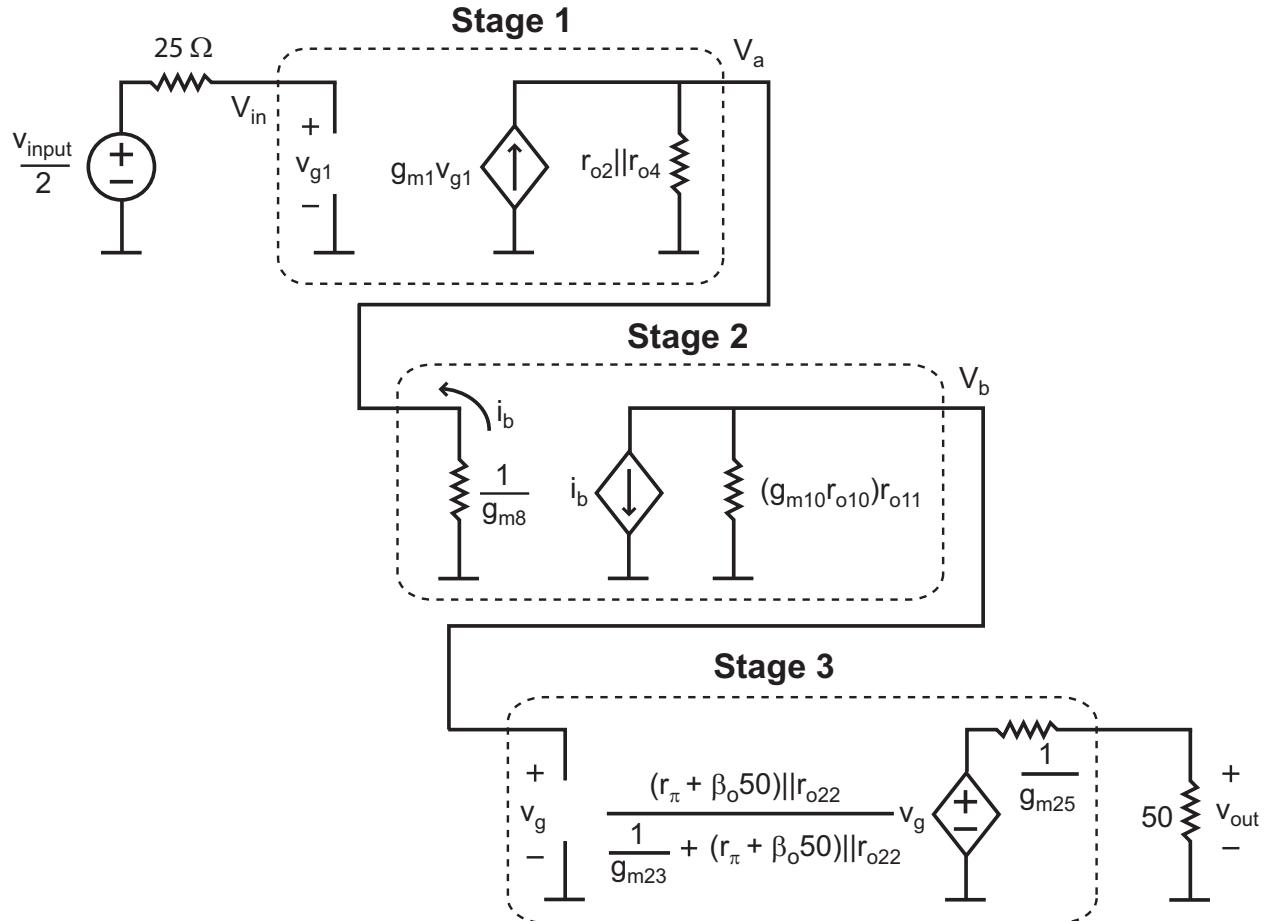

- What is the overall input/output resistance of the amp?
- What is the overall gain?
- Which stage contributes the most gain?
- What is the function of each stage?