

***Analysis and Design of Analog Integrated Circuits***  
***Lecture 17***

***Basic Two Stage CMOS Opamp***


**Michael H. Perrott**

**April 4, 2012**

**Copyright © 2012 by Michael H. Perrott**


**All rights reserved.**
 
# Opamps Are Basic Analog Building Blocks



- **Enable active filters**
  - Can achieve arbitrary pole/zero placement using only capacitor/resistor networks around the opamp
- **Allow accurate voltage to current translation**
- **Provide accurate charge transfer between capacitors**
  - Extremely useful for switched capacitor circuits used in analog-to-digital converters and discrete-time analog filters

 
# Key Specifications of Opamps (Open Loop)



**For Open Loop Characterization**


Set  $R_{huge} \gg |Z_{out}|$

 and  $1/(R_{huge} C_{huge}) \ll \omega_{dom}$



- DC small signal gain:  $K$
- Unity gain frequency:  $\omega_0$
- Dominant pole frequency:  $\omega_{dom}$
- Parasitic pole frequencies:  $\omega_p$  (and higher order poles)
- Output swing (max output range for DC gain  $> K_{min}$ )
 
# Key Specifications of Opamps (Closed Loop)




- Offset voltage
- Settling time (closed loop bandwidth)
- Input common mode range
- Equivalent Input-Referred Noise
- Common-Mode Rejection Ratio (**CMRR**)

$$CMRR = \left( \frac{\delta V_{offset}}{\delta V_{in}} \right)^{-1}$$

- Power Supply Rejection Ratio (**PSRR**)


$$PSRR^+ = \left( \frac{\delta V_{offset}}{\delta V_{dd}} \right)^{-1} \quad PSRR^- = \left( \frac{\delta V_{offset}}{\delta V_{ss}} \right)^{-1}$$

# Slew Rate Issues for Opamps

 


- **Output currents of practical opamps have max limits**
  - Impacts maximum rate of charging or discharging load capacitance,  $C_L$
  - For large step response, this leads to the output lagging behind the ideal response based on linear modeling
    - We refer to this condition as being slew-rate limited
- **Where slew-rate is of concern, the output stage of the opamp can be designed to help mitigate this issue**
  - Will lead to extra complexity and perhaps other issues

# Basic Two Stage CMOS Op Amp

 

- This is a common “workhorse” opamp for medium performance applications
- Provides a nice starting point to discuss various CMOS opamp design issues
- Starting assumptions:  $W_1/L_1 = W_2/L_2$ ,  $W_3/L_3 = W_4/L_4$

# First Stage Analysis

 


- Derive two port model assuming differential input:

$$Z_{in1} = \frac{1}{s(C_{gs1}/2)} = \frac{1}{s(C_{gs2}/2)}$$

$$G_{m1} = g_{m1} = g_{m2}$$

$$R_{out1} = r_{o2} || r_{o4}$$
 
## Derivation of $R_{out1}$ (Incorrect Approach)




- Application of Thevenin analysis seems to imply that

$$R_{out1} = 2r_{o2} || r_{o4}$$

- Why is this incorrect?
 
## Derivation of $R_{out1}$ (Correct Approach)




- **Correct approach includes the impact of the current mirror feedback**

$$i_{test} = i_1 + i_2 = i_1 + i_1 + \frac{v_{test}}{r_{o4}} = 2 \frac{v_{test}}{2r_{o2}} + \frac{v_{test}}{r_{o4}}$$

$$\Rightarrow \boxed{R_{out1} = r_{o2} || r_{o4}}$$

## Derivation of $G_{m1}$

 


- For differential input, we can approximate the source of  $M_1$  and  $M_2$  as being at incremental ground

$$i_1 = -g_{m1}(-v_{id}/2) = \frac{g_{m1}}{2}v_{id}$$

$$i_2 = g_{m2}(v_{id}/2) = \frac{g_{m2}}{2}v_{id} = \frac{g_{m1}}{2}v_{id}$$

$$\Rightarrow i_{out} = g_{m1}v_{id} \Rightarrow \boxed{G_{m1} = g_{m1} = g_{m2}}$$


# Derivation of $Z_{in}$

 

- For differential input, we can simplify the input capacitance calculation through the steps shown at the right

$$\Rightarrow Z_{in1} = \frac{1}{sC_{gs1}/2} = \frac{1}{sC_{gs2}/2}$$

# Second Stage Analysis

 


- Two port model derivation is straightforward
  - This is a common source amplifier

$$Z_{in2} = \frac{1}{sC_{gs6}}$$

$$G_{m2} = g_{m6}$$

$$R_{out2} = r_{o6} || r_{o7}$$

# Overall Opamp Model

 

## Overall transfer function

$$H(s) = \frac{v_{out}(s)}{v_{id}(s)} = \frac{K}{(1 + s/w_{p1})(1 + s/w_{p2})}$$

### DC gain


$$K = g_{m1}(r_{o2} || r_{o4})g_{m6}(r_{o6} || r_{o7})$$

### Poles

$$w_{p1} = \frac{1}{(r_{o2} || r_{o4})C_{gs6}} \quad w_{p2} = \frac{1}{(r_{o6} || r_{o7})C_L}$$

- In general,  $w_{p2} \ll w_{p1}$  since  $C_L \gg C_{gs6}$
 
## Consider The Dominant Pole To Be $w_{p2}$




$$H(s) = \frac{K}{1 + s/w_{p2}} = \frac{g_{m1}(r_{o2}||r_{o4})g_{m6}(r_{o6}||r_{o7})}{1 + s(r_{o6}||r_{o7})C_L}$$

- At frequencies  $\gg w_{p2}$

$$H(s) \approx \frac{g_{m1}(r_{o2}||r_{o4})g_{m6}}{sC_L} \Rightarrow w_0 \approx \frac{g_{m1}(r_{o2}||r_{o4})g_{m6}}{C_L}$$

**We want  $w_{p1} > w_0$  for good phase margin with unity gain feedback**
 
# Key Issue for Achieving Adequate Phase Margin




$$w_0 \approx \frac{g_{m1}(r_{o2}||r_{o4})g_{m6}}{C_L}$$

- To achieve  $w_{p1} > w_0$

$$w_{p1} = \frac{1}{(r_{o2}||r_{o4})C_{gs6}} > w_0 \Rightarrow C_L > g_{m1}g_{m6}(r_{o2}||r_{o4})^2 C_{gs6}$$

- We need a very large value of  $C_L$  relative to  $C_{gs6}$ 
  - This will generally be impractical!
 
# Pole Splitting Using a Compensation Capacitor



- Consider placing capacitor  $C_c$  across the second stage
  - Load capacitance seen by stage 1 becomes roughly


$$C_M = (1 + g_{m6}(r_{o6} || r_{o7}))C_c \approx g_{m6}(r_{o6} || r_{o7})C_c$$

- This large Miller capacitance now causes  $\omega_{p1}$  to become dramatically lower such that it forms the dominant pole

$$\omega_{p1} \approx \frac{1}{(r_{o2} || r_{o4})C_M} \approx \frac{1}{(r_{o2} || r_{o4})g_{m6}(r_{o6} || r_{o7})C_c}$$

- We will see that  $\omega_{p2}$  actually increases in frequency!
 
## Pole Splitting Using a Compensation Capacitor (Part 2)




- Assuming  $\omega_{p1}$  forms the dominant pole, we can approximate  $C_c$  as a short when calculating  $\omega_{p2}$

$$R_{th\_CL} \approx \frac{1}{g_{m6}}$$

$$\Rightarrow \omega_{p2} \approx \frac{1}{(1/g_{m6})(C_{gs6} + C_L)} = \frac{g_{m6}}{C_{gs6} + C_L}$$


- Note: we must have  $C_c \gg C_{gs6}$  for this to be accurate
- The inclusion of capacitor  $C_c$  has led to  $\omega_{p2}$  increasing in frequency
 
## Impact of Pole Splitting using Compensation Cap



- Pole splitting allows the dominant pole frequency to be dramatically decreased and the main parasitic pole to be dramatically increased**
  - We can achieve higher unity gain frequency with improved phase margin and with reasonable area**
 
# Unity Gain Frequency with Compensation Cap




$$H(s) = \frac{K}{1 + s/w_{p1}} = \frac{g_{m1}(r_{o2}\parallel r_{o4})g_{m6}(r_{o6}\parallel r_{o7})}{1 + s(r_{o2}\parallel r_{o4})g_{m6}(r_{o6}\parallel r_{o7})C_c}$$

- At frequencies  $\gg w_{p1}$

$$H(s) \approx \frac{g_{m1}(r_{o2}\parallel r_{o4})g_{m6}(r_{o6}\parallel r_{o7})}{s(r_{o2}\parallel r_{o4})g_{m6}(r_{o6}\parallel r_{o7})C_c} \Rightarrow w_0 \approx \frac{g_{m1}}{C_c}$$

**We want  $w_{p2} > w_0$  for good phase margin with unity gain feedback**
 
# Key Constraints for Achieving Adequate Phase Margin




$$w_o \approx \frac{g_{m1}}{C_c}$$

- To achieve  $w_{p2} > w_o$

$$w_{p2} = \frac{g_{m6}}{C_{gs6} + C_L} > w_o \Rightarrow C_c > \frac{g_{m1}}{g_{m6}}(C_{gs6} + C_L)$$

- Note: we must have  $C_c \gg C_{gs6}$  for this to be accurate
 
## More Accurate Calculations Related to Phase Margin




$$w_0 \approx \frac{g_{m1}}{C_c}$$

- To achieve  $w_{p2} > w_0$

$$w_{p2} > w_0 \Rightarrow C_c > \frac{g_{m1}}{g_{m6}} \left( \frac{C_{gs6}C_L}{C_c} + C_{gs6} + C_L \right)$$
 
# A More Accurate Transfer Function Model



$$H(s) = \frac{v_{out}(s)}{v_{id}(s)} = \frac{K(1 + s/w_z)}{(1 + s/w_{p1})(1 + s/w_{p2})}$$

$$K = g_{m1}(r_{o2} || r_{o4})g_{m6}(r_{o6} || r_{o7})$$

$$w_{p1} = \frac{1}{(r_{o2} || r_{o4})g_{m6}(r_{o6} || r_{o7})C_c}$$

$$w_{p2} = \frac{g_{m6}C_c}{C_{gs6}C_L + C_c(C_{gs6} + C_L)}$$

$$w_z = -\left(\frac{g_{m6}}{C_c}\right)$$


← **Right half plane (RHP) zero causes potential stability issues**

## Plotting the Magnitude of a RHP Zero

- Plot the magnitude response of right half plane  $w_z$

$$20 \log |A_z(w)| = 20 \log |1 - jw/w_z|$$

- For  $w \ll /w_z/$ :  $20 \log |A_z(w)| \approx 20 \log |1| = 0$
- For  $w \gg /w_z/$ :  $20 \log |A_z(w)| \approx 20 \log |w/w_z|$

 


**Magnitude response is the same as for left half plane zero**

## Plotting the Phase of a RHP Zero

- Plot the phase response of right half plane  $w_z$


$$\angle A_z(w) = \angle(1 - jw/w_z) = \arctan(-w/w_z)$$

- For  $w \ll |w_z|$ :  $\angle A_z(w) \approx \arctan(0) = 0^\circ$
- For  $w = |w_z|$ :  $\angle A_z(w) \approx \arctan(-1) = -45^\circ$
- For  $w \gg |w_z|$ :  $\angle A_z(w) \approx \arctan(-\infty) = -90^\circ$

 

Phase response is *negative* rather than positive (similar to pole)
 
## Phase Margin Degradation Due to RHP Zero




- Since the RHP zero adds negative phase (similar to pole), it reduces phase margin

- We want:

$$|w_z| \gg w_o \Rightarrow g_{m6} \gg g_{m1}$$

- This is not a desirable constraint

# Adding a Compensation Resistor

 

$$H(s) = \frac{v_{out}(s)}{v_{id}(s)} = \frac{K(1 + s/w_z)}{(1 + s/w_{p1})(1 + s/w_{p2})}$$

$$K = g_{m1}(r_{o2} || r_{o4})g_{m6}(r_{o6} || r_{o7})$$

$$w_{p1} = \frac{1}{(r_{o2} || r_{o4})g_{m6}(r_{o6} || r_{o7})C_c}$$


$$w_{p2} = \frac{g_{m6}C_c}{C_{gs6}C_L + C_c(C_{gs6} + C_L)}$$

$$w_z = - \left( \frac{g_{m6}}{C_c} \right) \frac{1}{1 - g_{m6}R_c}$$

- RHP zero effectively removed if  $R_c = 1/g_{m6}$
- Improved phase margin possible with  $R_c > 1/g_{m6}$ 
  - See Johns&Martin, pp. 242-244


 
# Calculations for Triode Compensation Resistor



- Triode resistance calculated as

$$R_c = \frac{1}{\mu_n C_{ox} (W_9/L_9) (V_{gs9} - V_{TH})}$$

$$= \frac{1}{\mu_n C_{ox} (W_9/L_9) (V_{dd} - V_{gs6} - V_{TH})}$$

- Assuming square law,  $1/g_{m6}$  is calculated as

$$\frac{1}{g_{m6}} = \frac{1}{\mu_n C_{ox} (W_6/L_6) (V_{gs6} - V_{TH})}$$

Depending on  $V_{dd}$ ,  $R_c$  can track  $1/g_{m6}$  across process/temp

# Summary

---

- **Basic two-stage CMOS opamp is a workhorse for many moderate performance analog applications**
  - Relatively simple structure with reasonable performance
- **Key issue: two-stages lead to two poles that are relatively close to each other**
  - This leads to very poor phase margin unless very large  $C_L$  is used
- **Inclusion of a compensation capacitor across the second stage leads to pole splitting such that stable performance can be achieved with reasonable area**
  - A compensation resistor is also desirable to help eliminate the impact of a RHP zero that occurs due to compensation

**We will use the basic two stage CMOS opamp structure to explore various opamp specifications in the next lecture**