
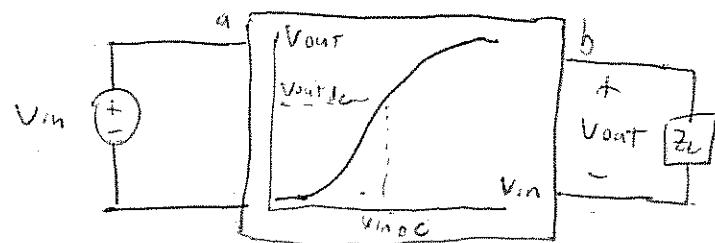


## LECTURE 2:


SLOPE 9) CREATE TWO PORT MODEL:

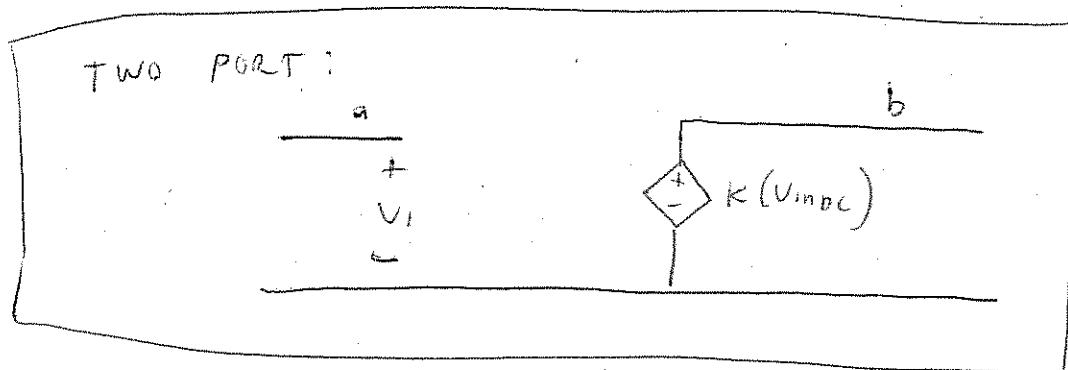

DEFINE  $k(V_{inDC})$  AS THE SLOPE


$$\frac{V_{out}}{V_{in}} \Big|_{V_{in} = V_{inDC}}$$


SLOPE 10)

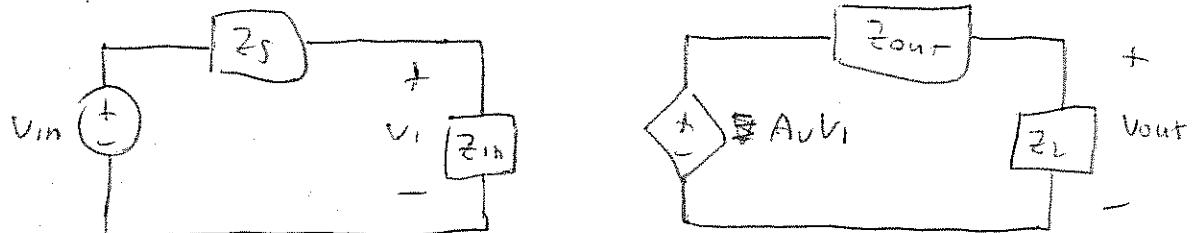


$$V_{out} = \frac{Z_L}{Z_{out} + Z_L} A_v V_i = \frac{Z_L}{Z_{out} + Z_L} \left( \frac{Z_{in}}{Z_S + Z_{in}} \right) V_{in} = V_{out}$$

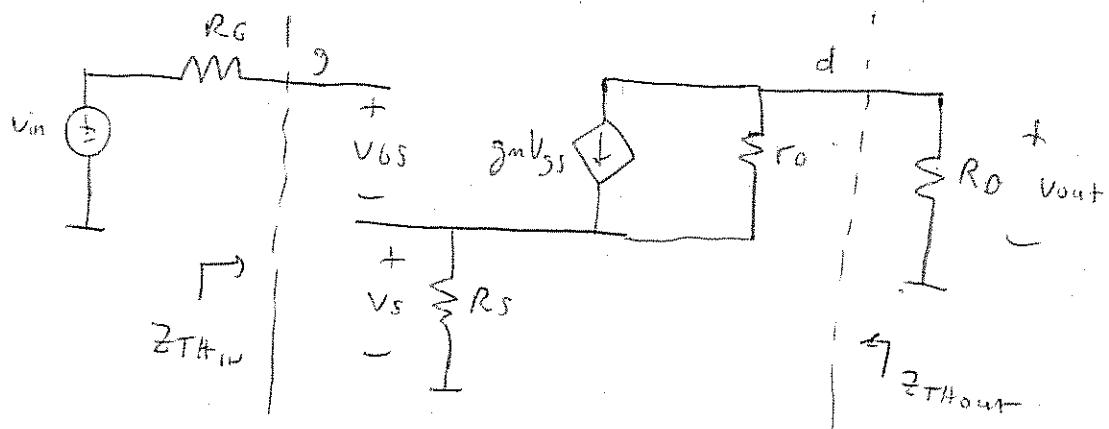SLIDE 11) WITH  $r_o = \infty$ ,  $g_{mb} = 0$  WE HAVE:



$Z_{TH_{IN}} = \infty$  SINCE NO CURRENT FLOW INTO TERMINAL g

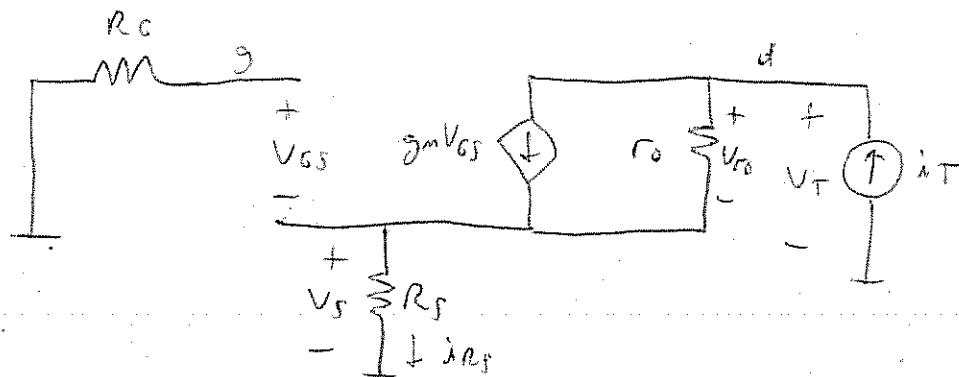$Z_{TH_{out}}$   $\Rightarrow$  MUST CALCULATE  $\rightarrow$  EASIER TO USE TEST CURRENT



$$i_{RS} = i_T \text{ BY KCL} \Rightarrow V_S = i_T R_S$$

$$\Rightarrow V_{DS} = 0 - i_T R_S = -i_T R_S$$

$$\Rightarrow g_m V_{DS} = -g_m i_T R_S$$

$$\Rightarrow V_{R_o} = (\cancel{g_m i_T R_S}) r_o / (g_m i_T R_S + i_T) r_o$$


$$\Rightarrow V_T = V_S + V_{R_o} = i_T R_S + g_m i_T R_S r_o + i_T r_o \\ = i_T (R_S + \cancel{g_m R_S r_o}) + r_o$$

$$\Rightarrow \boxed{Z_{TH_{out}} = \frac{V_T}{i_T} = R_S (1 + g_m r_o) + r_o}$$

TO BE CLEAR:

$$Z_{TH_{out}} = R_S (1 + g_m r_o) + r_o$$

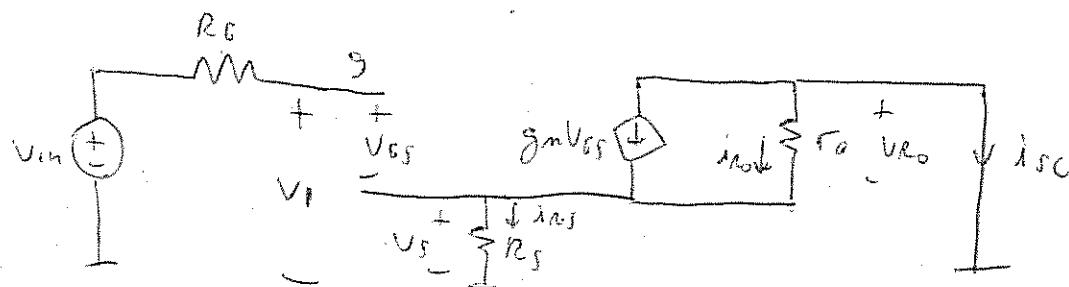SLIDE 11) DETERMINE  $G_m$  BY LOOKING AT SHORT CIRCUIT CURRENT:



$$\text{NOTE: } i_{R_S} = -i_{SC} \Rightarrow V_S = -i_{SC} R_S$$

$$\Rightarrow V_{GS} = V_1 - V_S = V_1 + R_S i_{SC}$$

$$\text{NOTE: } V_{RO} + V_S = 0 \Rightarrow V_{RO} = -V_S = i_{SC} R_S$$

$$\Rightarrow i_{R_o} = \frac{V_{RO}}{R_o} = i_{SC} \frac{R_S}{R_o}$$

$$\text{FINALLY: } i_{SC} = -i_{R_o} - g_m V_{GS}$$

$$= -i_{SC} \frac{R_S}{R_o} - g_m (V_1 + R_S i_{SC})$$

$$\Rightarrow i_{SC} \left( 1 + \frac{R_S}{R_o} + g_m R_S \right) = -g_m V_1$$

$$\Rightarrow i_{SC} = \frac{-g_m}{1 + g_m R_S \left( 1 + \frac{1}{g_m R_o} \right)} V_1$$


$$\text{NOTE THAT } G_m = -i_{SC}$$

$$\Rightarrow G_m = \frac{g_m}{1 + g_m R_S \left( 1 + \frac{1}{g_m R_o} \right)}$$

## LECTURE 2:

4

SLIDE 13)

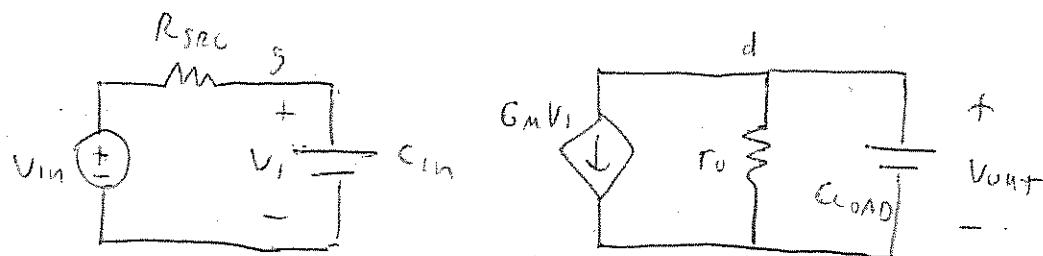

$$V_{out}(s) = -G_m V_1(s) \frac{1}{sC_{load}} \parallel r_o$$

$$= -G_m \frac{\frac{1}{sC_{load}} r_o}{\frac{1}{sC_{load}} + r_o} V_1(s)$$

$$= -G_m \frac{r_o}{1 + sC_{load}r_o} V_1(s)$$

AND  $V_1(s) = V_{in}(s) \frac{\frac{1}{sC_{in}}}{R_{src} + \frac{1}{sC_{in}}} = \frac{1}{1 + sR_{src}C_{in}} V_{in}(s)$

$$\Rightarrow V_{out}(s) = -G_m \frac{r_o}{1 + sC_{load}r_o} \left( \frac{1}{1 + sR_{src}C_{in}} \right) V_{in}(s)$$

$$\Rightarrow \boxed{\frac{V_{out}(s)}{V_{in}(s)} = -G_m \frac{r_o}{1 + sC_{load}r_o} \left( \frac{1}{1 + sR_{src}C_{in}} \right)}$$

~~NO ZEROS~~

NO ZEROS

POLES AT  $\frac{1}{CLoadr_o}$  AND  $\frac{1}{CinRsrc}$

SLIDE 14)

$$\boxed{\frac{V_{out}(f)}{V_{in}(f)} = \frac{-G_m r_o}{1 + j2\pi f C_{load}r_o} \left( \frac{1}{1 + j2\pi f C_{in} R_{src}} \right)}$$