

General Thevenin Resistance View with C-B Feedback

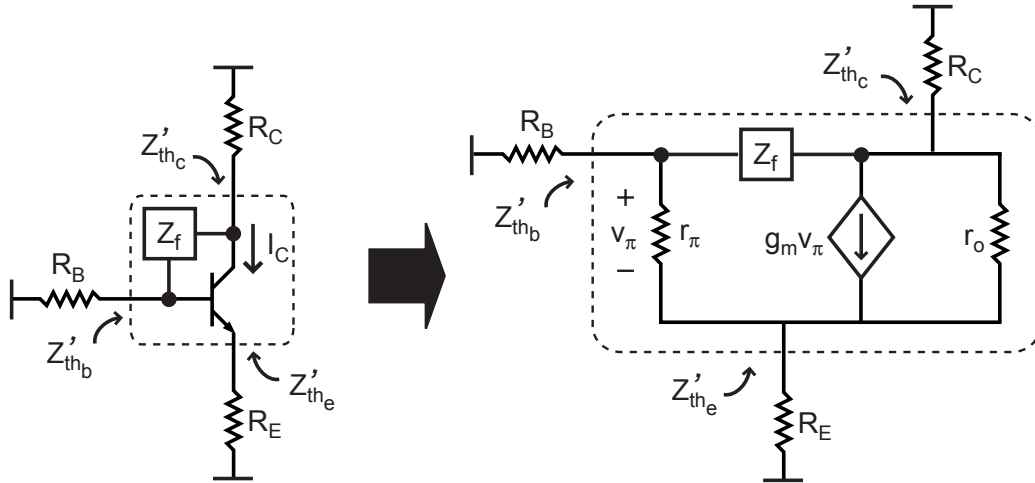


Figure 1 Definition of Thevenin Resistances.

Thevenin resistance at collector:

$$Z'_{thc} \approx R_{thc} \parallel \frac{Z_f}{(Z_f \parallel R_{thb} \parallel R_b)(G_m + 1/(R_{thb} \parallel R_b))}$$

Thevenin resistance at base:

$$Z'_{thb} \approx R_{thb} \parallel \frac{Z_f}{(Z_f \parallel R_{thc} \parallel R_c)(G_m + 1/(R_{thc} \parallel R_c))}$$

Thevenin resistance at emitter:

$$Z'_{the} \approx \frac{1}{g_m} + \frac{1}{1 + \beta_o} (R_b \parallel (R_c + Z_f)) + \frac{1}{1 + R_f/R_c} (R_b \parallel (R_c + Z_f))$$

Where:

$$R_{thc} \approx (1 + g_m(r_\pi \parallel R_E))r_o \quad \text{for } R_B \ll r_\pi, R_E$$

$$R_{thb} \approx r_\pi + (\beta_o + 1)R_E \quad \text{for } R_C \ll r_o, R_E \ll r_o$$

$$G_m = \frac{1}{1/g_m + R_E}$$