

High Speed Communication Circuits and Systems
Lecture 10
Mixers


Michael H. Perrott

March 5, 2004

Copyright © 2004 by Michael H. Perrott

All rights reserved.


Mixer Design for Wireless Systems

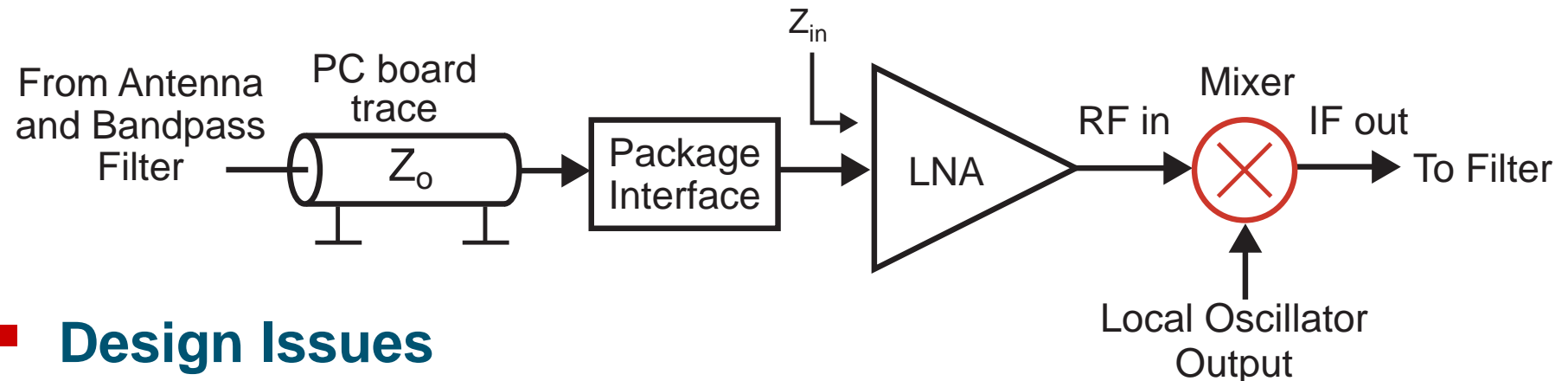

■ Design Issues


- **Noise Figure** – impacts receiver sensitivity
- **Linearity (IIP3)** – impacts receiver blocking performance
- **Conversion gain** – lowers noise impact of following stages
- **Power match** – want max voltage gain rather than power match for integrated designs
- **Power** – want low power dissipation
- **Isolation** – want to minimize interaction between the RF, IF, and LO ports
- **Sensitivity to process/temp variations** – need to make it manufacturable in high volume

Ideal Mixer Behavior

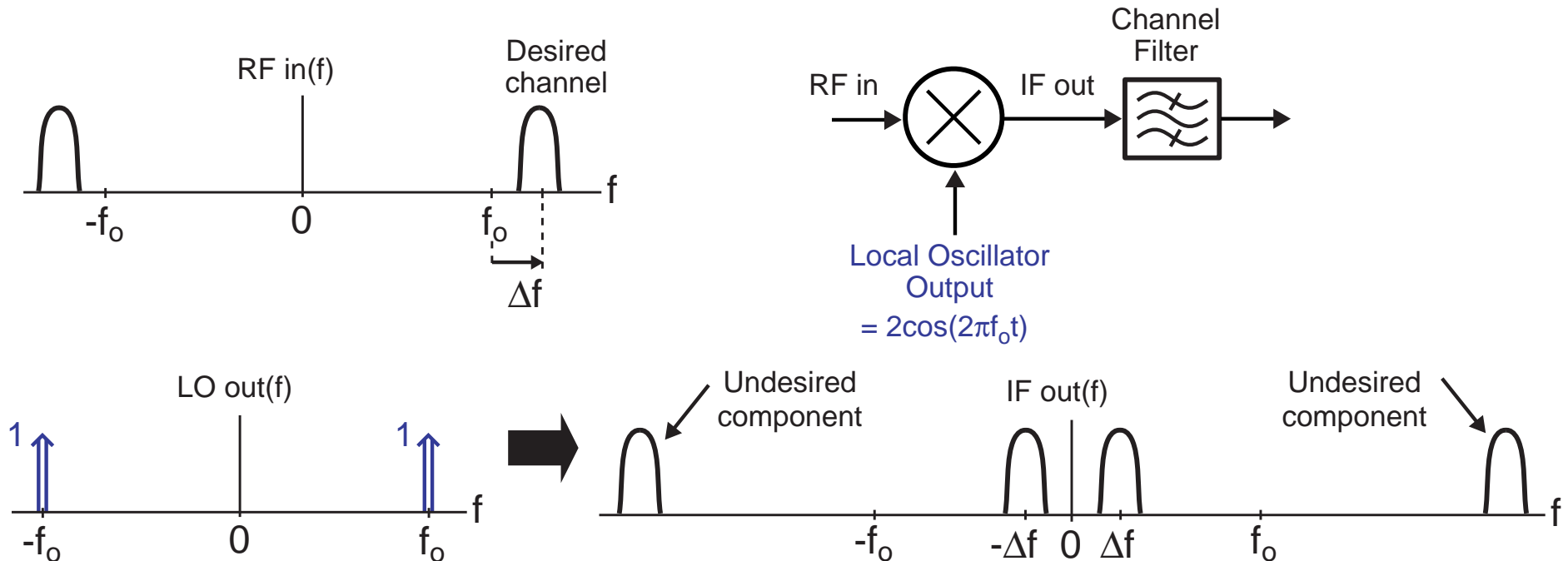


- **RF spectrum converted to a lower IF center frequency**
 - IF stands for intermediate frequency
 - If IF frequency is nonzero – heterodyne or low IF receiver
 - If IF frequency is zero – homodyne receiver
- **Use a filter at the IF output to remove undesired high frequency components**

The Issue of Aliasing

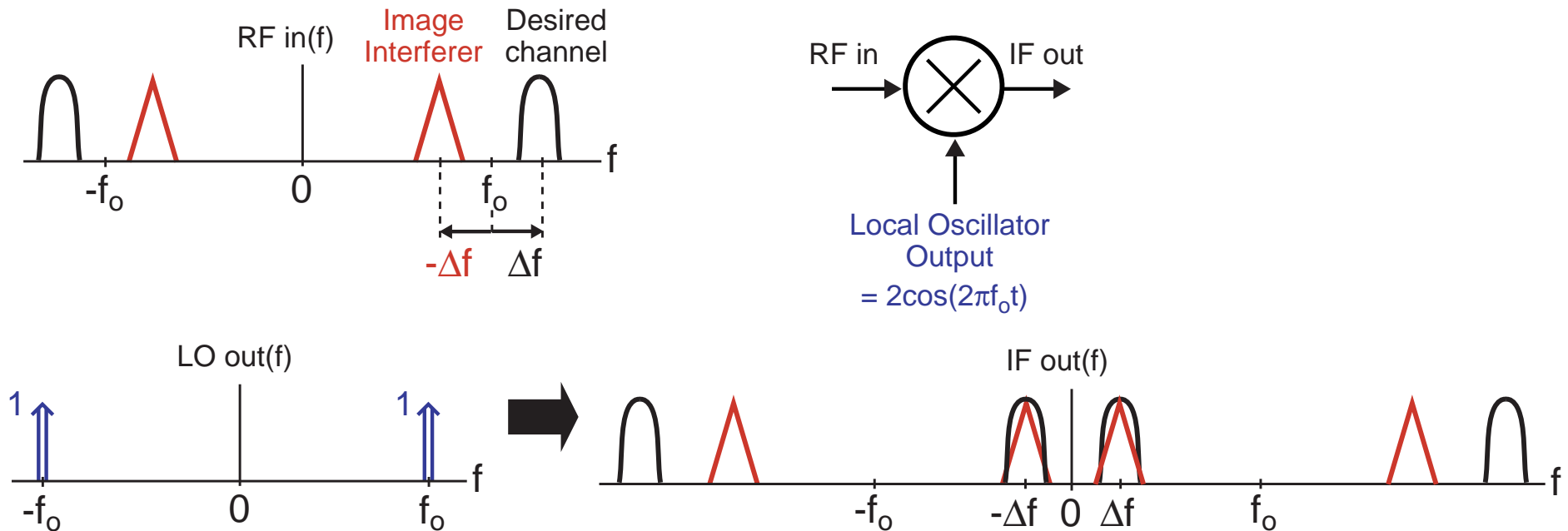


- **When the IF frequency is nonzero, there is an image band for a given desired channel band**
 - Frequency content in image band will combine with that of the desired channel at the IF output
 - The impact of the image interference cannot be removed through filtering at the IF output!

LO Feedthrough

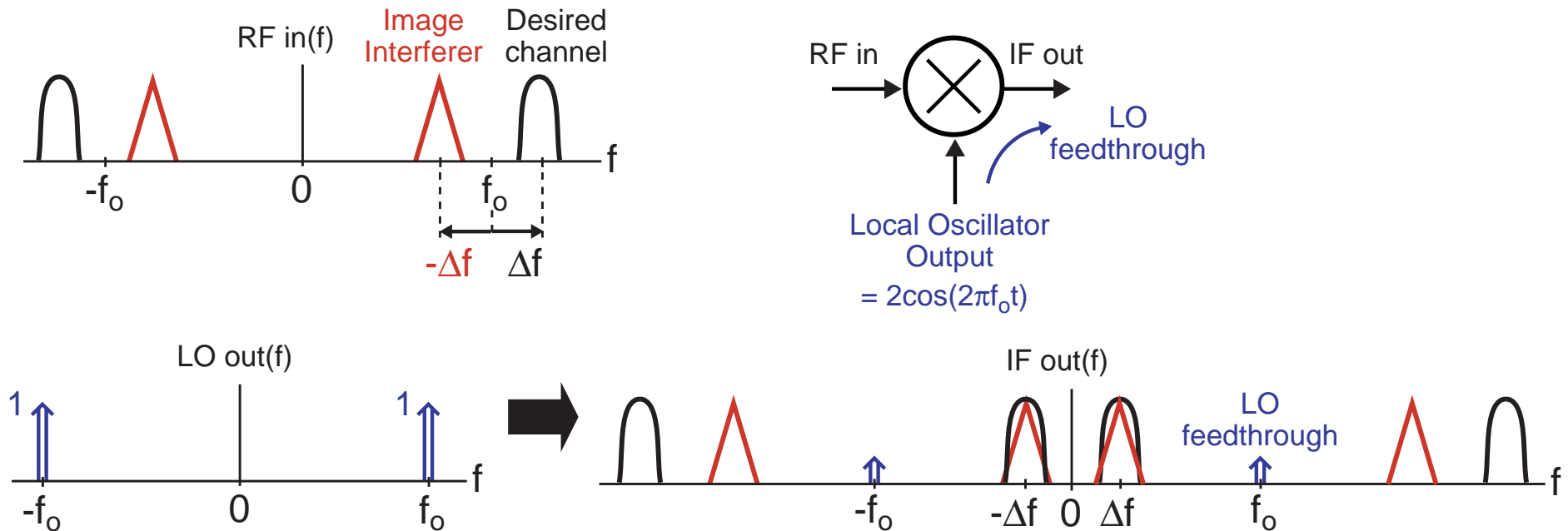


- **LO feedthrough will occur from the LO port to IF output port due to parasitic capacitance, power supply coupling, etc.**
 - **Often significant since LO output much higher than RF signal**
 - If large, can potentially desensitize the receiver due to the extra dynamic range consumed at the IF output
 - If small, can generally be removed by filter at IF output

Reverse LO Feedthrough

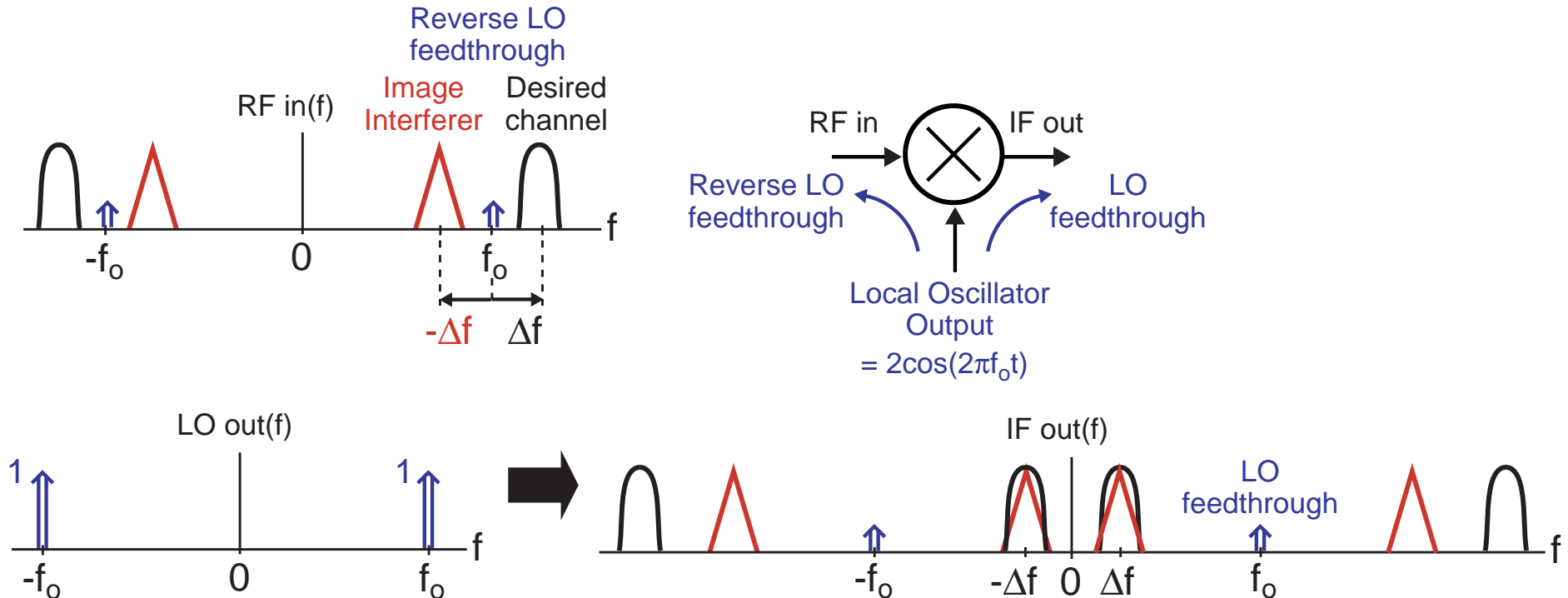


- **Reverse LO feedthrough will occur from the LO port to RF input port due to parasitic capacitance, etc.**
 - If large, and LNA doesn't provide adequate isolation, then LO energy can leak out of antenna and violate emission standards for radio
 - Must insure that isolate to antenna is adequate

Self-Mixing of Reverse LO Feedthrough

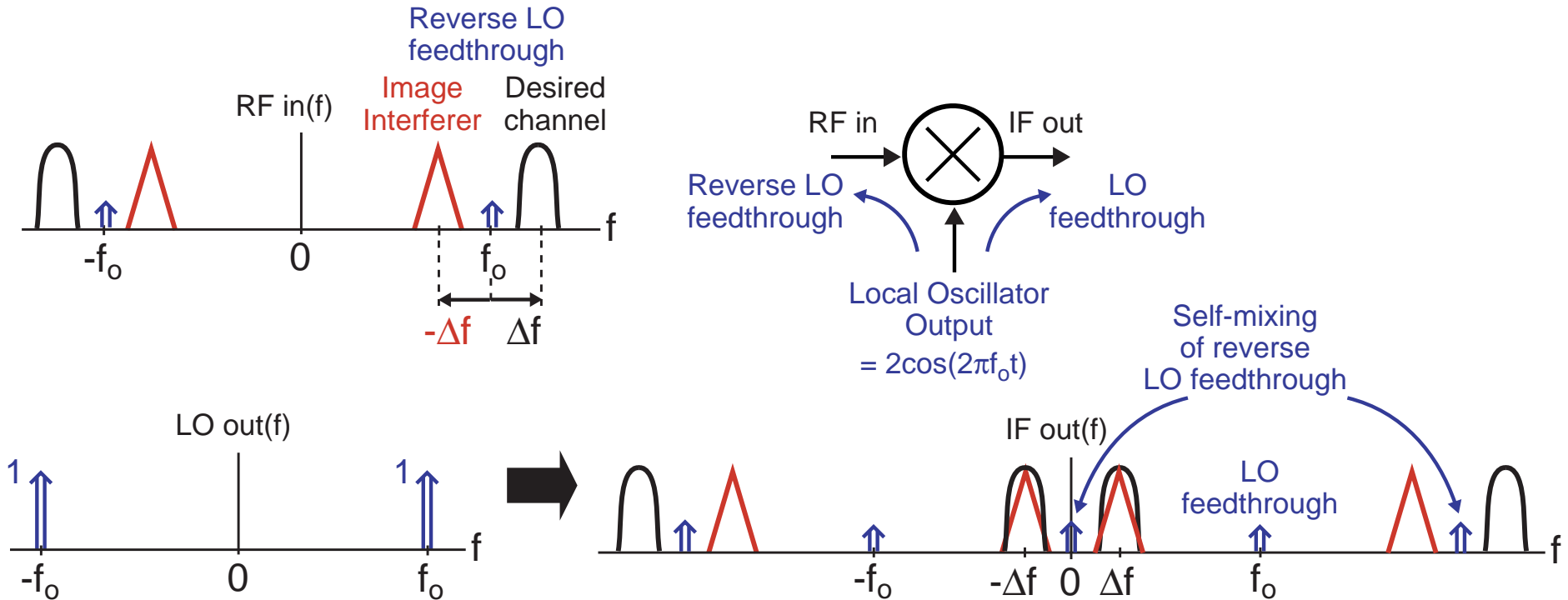


- **LO component in the RF input can pass back through the mixer and be modulated by the LO signal**
 - **DC and $2f_0$ component created at IF output**
 - **Of no consequence for a heterodyne system, but can cause problems for homodyne systems (i.e., zero IF)**

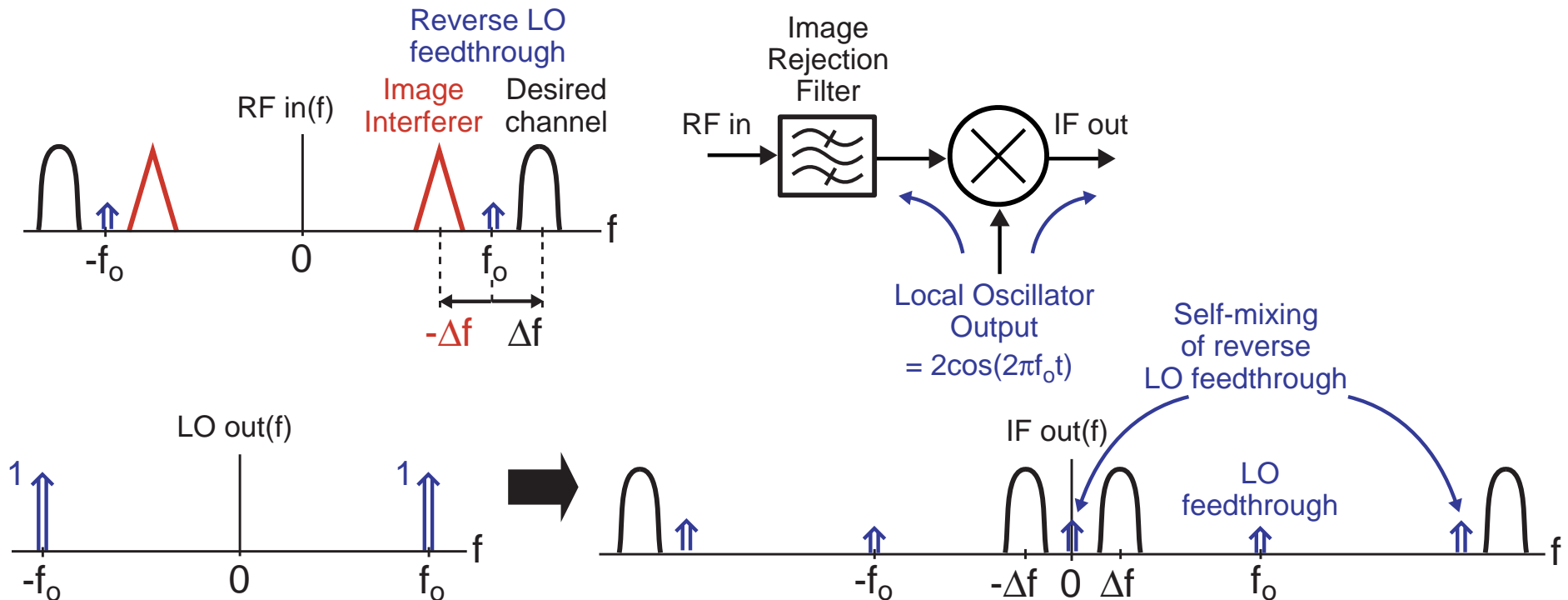Removal of Image Interference – Solution 1




- An image reject filter can be used *before* the mixer to prevent the image content from aliasing into the desired channel at the IF output
- Issue – must have a high IF frequency
 - Filter bandwidth must be large enough to pass all channels
 - Filter Q cannot be arbitrarily large (low IF requires high Q)

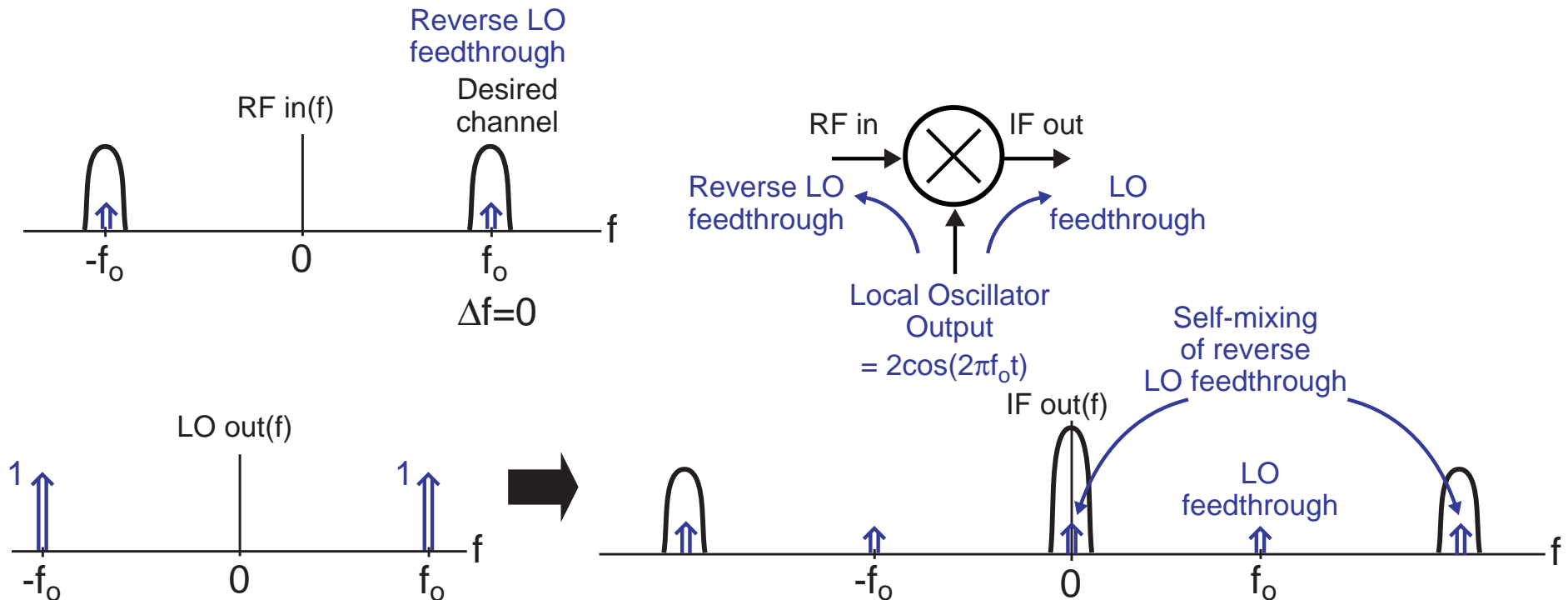Removal of Image Interference – Solution 2



- **Mix directly down to baseband (i.e., homodyne approach)**
 - With an IF frequency of zero, there is no image band
- **Issues – many!**
 - DC term of LO feedthrough can corrupt signal if time-varying
 - DC offsets can swamp out dynamic range at IF output
 - $1/f$ noise, back radiation through antenna

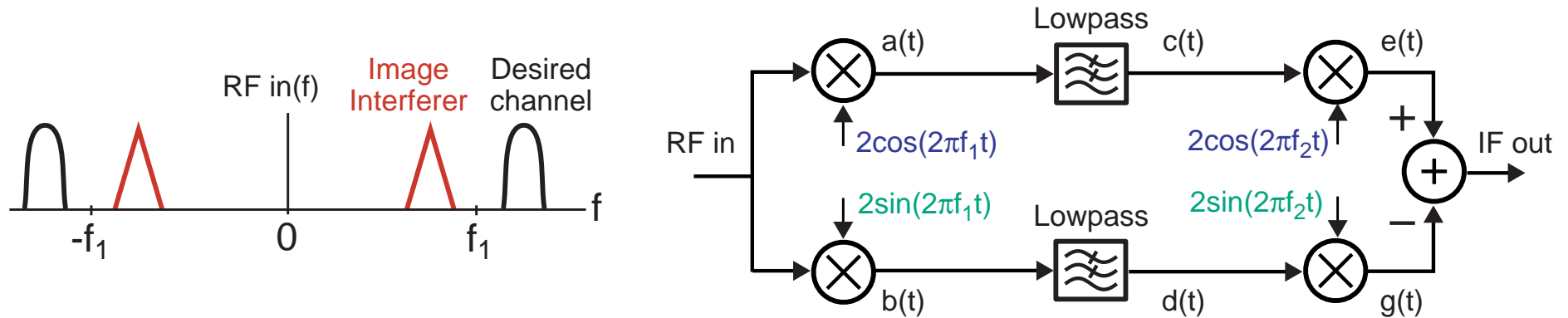Removal of Image Interference – Solution 3



- Rather than filtering out the image, we can cancel it out using an image rejection mixer



- Advantages

- Allows a low IF frequency to be used without requiring a high Q filter
- Very amenable to integration

- Disadvantage

- Level of image rejection is determined by mismatch in gain and phase of the top and bottom paths
- Practical architectures limited to 40-50 dB image rejection

Image Reject Mixer Principles – Step 1

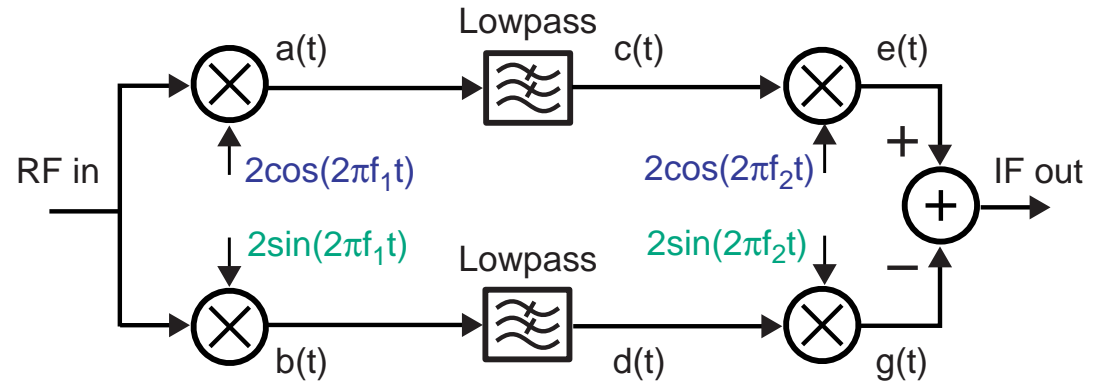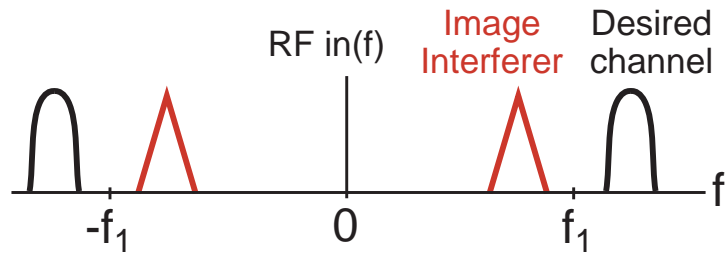

- **Note: we are assuming RF in(f) is purely real right now**

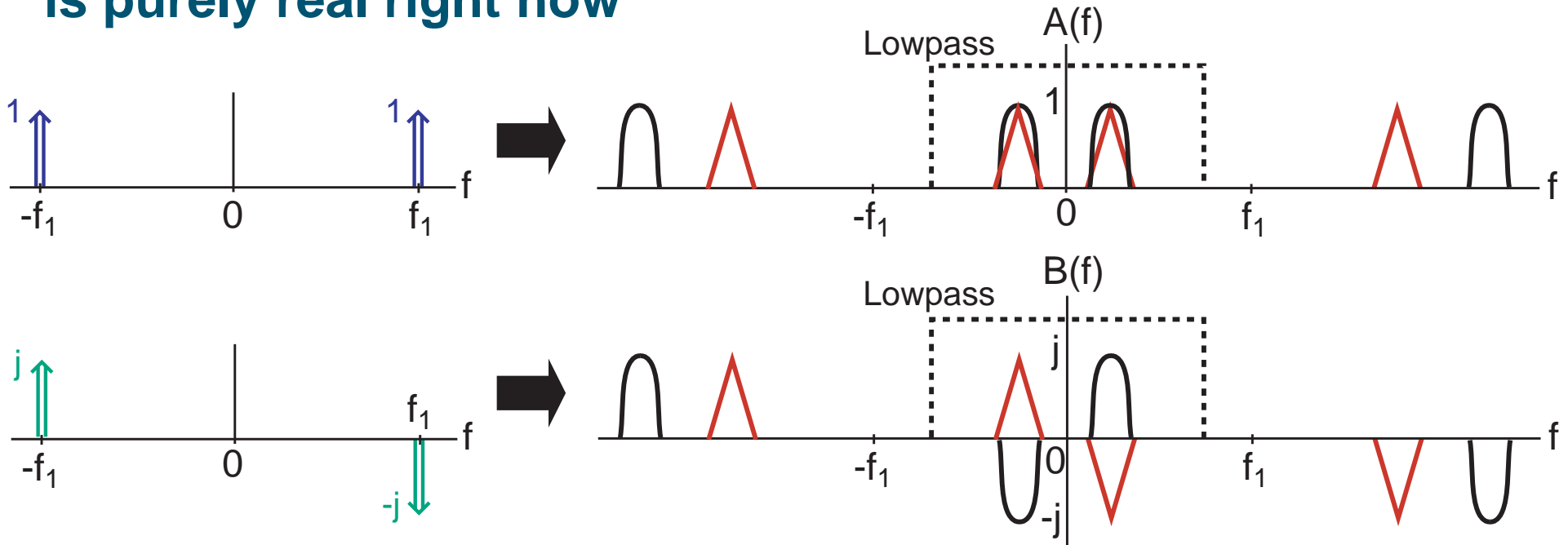


Image Reject Mixer Principles – Step 2

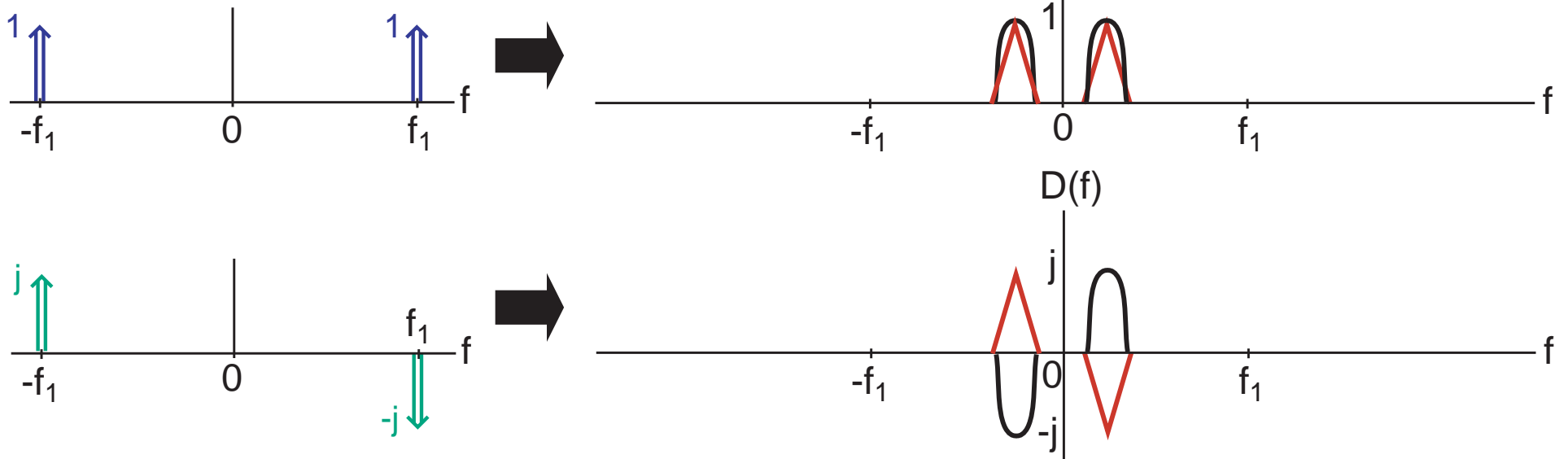
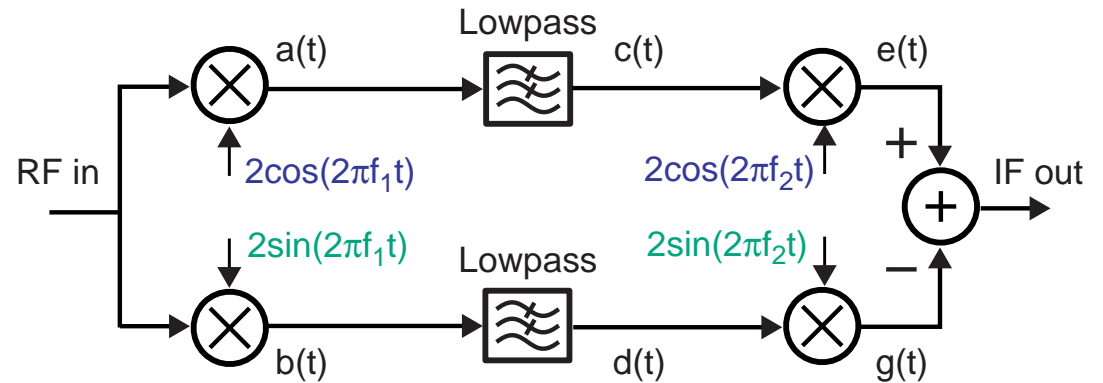
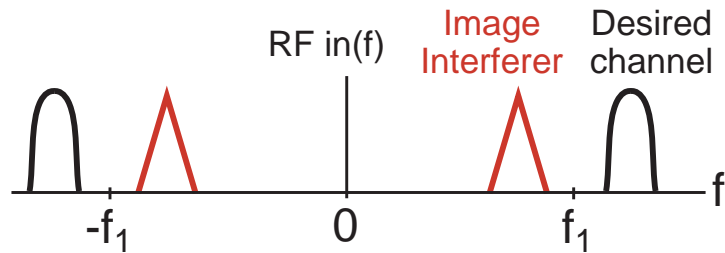


Image Reject Mixer Principles – Step 3

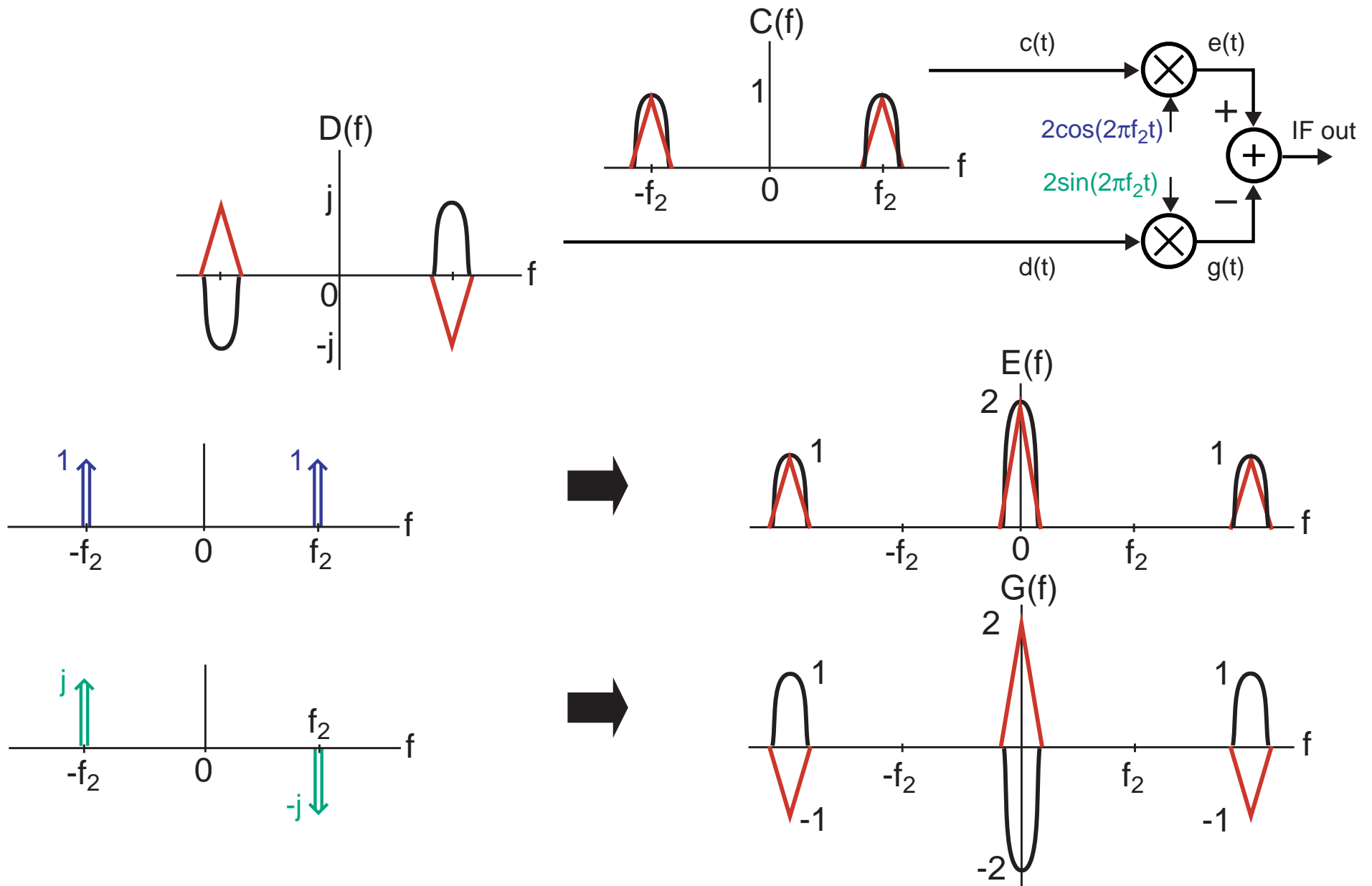


Image Reject Mixer Principles – Step 4



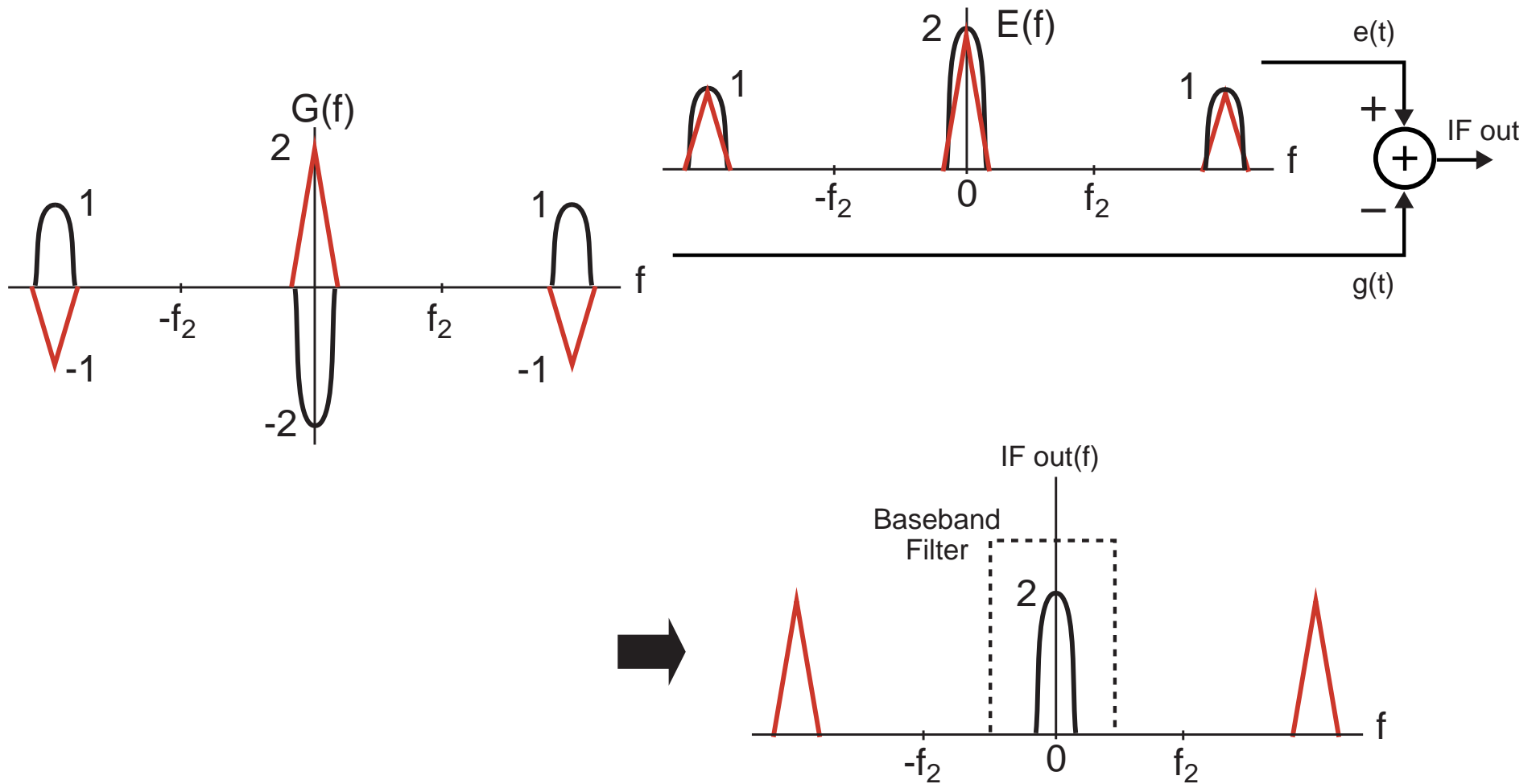


Image Reject Mixer Principles – Implementation Issues

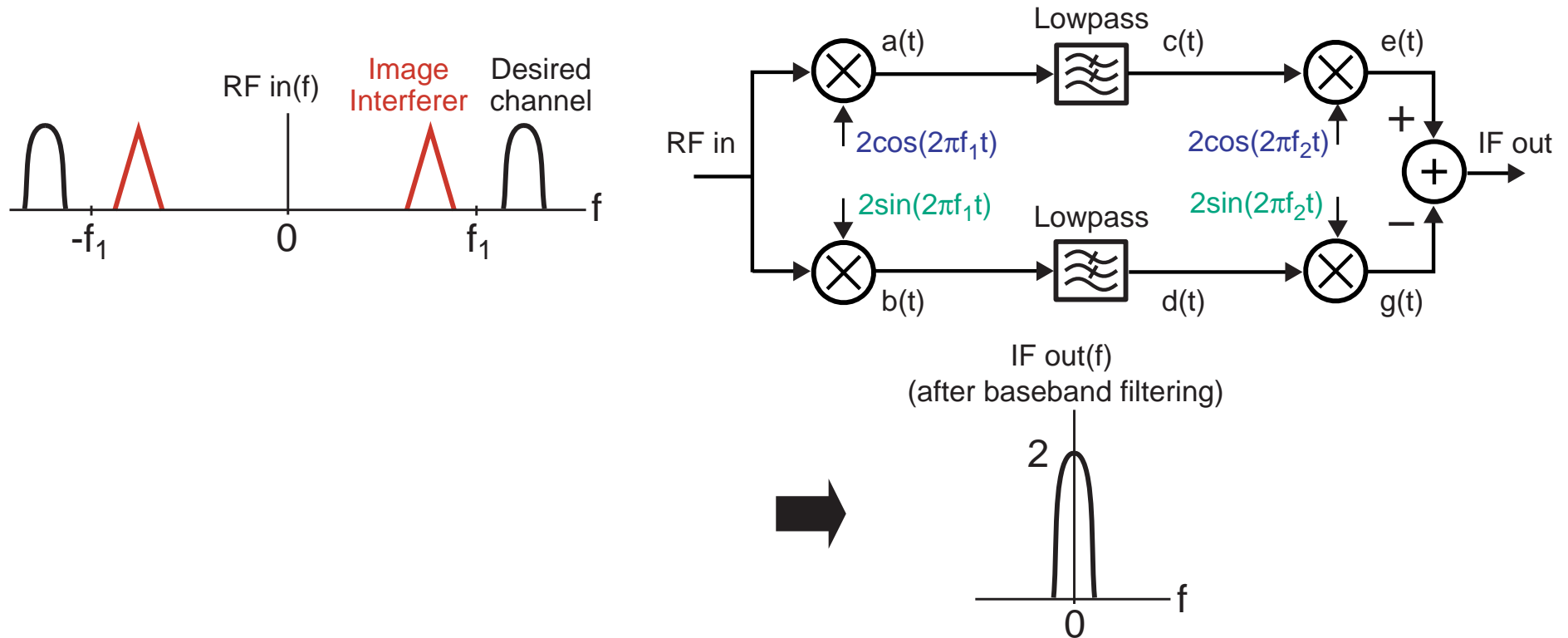


- For all analog architecture, going to zero IF introduces sensitivity to $1/f$ noise at IF output
 - Can fix this problem by digitizing $c(t)$ and $d(t)$, and then performing final mixing in the digital domain
- Can generate accurate quadrature sine wave signals by using a frequency divider

What if RF $in(f)$ is Purely Imaginary?

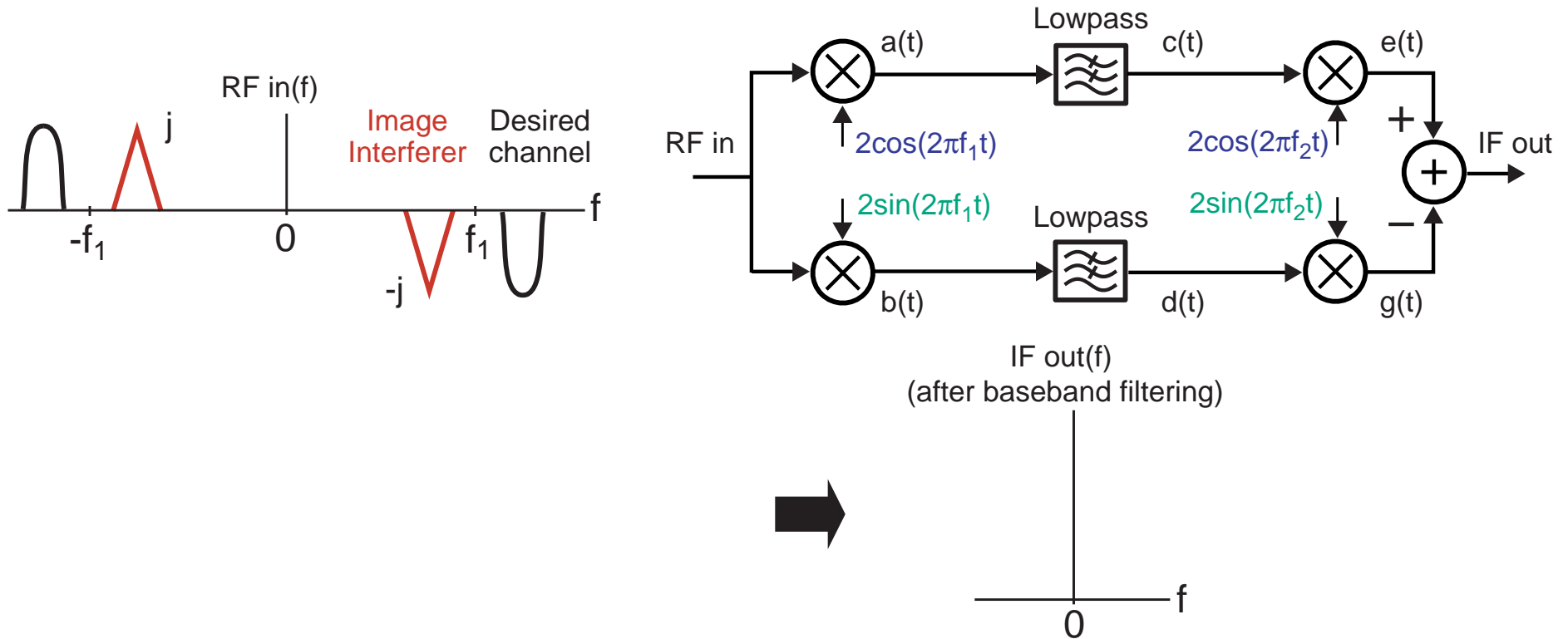


- **Both desired and image signals disappear!**
 - Architecture is sensitive to the phase of the RF input
- **Can we modify the architecture to fix this issue?**

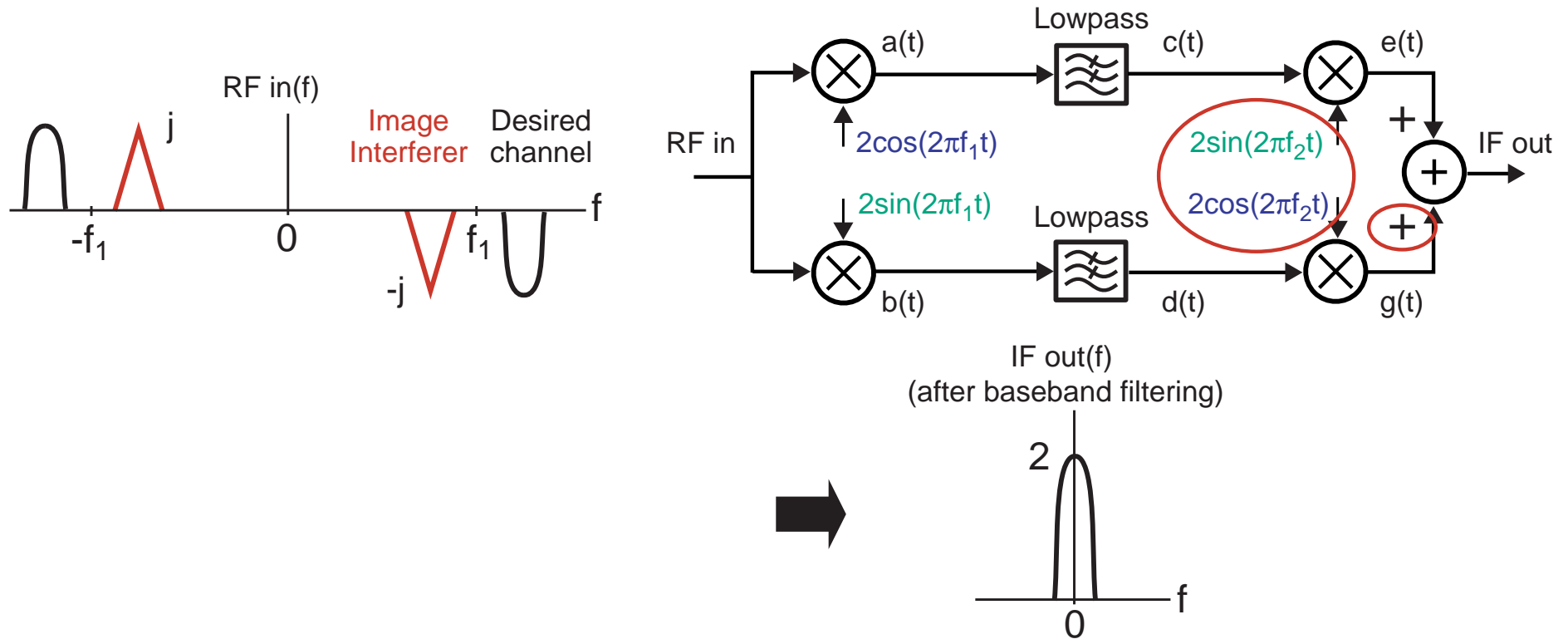Modification of Mixer Architecture for Imaginary RF in(f)




- **Desired channel now appears given two changes**
 - Sine and cosine demodulators are switched in second half of image rejection mixer
 - The two paths are now added rather than subtracted
- **Issue – architecture now zeros out desired channel when RF in(f) is purely real**

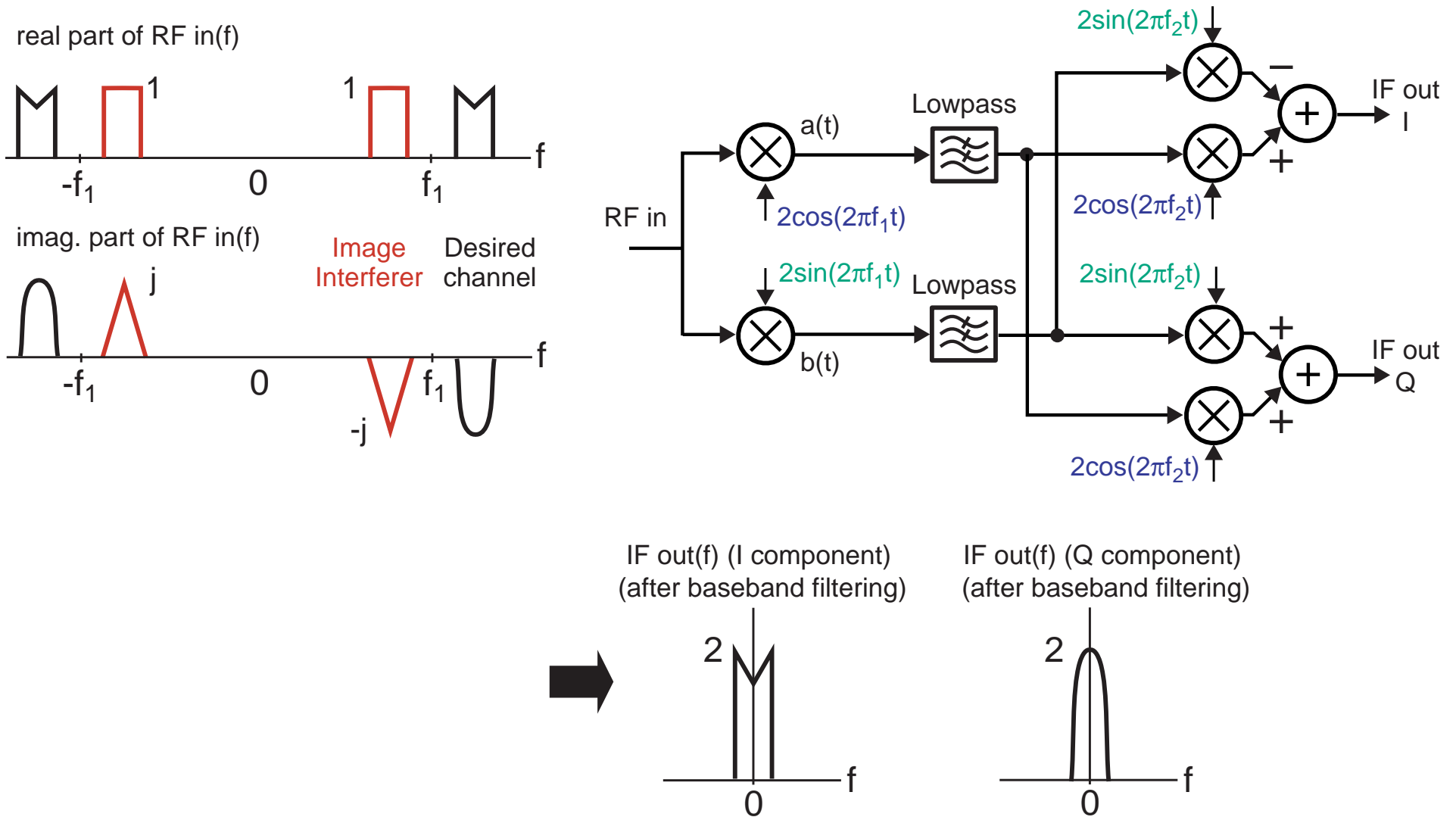Overall Mixer Architecture – Use I/Q Demodulation




- Both real and imag. parts of RF input now pass through

Mixer Single-Sideband (SSB) Noise Figure

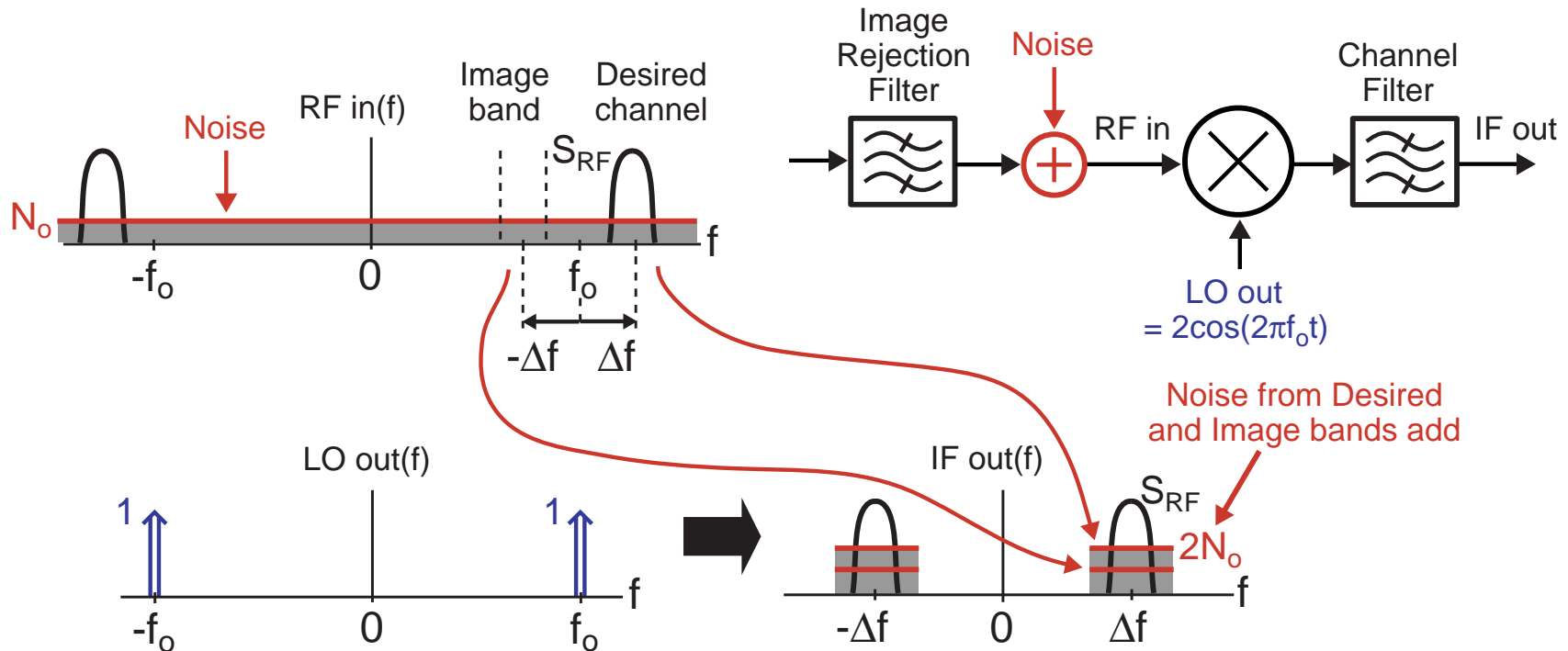


- **Issue – broadband noise from mixer or front end filter will be located in both image and desired bands**
 - Noise from both image and desired bands will combine in desired channel at IF output
 - Channel filter cannot remove this
 - **Mixers are inherently noisy!**

Mixer Double-Sideband (DSB) Noise Figure

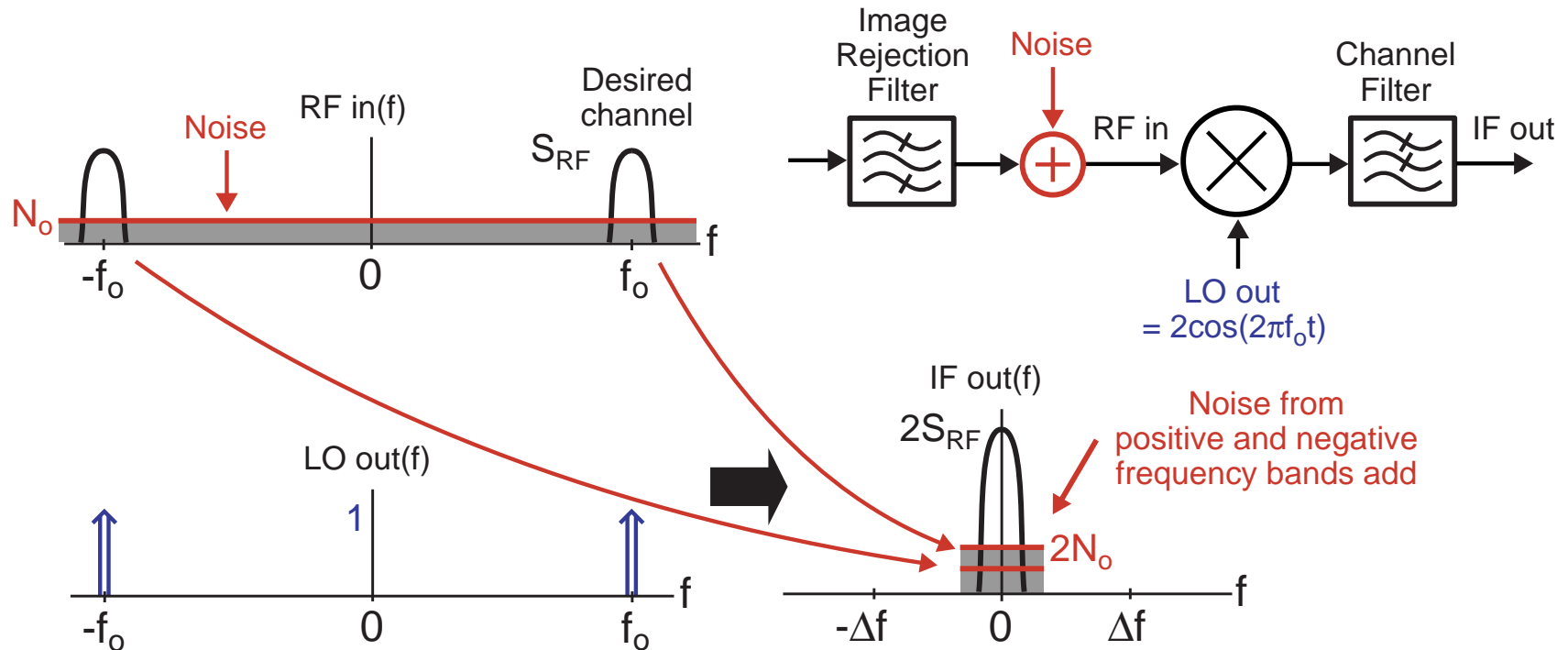

- For zero IF, there is no image band
 - Noise from positive and negative frequencies combine, but the signals do as well
- DSB noise figure is 3 dB lower than SSB noise figure
 - DSB noise figure often quoted since it sounds better
- For either case, Noise Figure computed through simulation

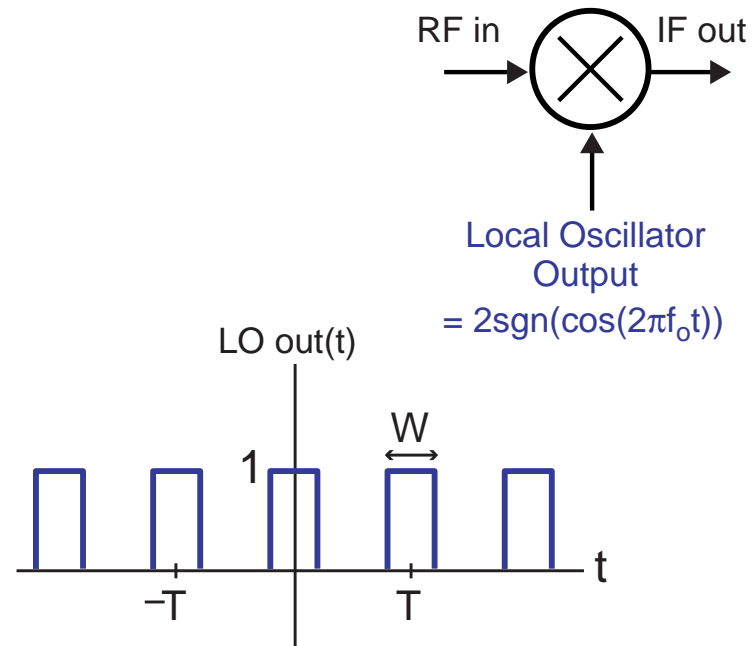
A Practical Issue – Square Wave LO Oscillator Signals




- **Square waves are easier to generate than sine waves**
 - How do they impact the mixing operation when used as the LO signal?
 - We will briefly review Fourier transforms (series) to understand this issue

Two Important Transform Pairs

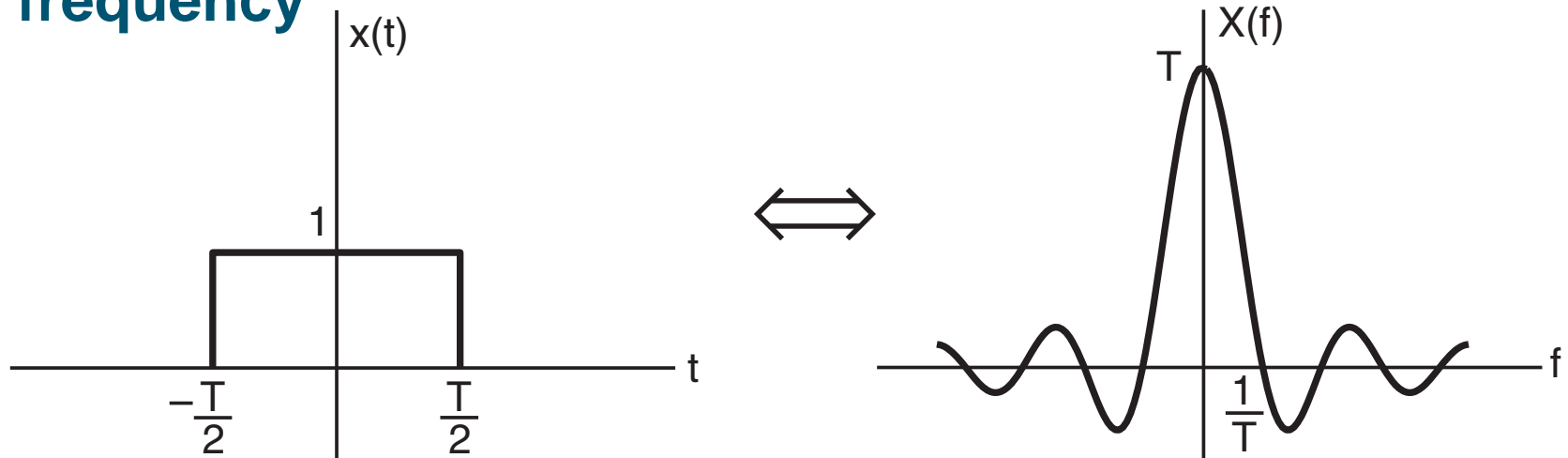- Transform of a rectangle pulse in time is a sinc function in frequency




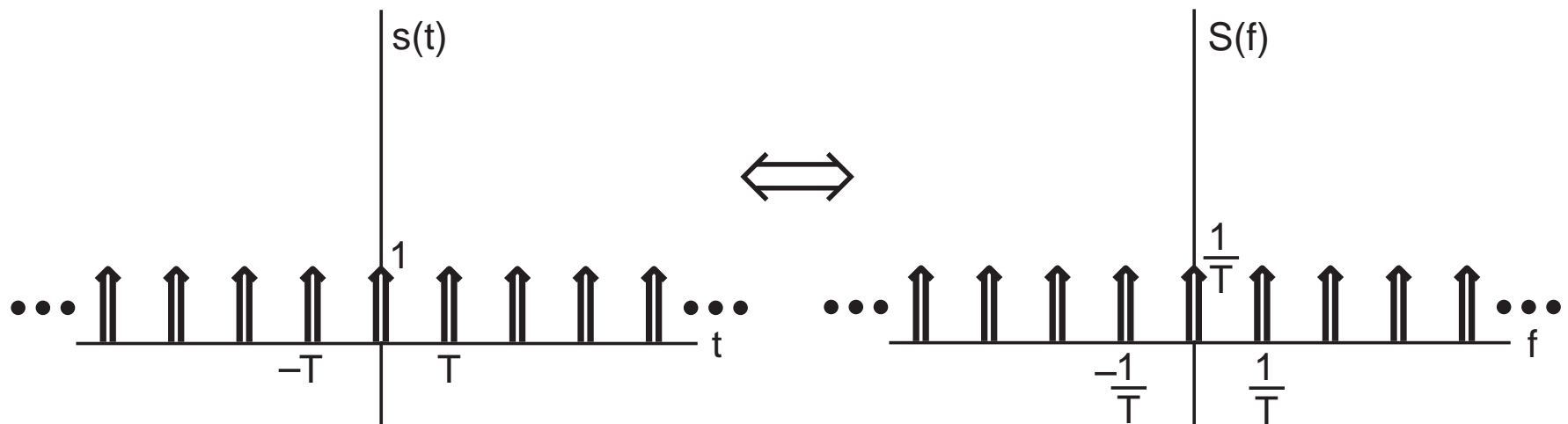- Transform of an impulse train in time is an impulse train in frequency




Decomposition of Square Wave to Simplify Analysis

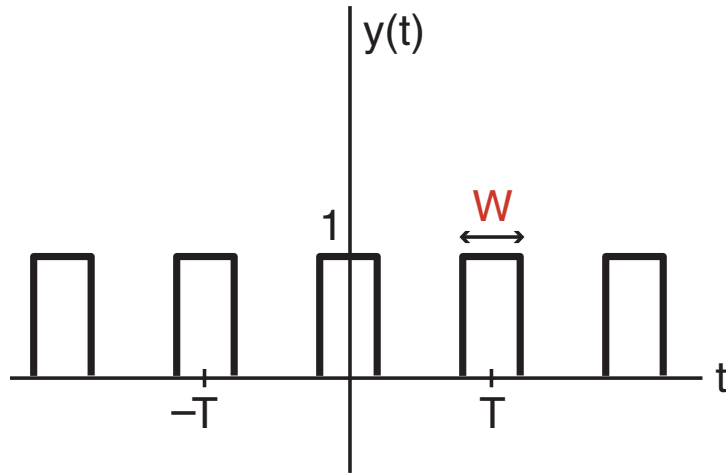
- Consider now a square wave with duty cycle W/T



- Decomposition in time

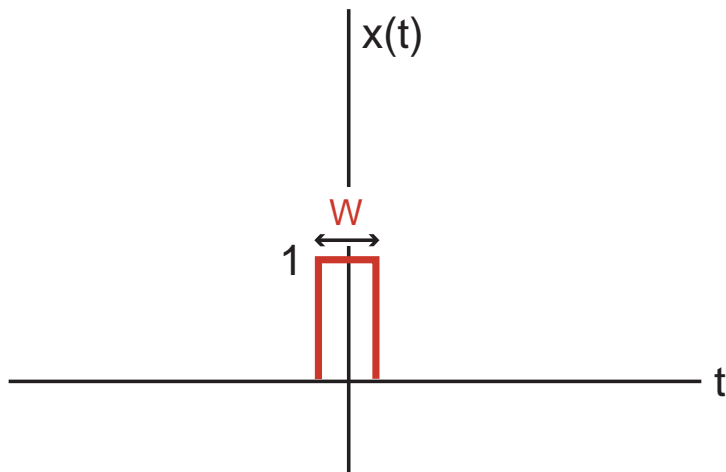


*

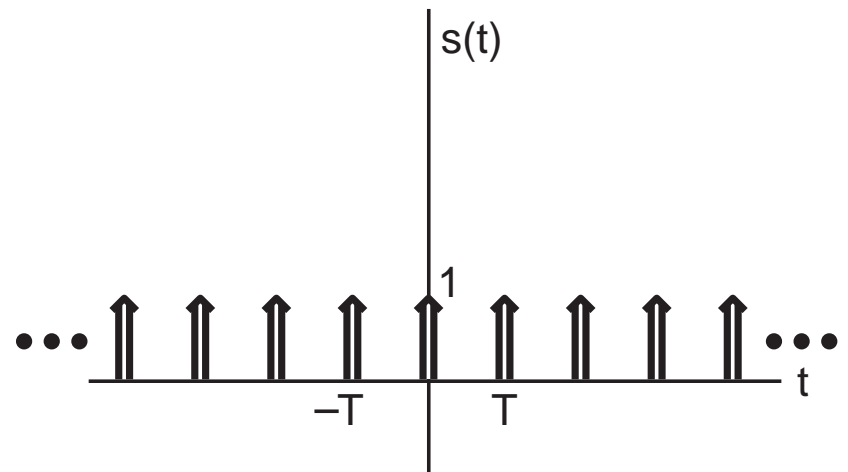


Associated Frequency Transforms

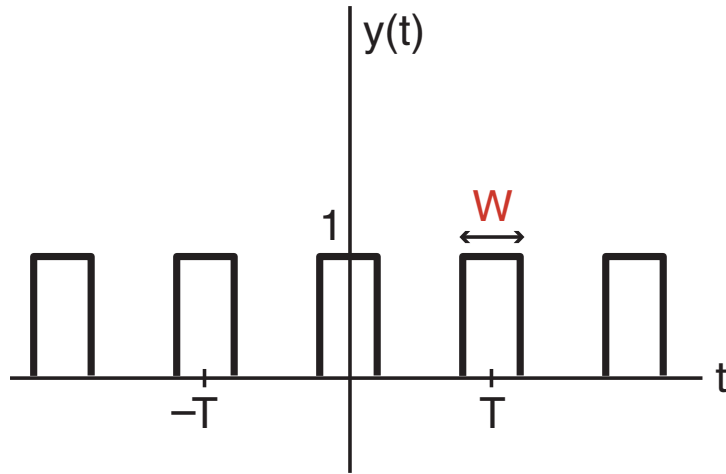- Consider now a square wave with duty cycle W/T




- Decomposition in frequency

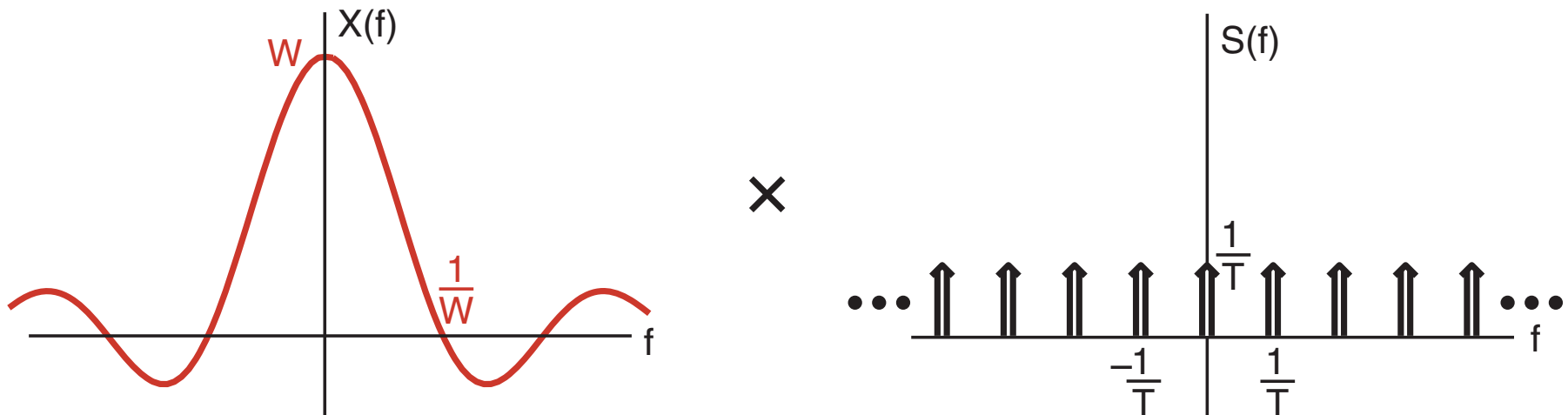


Overall Frequency Transform of a Square Wave

- **Resulting transform relationship**

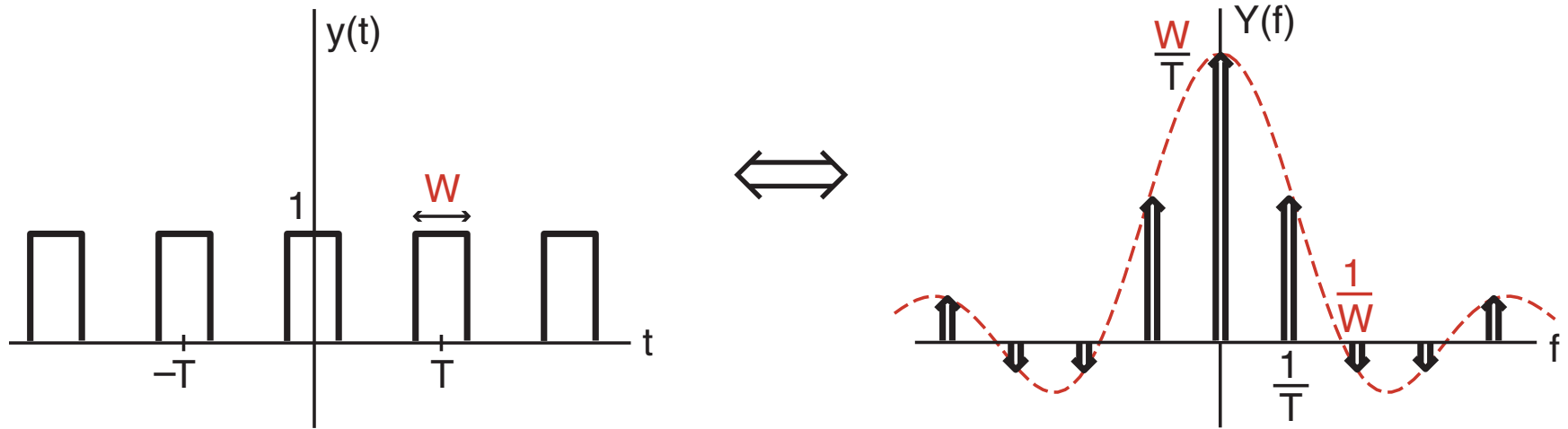


- **Fundamental at frequency $1/T$**
 - Higher harmonics have lower magnitude
- **If $W = T/2$ (i.e., 50% duty cycle)**
 - No even harmonics!
- **If amplitude varies between 1 and -1 (rather than 1 and 0)**
 - No DC component

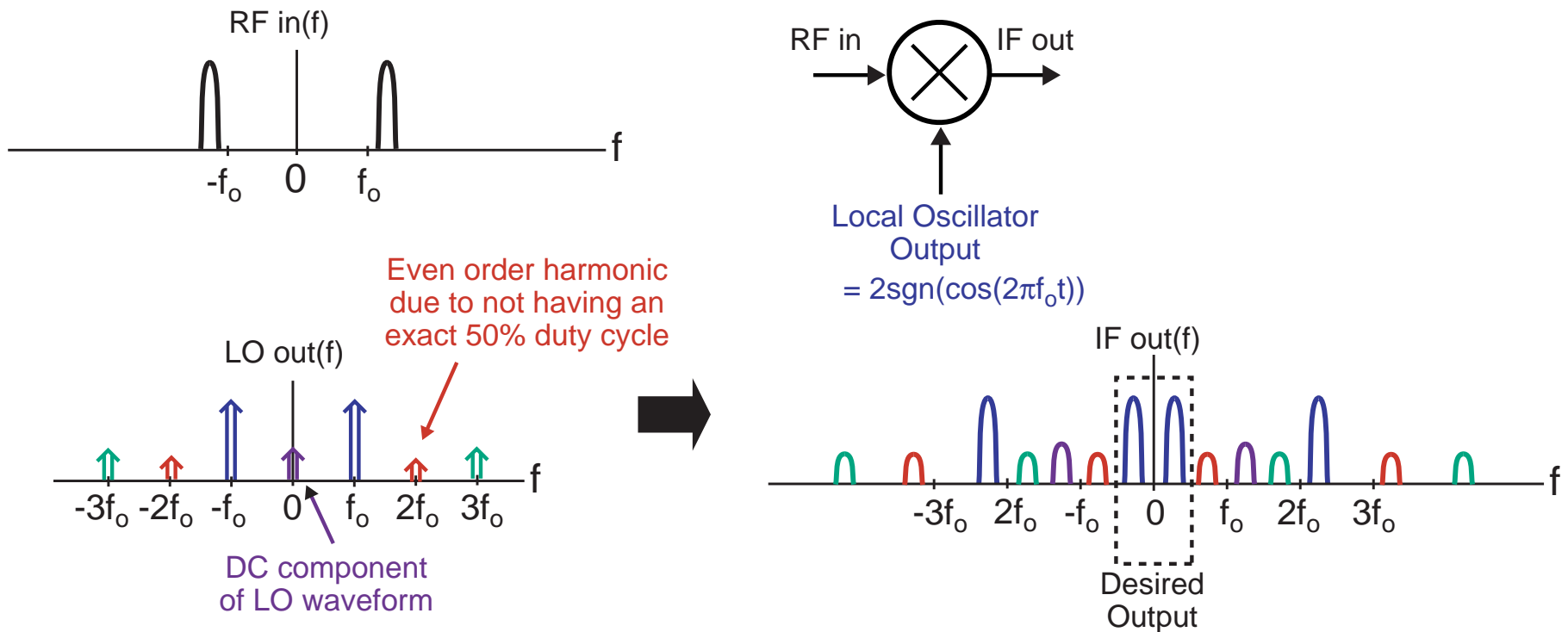Analysis of Using Square-Wave for LO Signal



- **Each frequency component of LO signal will now mix with the RF input**
 - If RF input spectrum sufficiently narrowband with respect to f_0 , then no aliasing will occur
- **Desired output (mixed by the fundamental component) can be extracted using a filter at the IF output**

Voltage Conversion Gain

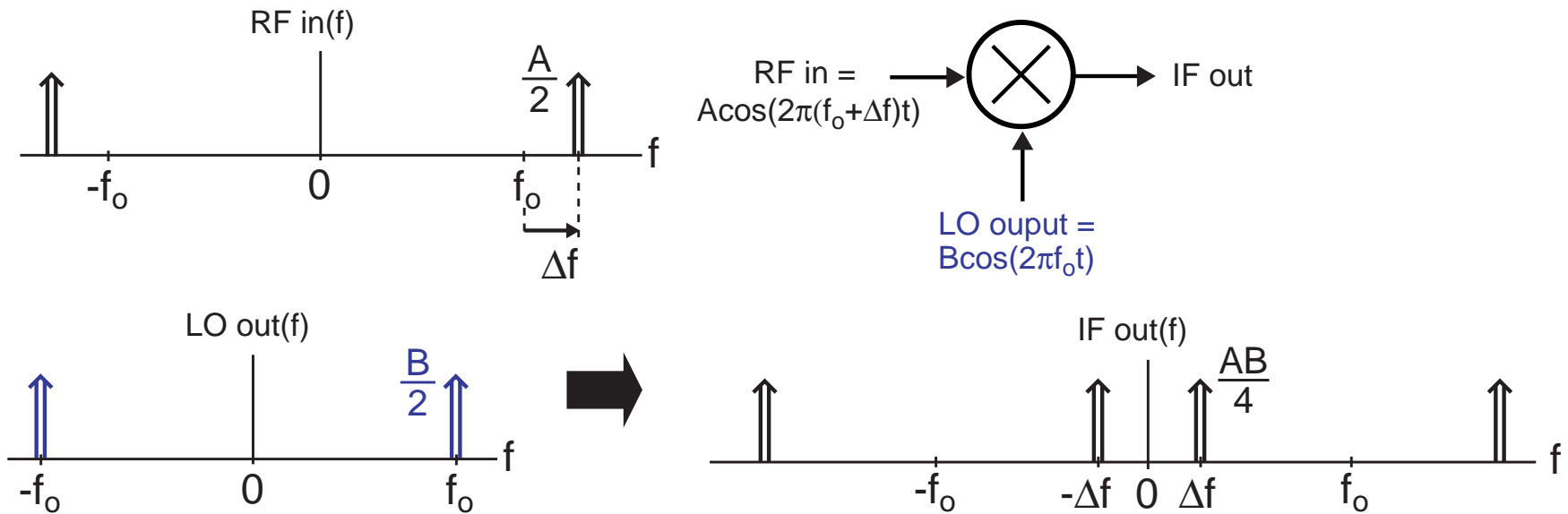


- Defined as voltage ratio of desired IF value to RF input
- Example: for an ideal mixer with RF input = $A \sin(2\pi(f_0 + \Delta f)t)$ and sine wave LO signal = $B \cos(2\pi f_0 t)$

$$IF \text{ out}(t) = \frac{AB}{2} \left(\cos(2\pi(\Delta f)t) + \cos(2\pi(2f_0 + \Delta f)t) \right)$$

$$\Rightarrow \text{Voltage Conversion Gain} = \frac{AB/2}{A} = \frac{B}{2}$$


- For practical mixers, value depends on mixer topology and LO signal (i.e., sine or square wave)

Impact of High Voltage Conversion Gain

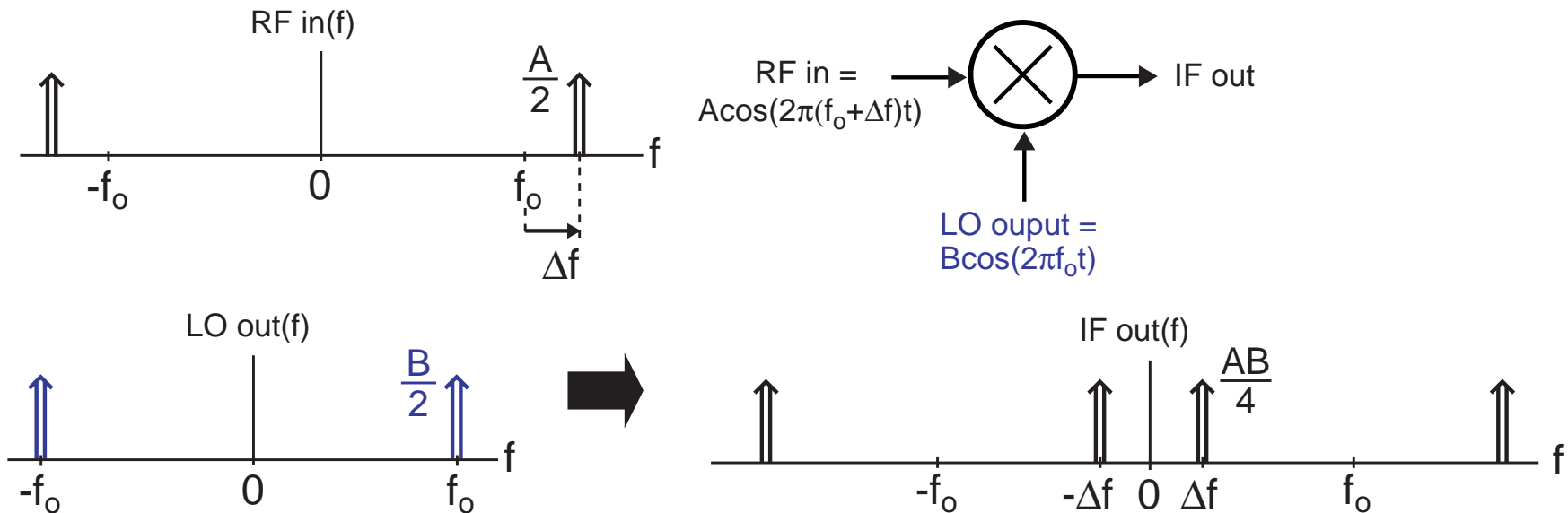


- **Benefit of high voltage gain**
 - The noise of later stages will have less of an impact
- **Issues with high voltage gain**
 - May be accompanied by higher noise figure than could be achieved with lower voltage gain
 - May be accompanied by nonlinearities that limit interference rejection (i.e., passive mixers can generally be made more linear than active ones)

Impact of Nonlinearity in Mixers

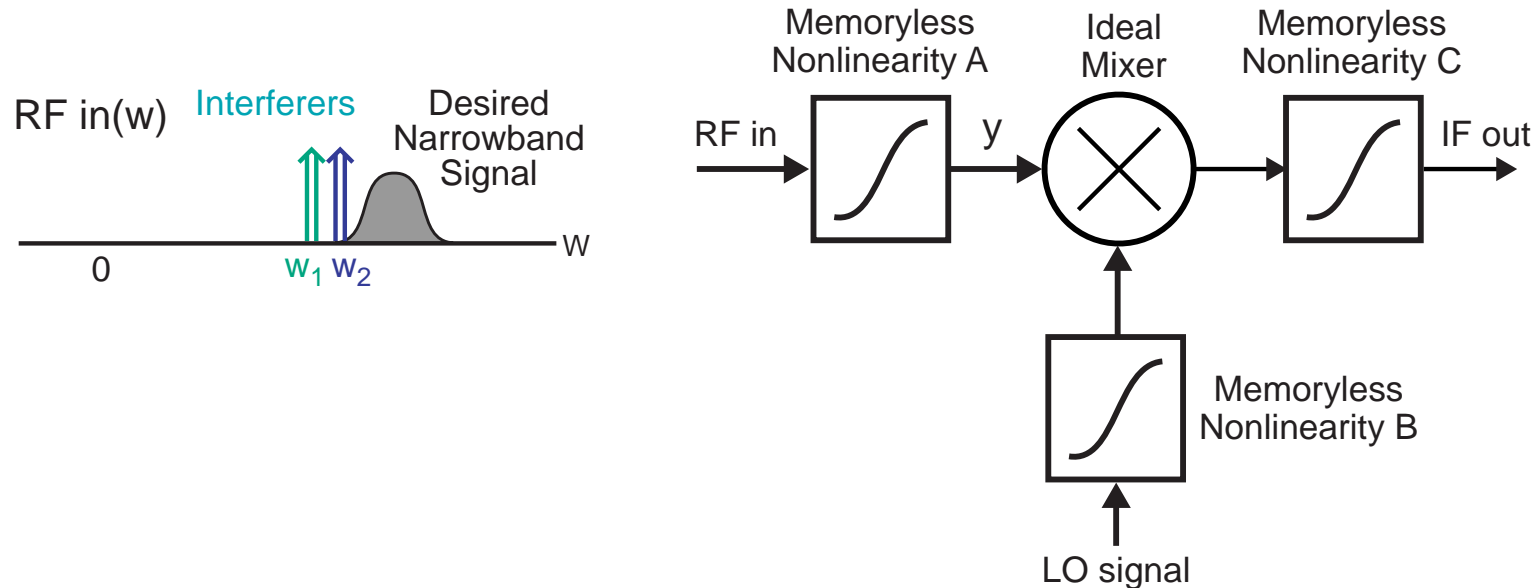


- Ignoring dynamic effects, we can model mixer as nonlinearities around an ideal mixer
 - Nonlinearity A will have the same impact as LNA nonlinearity (measured with IIP3)
 - Nonlinearity B will change the spectrum of the LO signal
 - Causes additional mixing that must be analyzed
 - Changes conversion gain somewhat
 - Nonlinearity C will cause self mixing of IF output

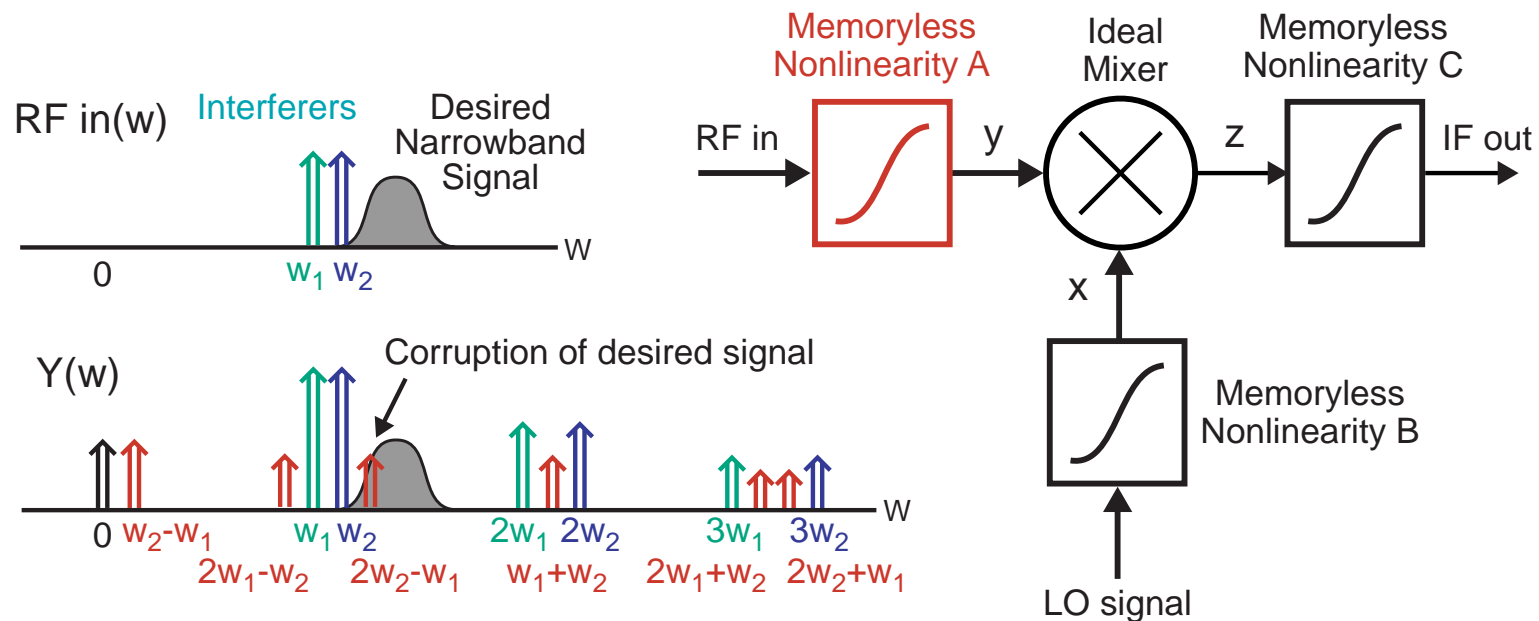Primary Focus is Typically Nonlinearity in RF Input Path



- **Nonlinearity B not detrimental in most cases**
 - LO signal often a square wave anyway
- **Nonlinearity C can be avoided by using a linear load (such as a resistor)**
- **Nonlinearity A can hamper rejection of interferers**
 - Characterize with IIP3 as with LNA designs
 - Use two-tone test to measure (similar to LNA)


The Issue of Balance in Mixers

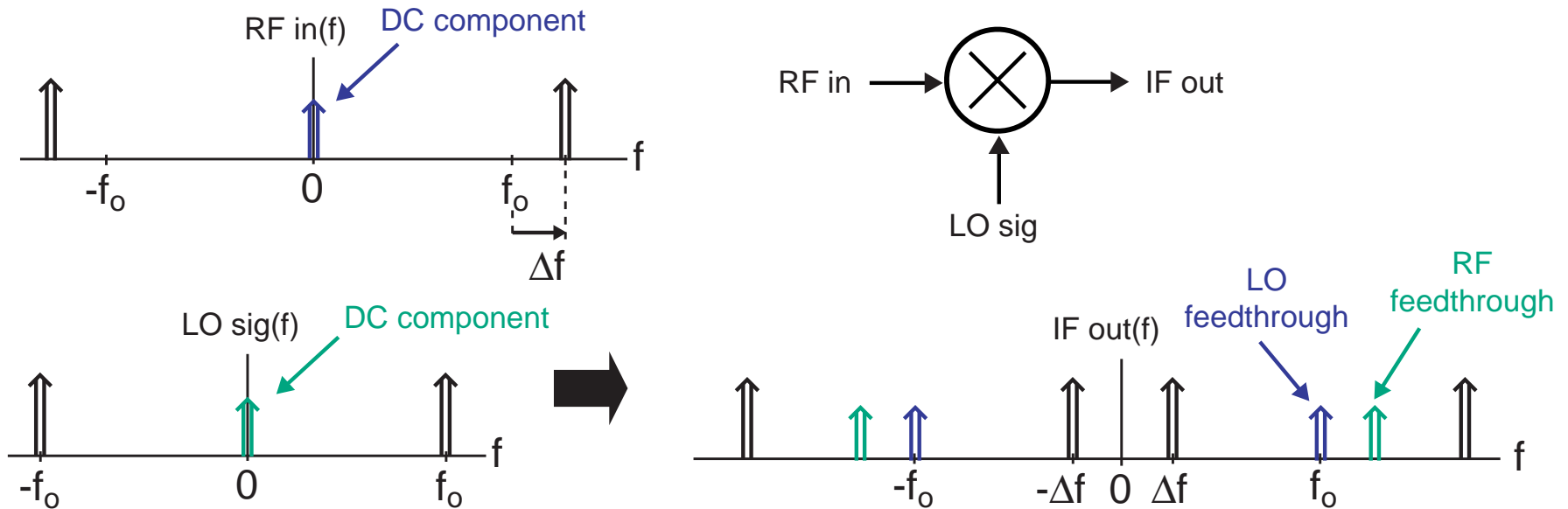

- A balanced signal is defined to have a zero DC component
- Mixers have two signals of concern with respect to this issue – LO and RF signals
 - Unbalanced RF input causes LO feedthrough
 - Unbalanced LO signal causes RF feedthrough
- Issue – transistors require a DC offset


Achieving a Balanced LO Signal with DC Biasing

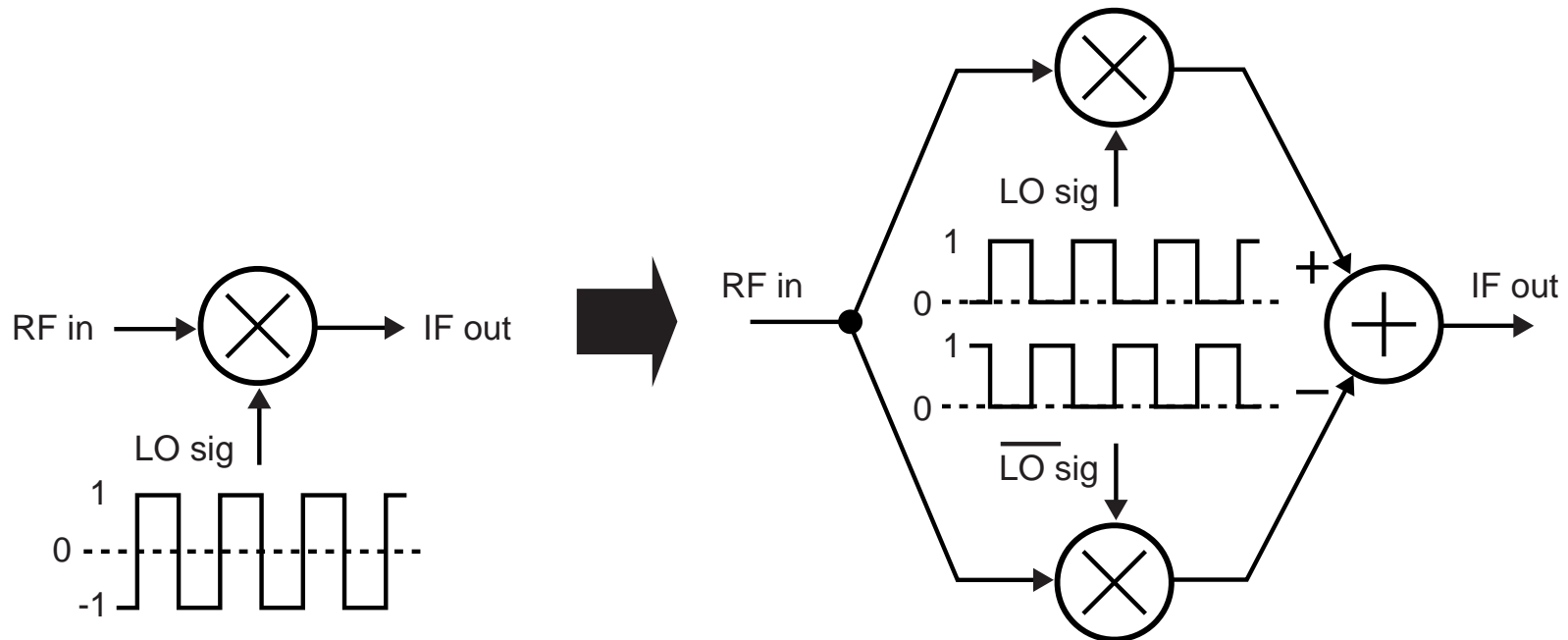- Combine two mixer paths with LO signal 180 degrees out of phase between the paths




- DC component is cancelled

Single-Balanced Mixer

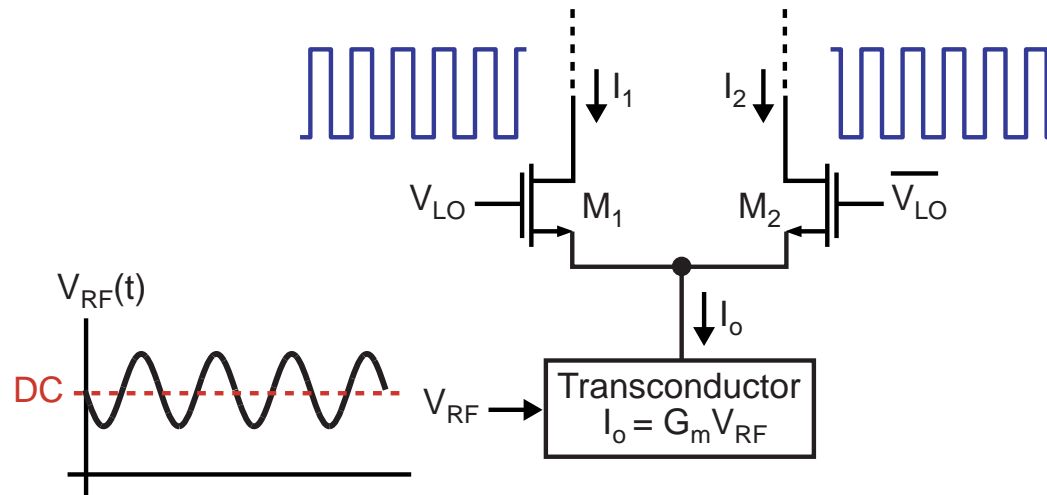


- Works by converting RF input voltage to a current, then switching current between each side of differential pair
- Achieves LO balance using technique on previous slide
 - Subtraction between paths is inherent to differential output
- LO swing should be no larger than needed to fully turn on and off differential pair
 - Square wave is best to minimize noise from M_1 and M_2
- Transconductor designed for high linearity

Transconductor Implementation 1

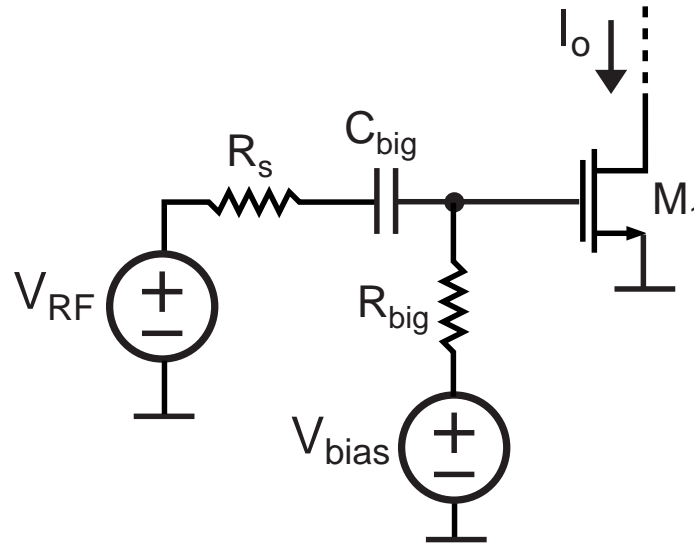


- Apply RF signal to input of common source amp
 - Transistor assumed to be in saturation
 - Transconductance value is the same as that of the transistor
- High V_{bias} places device in velocity saturation
 - Allows high linearity to be achieved

Transconductor Implementation 2

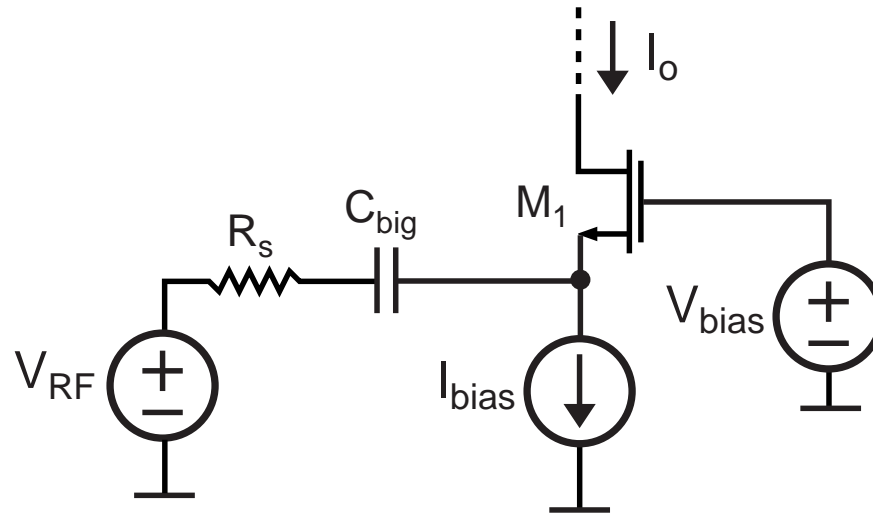


- Apply RF signal to a common gate amplifier
- Transconductance value set by inverse of series combination of R_s and $1/g_m$ of transistor
 - Amplifier is effectively degenerated to achieve higher linearity
- I_{bias} can be set for large current density through device to achieve higher linearity (velocity saturation)

Transconductor Implementation 3

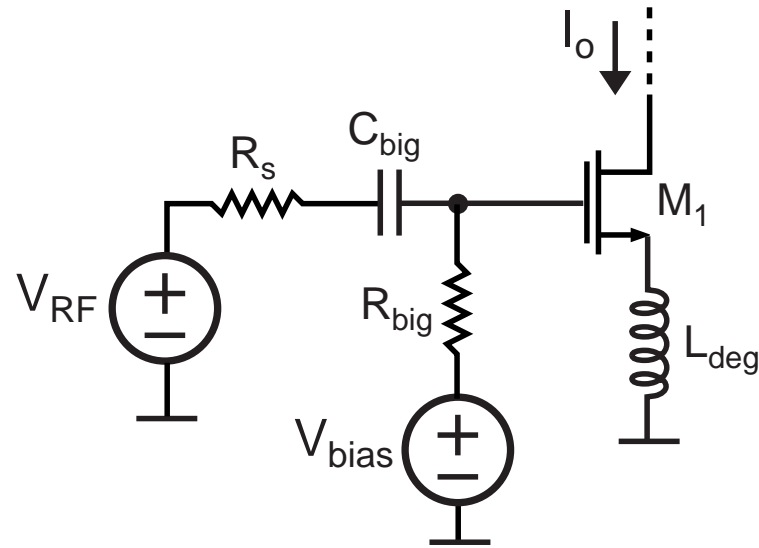


- **Add degeneration to common source amplifier**
 - **Inductor better than resistor**
 - No DC voltage drop
 - Increased impedance at high frequencies helps filter out undesired high frequency components
 - **Don't generally resonate inductor with C_{gs}**
 - Power match usually not required for IC implementation due to proximity of LNA and mixer

LO Feedthrough in Single-Balanced Mixers

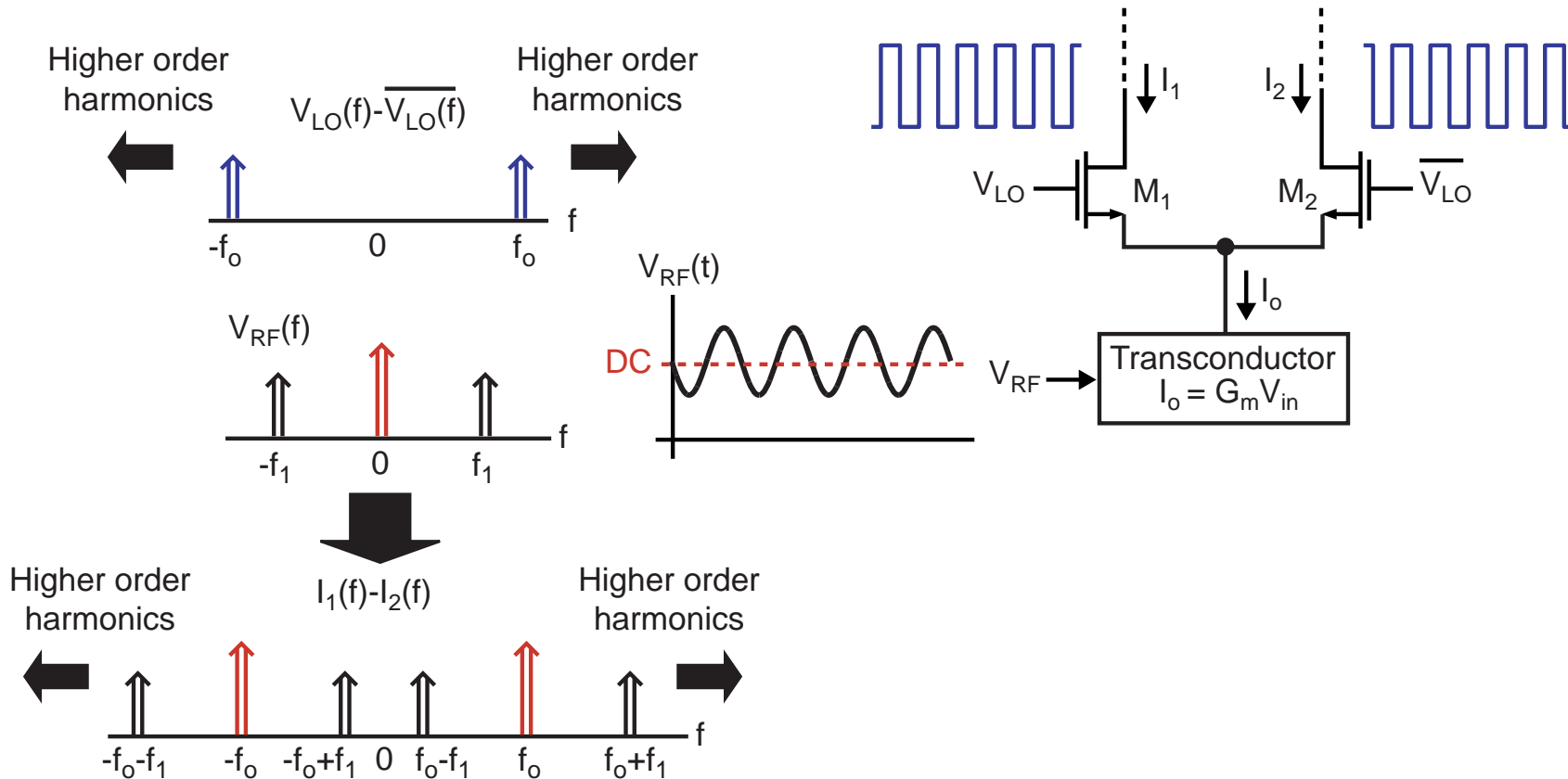

- **DC component of RF input causes very large LO feedthrough**
 - Can be removed by filtering, but can also be removed by achieving a zero DC value for RF input


Double-Balanced Mixer

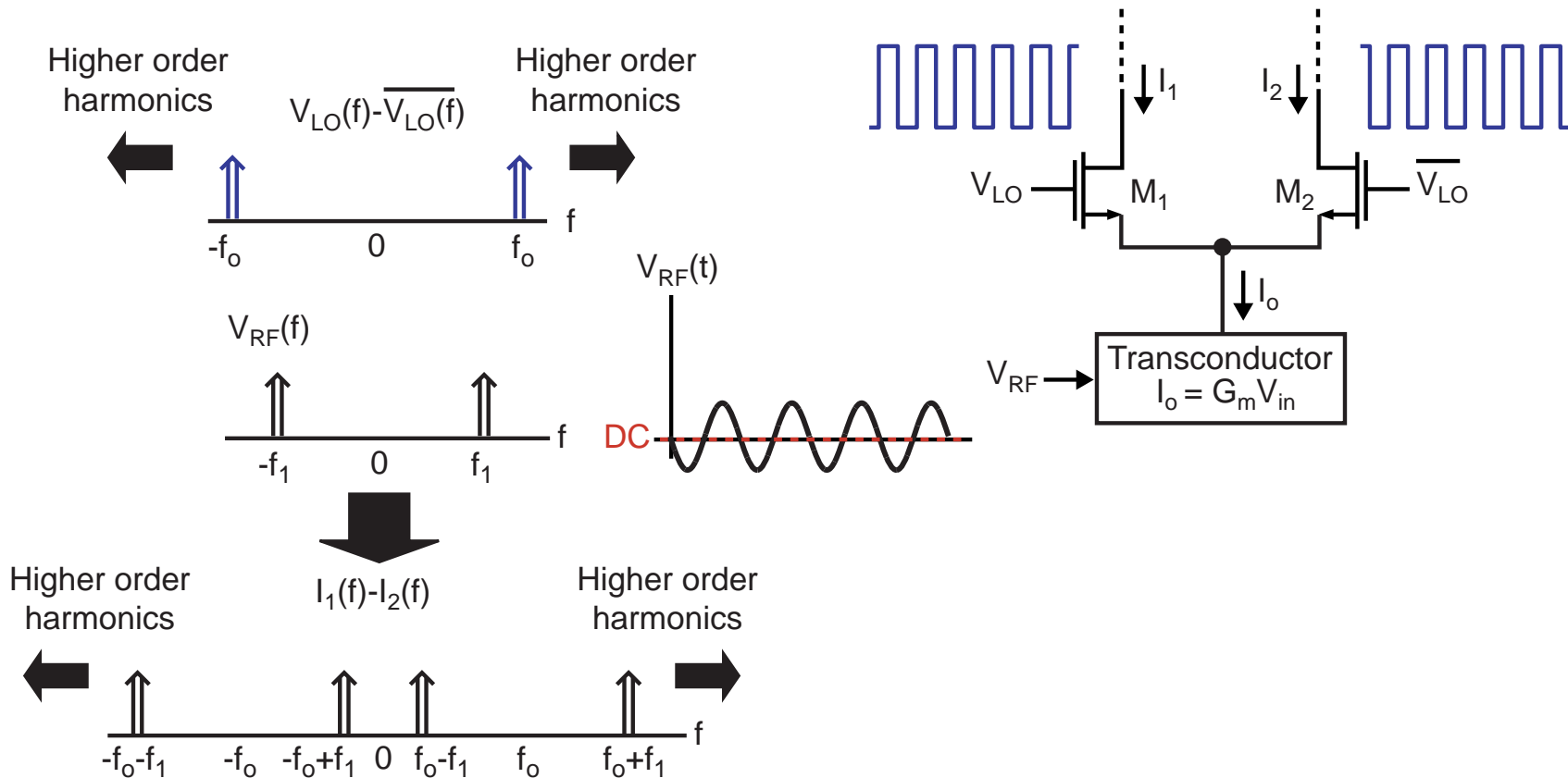


- DC values of LO and RF signals are zero (balanced)
- LO feedthrough dramatically reduced!
- But, practical transconductor needs bias current

Achieving a Balanced RF Signal with Biasing

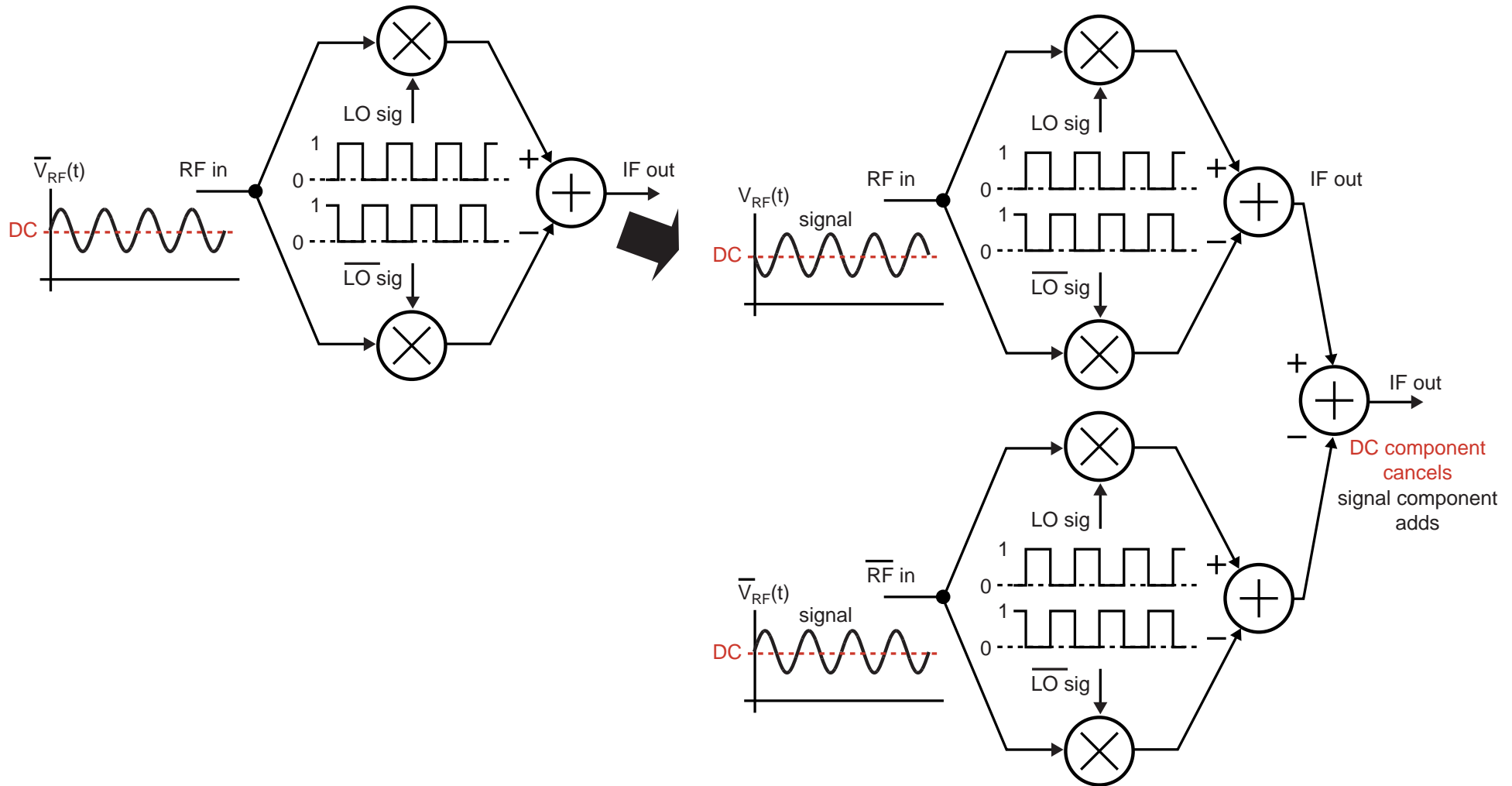- Use the same trick as with LO balancing




Double-Balanced Mixer Implementation

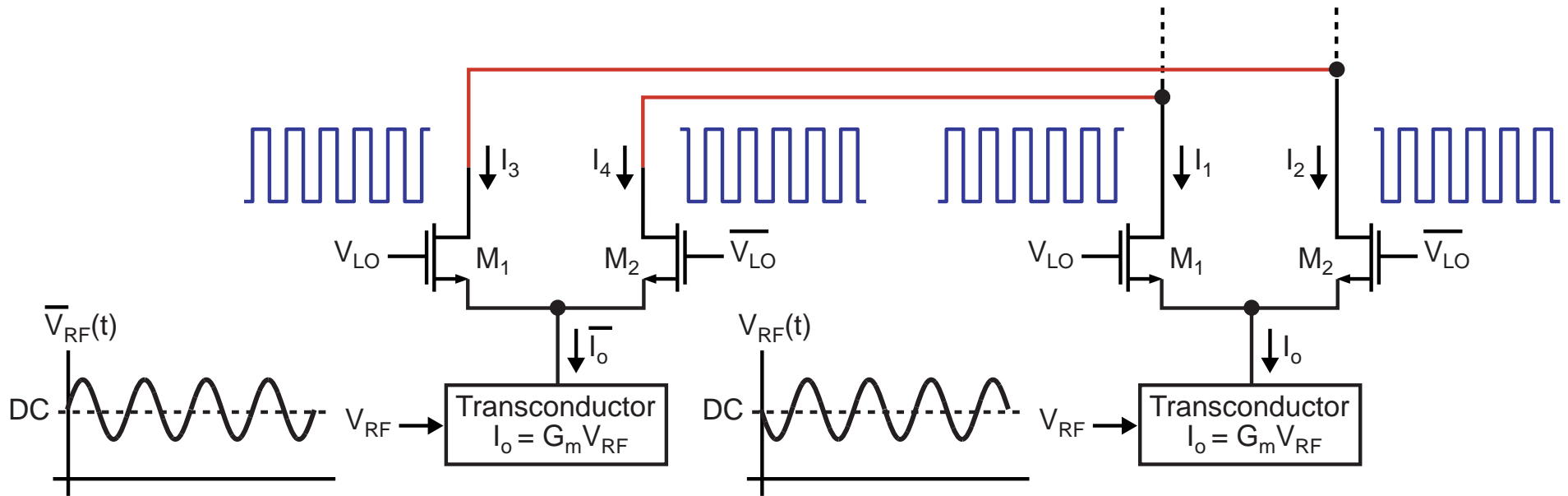


- Applies technique from previous slide
 - Subtraction at the output achieved by cross-coupling the output current of each stage

Gilbert Mixer

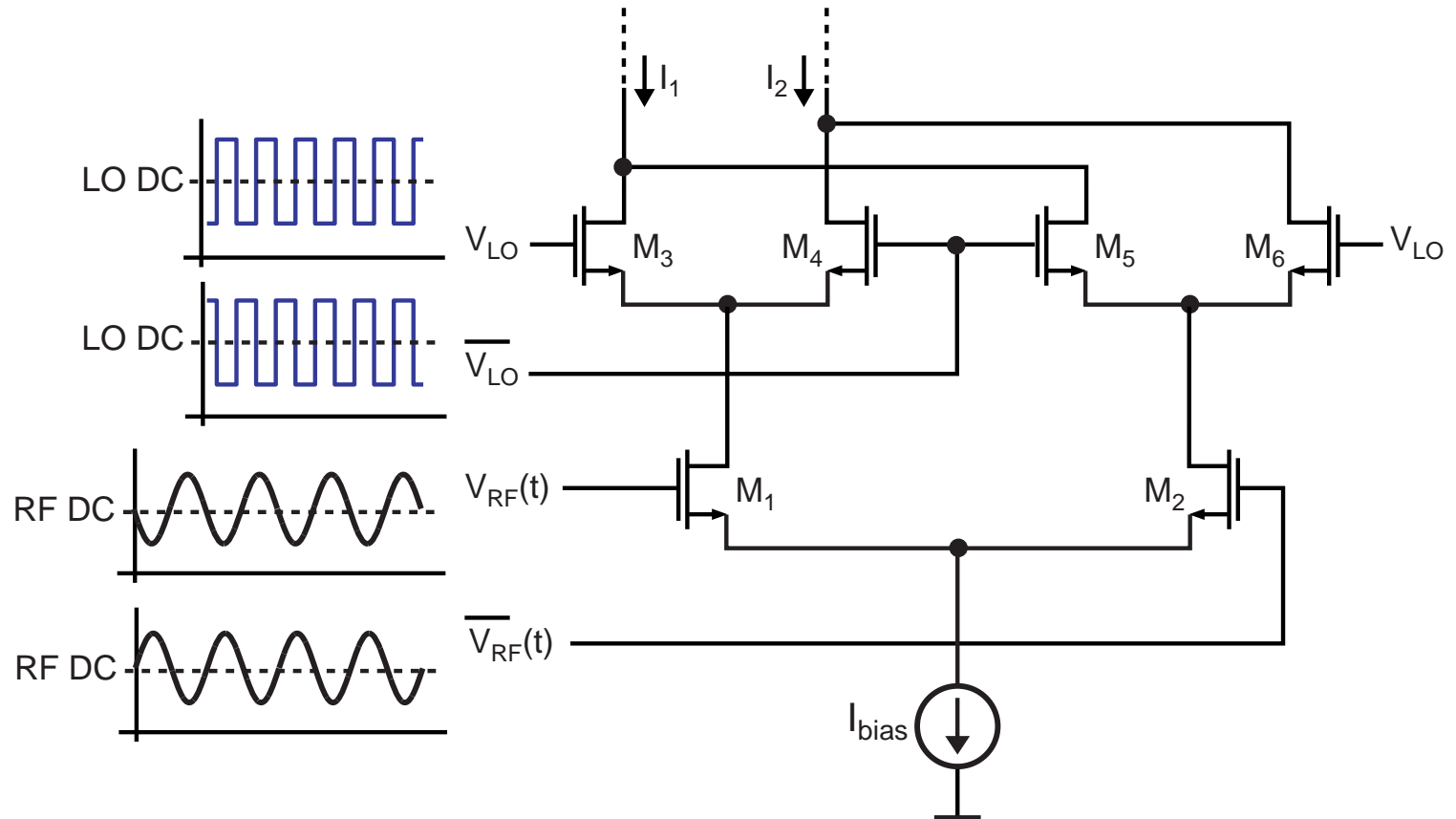


- Use a differential pair to achieve the transconductor implementation
- This is the preferred mixer implementation for most radio systems!

A Highly Linear CMOS Mixer

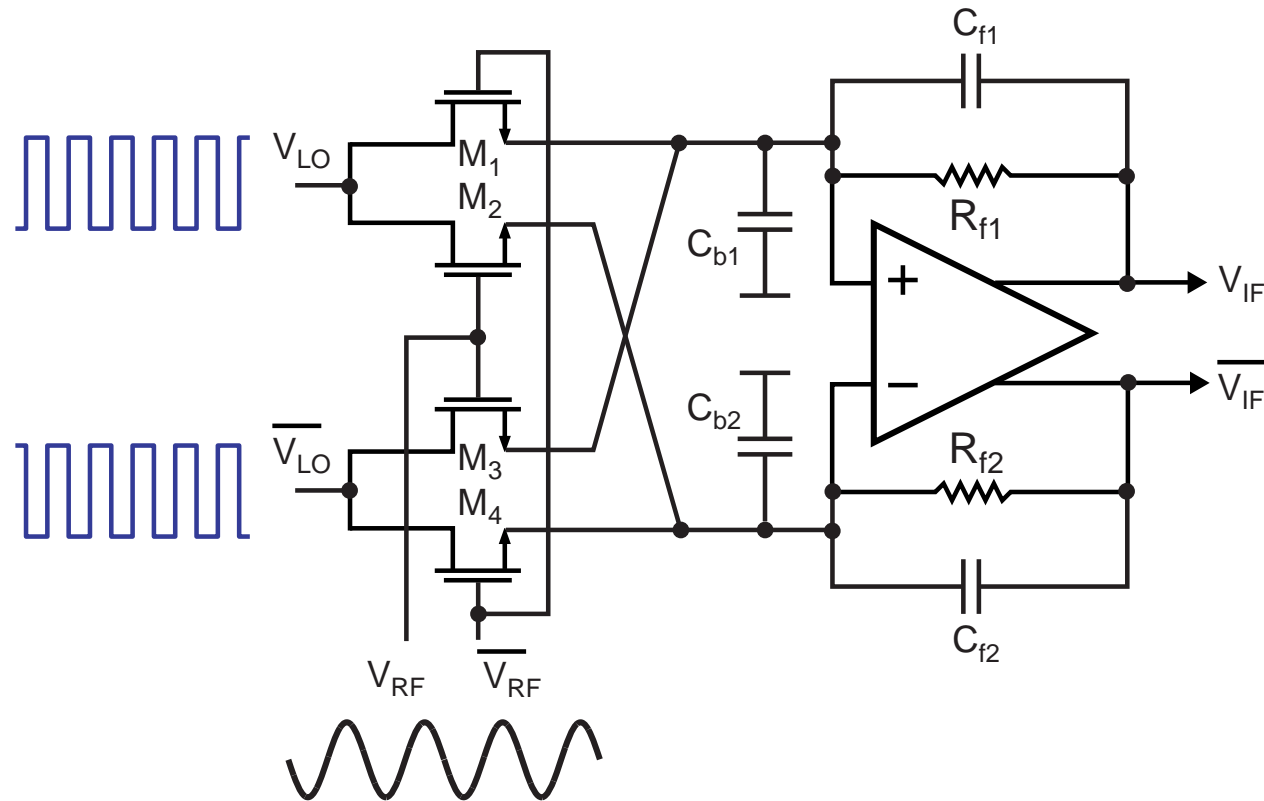


- Transistors are alternated between the off and triode regions by the LO signal
 - RF signal varies resistance of channel when in triode
 - Large bias required on RF inputs to achieve triode operation
- High linearity achieved, but very poor noise figure

Passive Mixers

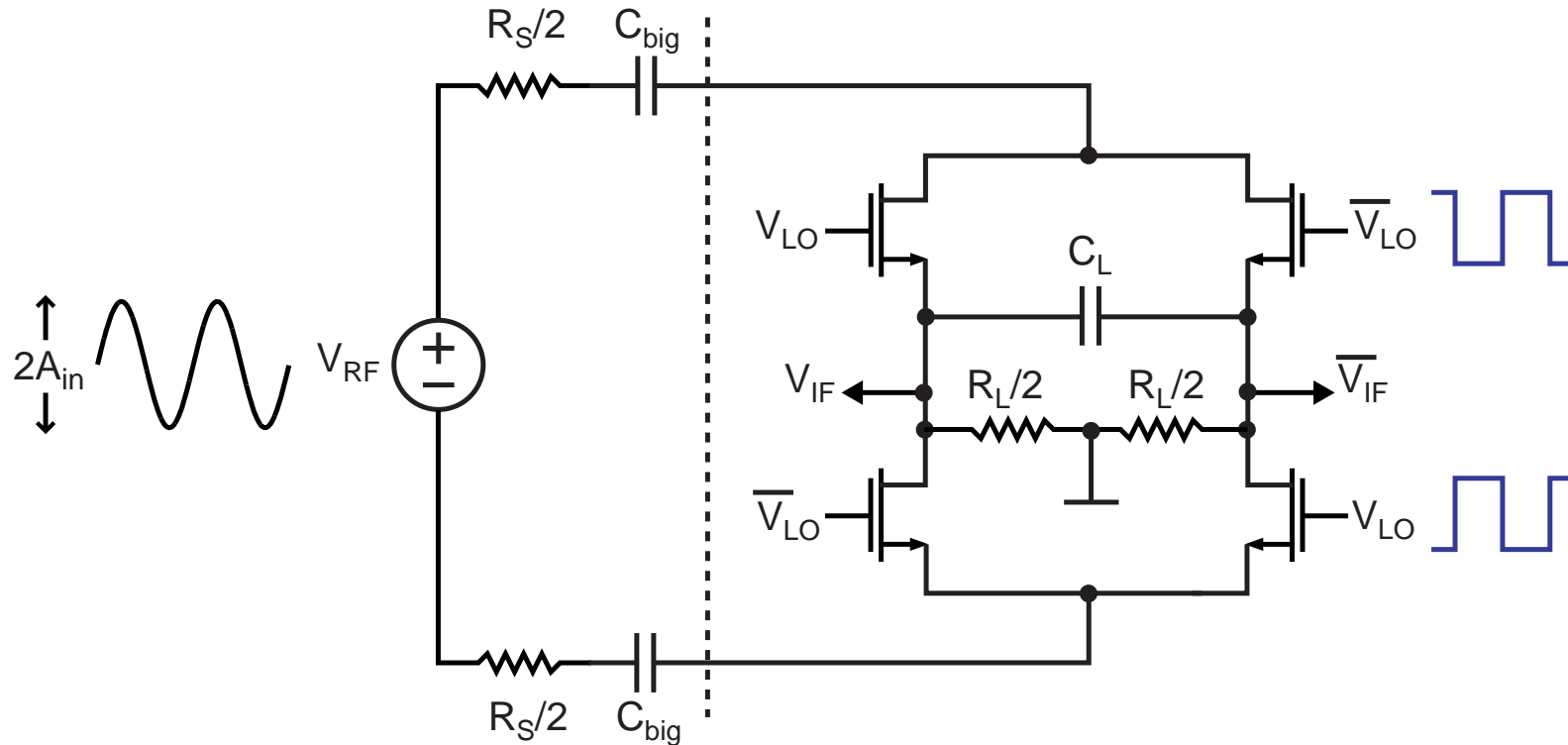

- We can avoid the transconductor and simply use switches to perform the mixing operation
 - No bias current required allows low power operation to be achieved
- You can learn more about it in Homework 4!

Square-Law Mixer

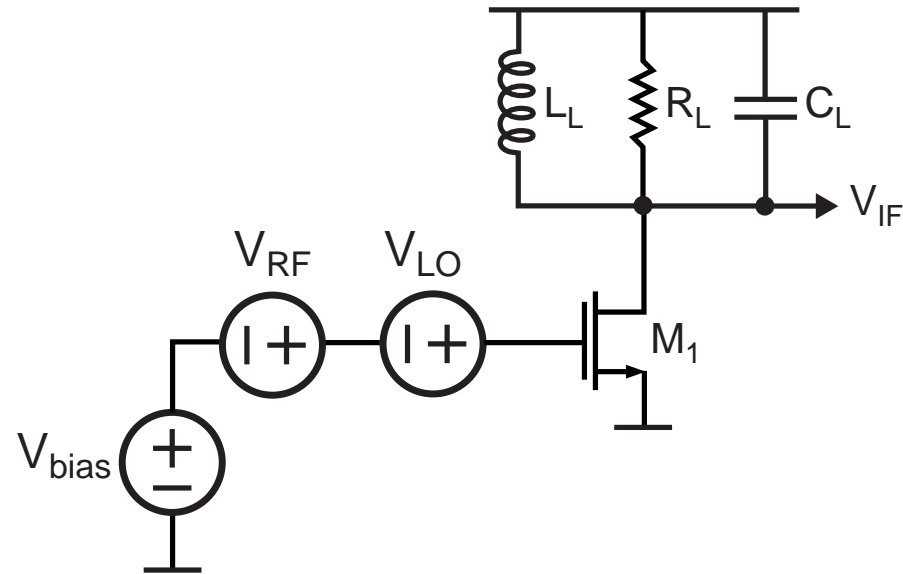


- Achieves mixing through nonlinearity of MOS device
 - Ideally square law, which leads to a multiplication term

$$(V_{RF} + V_{LO})^2 = V_{RF}^2 + 2V_{RF}V_{LO} + V_{LO}^2$$

- Undesired components must be filtered out
- Need a long channel device to get square law behavior
- Issue – no isolation between LO and RF ports

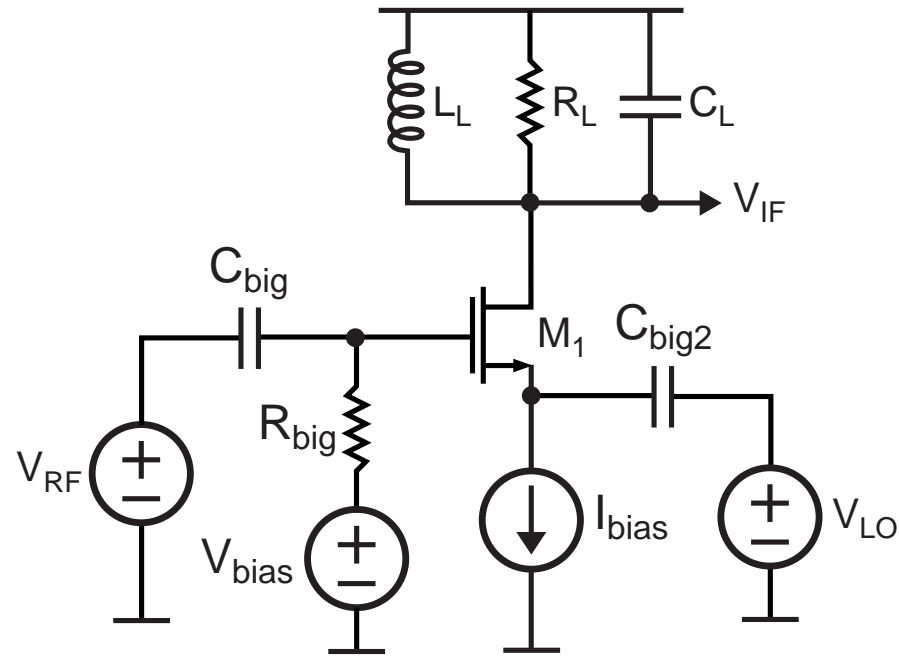Alternative Implementation of Square Law Mixer



- **Drives LO and RF inputs on separate parts of the transistor**
 - Allows some isolation between LO and RF signals
- **Issue - poorer performance compared to multiplication-based mixers**
 - Lots of undesired spectral components
 - Poorer isolation between LO and RF ports