

High Speed Communication Circuits and Systems
Lecture 17
Advanced Frequency Synthesizers


Michael H. Perrott

April 7, 2004

Copyright © 2004 by Michael H. Perrott

All rights reserved.

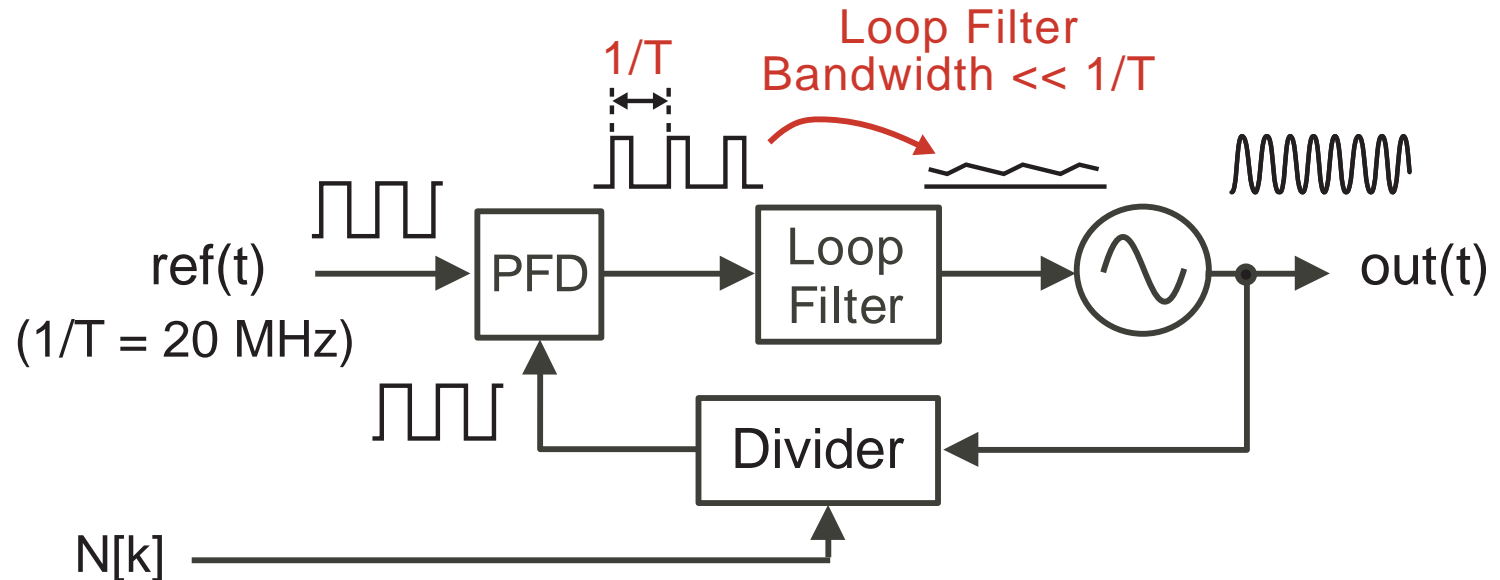
Bandwidth Constraints for Integer-N Synthesizers



- **PFD output has a periodicity of $1/T$**
 - $1/T =$ reference frequency
- **Loop filter must have a bandwidth $\ll 1/T$**
 - PFD output pulses must be filtered out and average value extracted


Closed loop PLL bandwidth often chosen to be a factor of ten lower than $1/T$

Bandwidth Versus Frequency Resolution

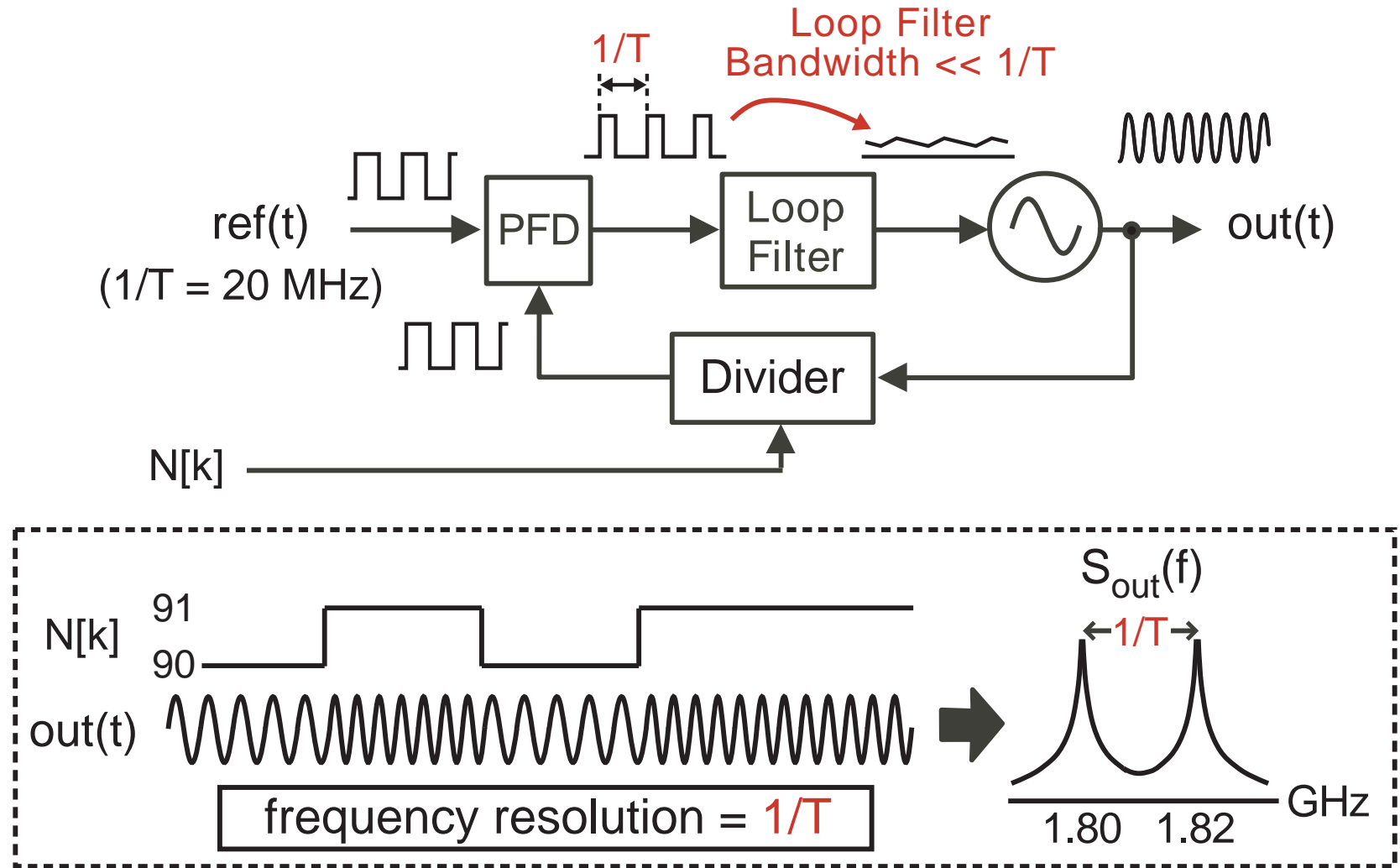


- Frequency resolution set by reference frequency ($1/T$)
 - Higher resolution achieved by lowering $1/T$

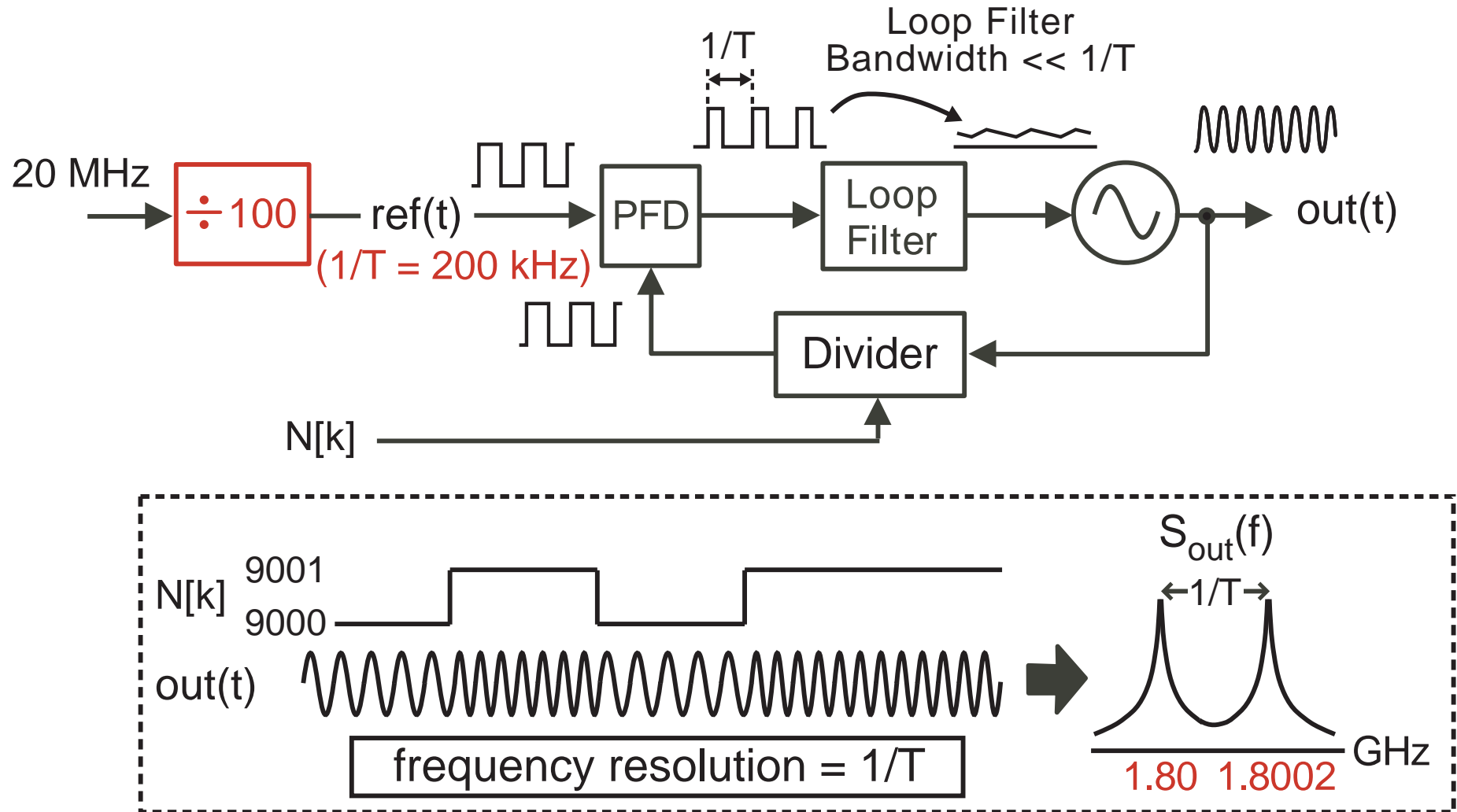Increasing Resolution in Integer-N Synthesizers




- Use a reference divider to achieve lower $1/T$
 - Leads to a low PLL bandwidth ($< 20 \text{ kHz}$ here)

The Issue of Noise

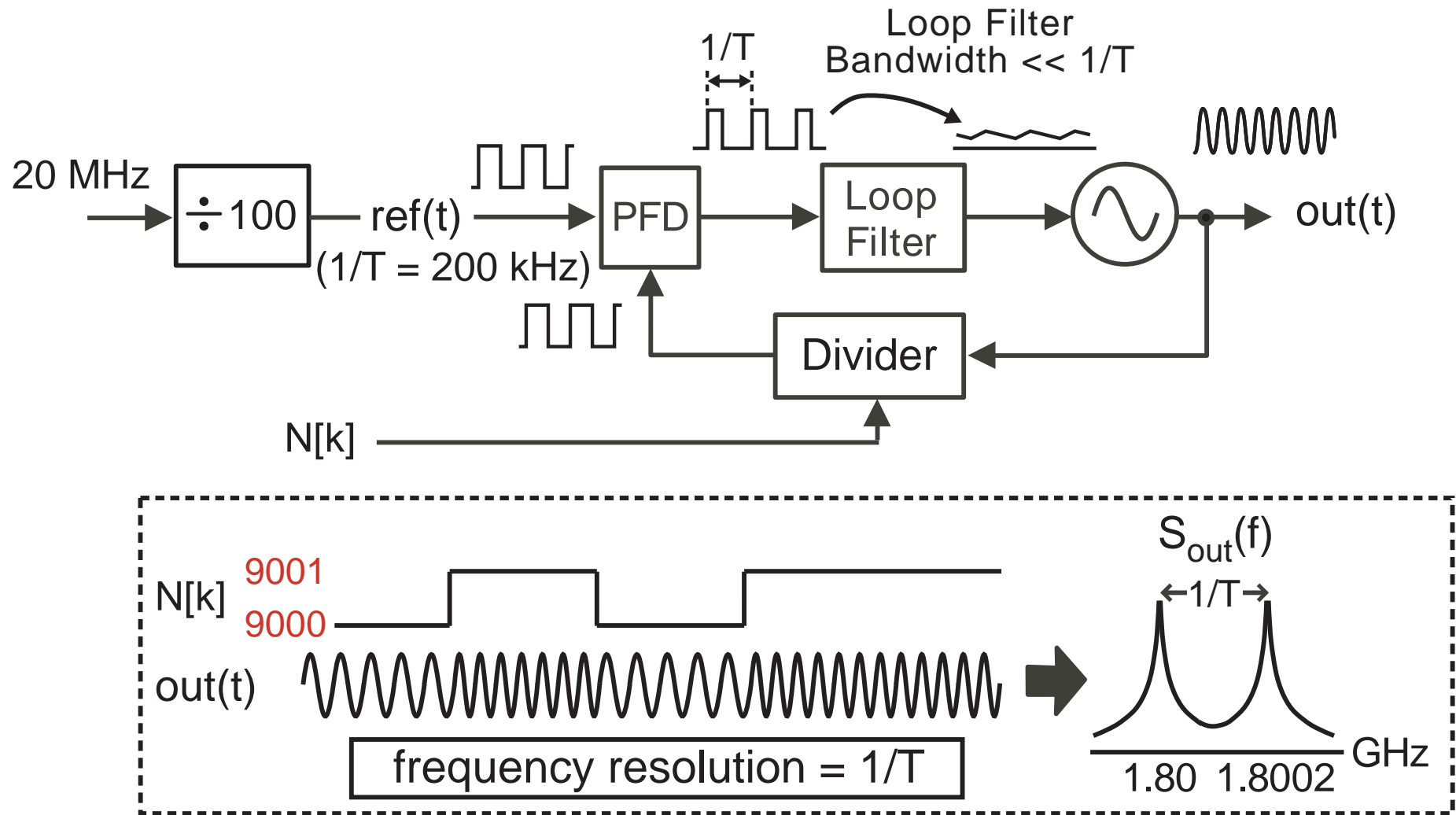

- Lower $1/T$ leads to higher divide value
 - Increases PFD noise at synthesizer output


Modeling PFD Noise Multiplication

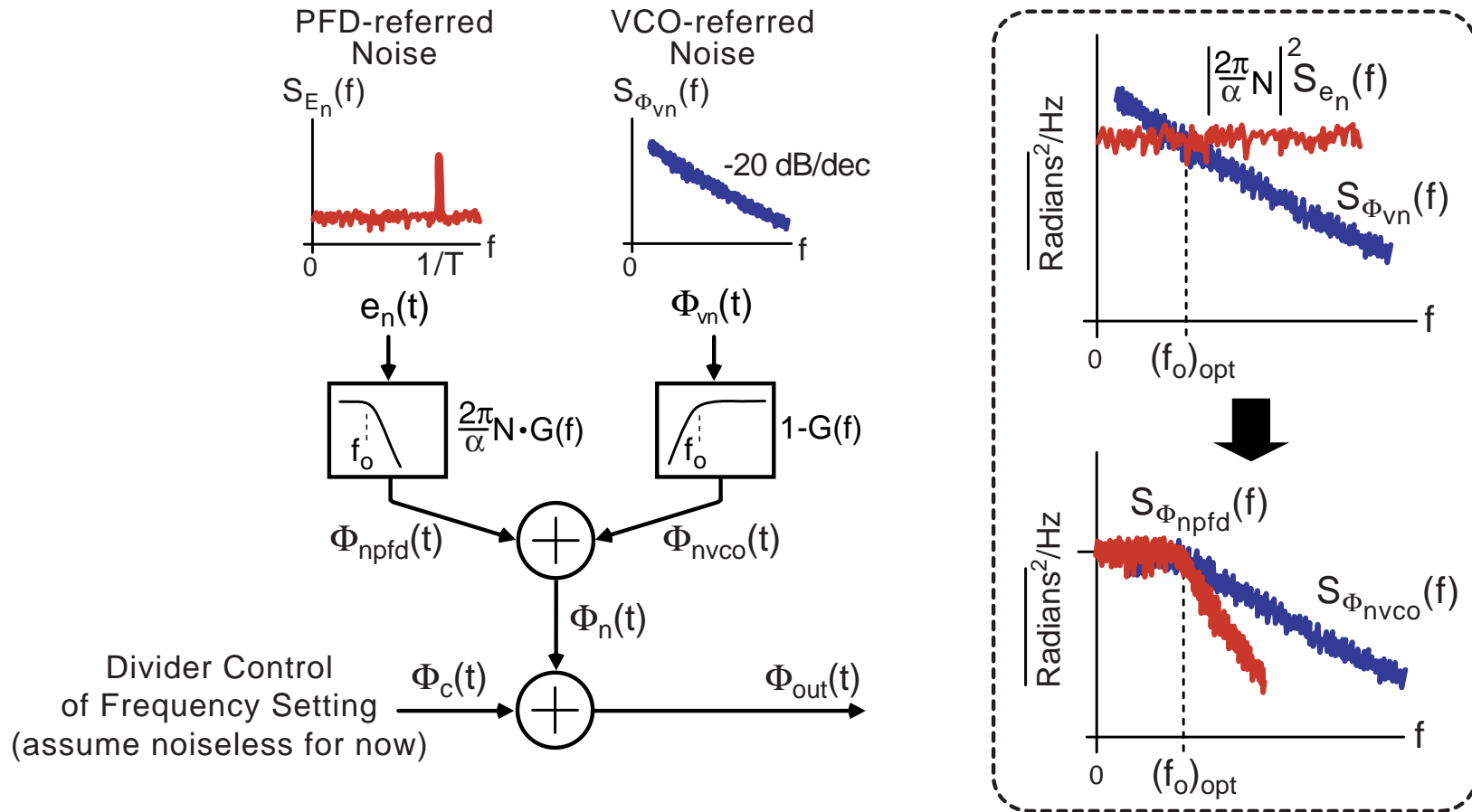

- **Influence of PFD noise seen in model from Lecture 16**
 - PFD spectral density multiplied by N^2 before influencing PLL output phase noise

High divide values \Rightarrow high phase noise at low frequencies

Dual-Loop Frequency Synthesizer

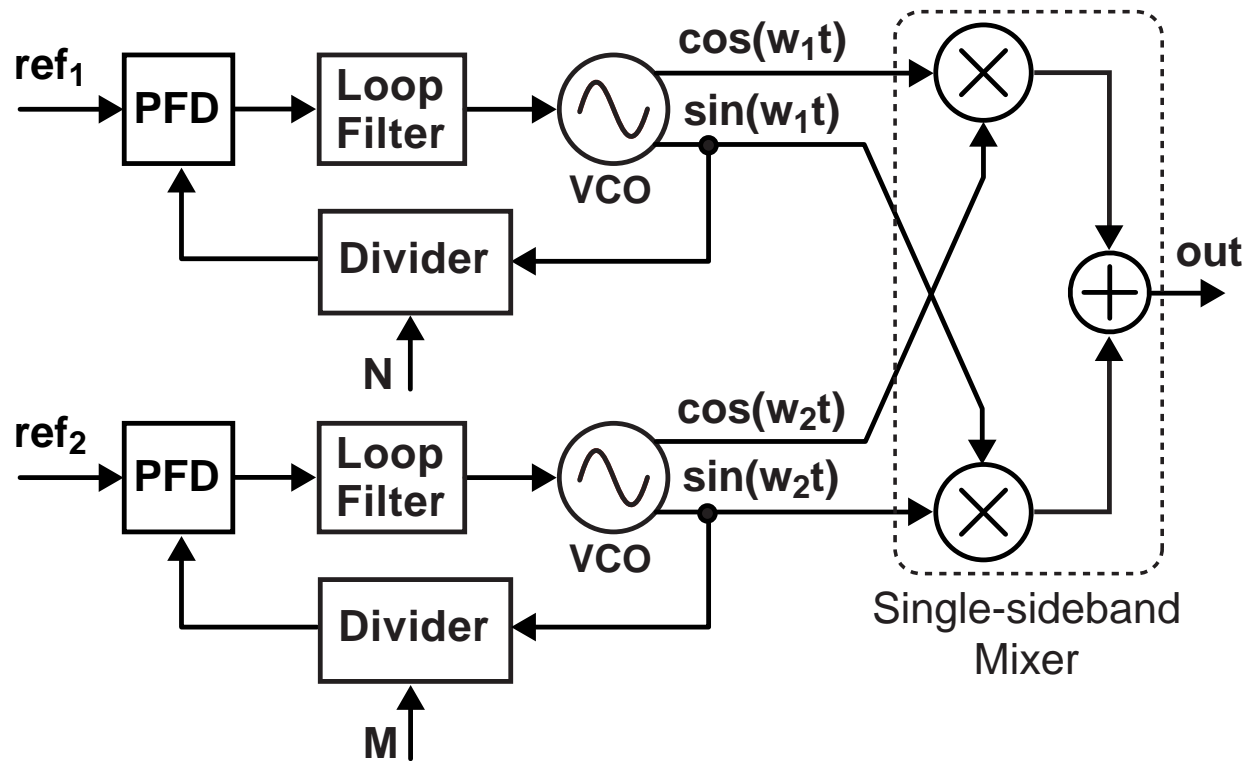


- Overall synthesizer output

$$out(t) = \cos(w_1t) \cos(w_2t) + \sin(w_1t) \sin(w_2t)$$

- From trigonometry: $\cos(A-B) = \cos A \cos B + \sin A \sin B$


$$\Rightarrow out(t) = \cos((w_1 - w_2)t)$$

Advantage #1: Avoids Large Divide Values

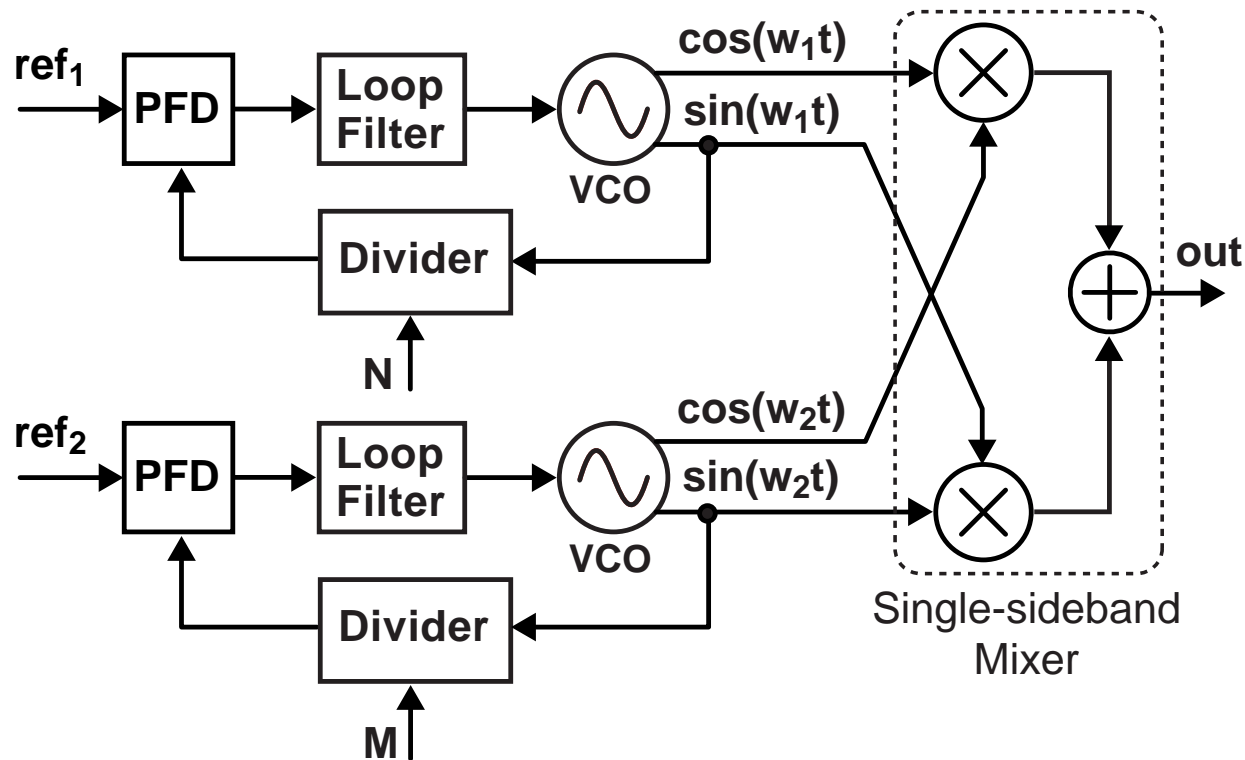


- Choose top synthesizer to provide coarse tuning and bottom synthesizer to provide fine tuning
 - Choose ω_1 to be high in frequency
 - Set ref_1 to be high to avoid large N \Rightarrow low resolution
 - Choose ω_2 to be low in frequency
 - Allows ref_2 to be low without large M \Rightarrow high resolution

 Advantage #2: Provides Suppression of VCO Noise



- Top VCO has much more phase noise than bottom VCO due to its much higher operating frequency
 - Suppress top VCO noise by choosing a high PLL bandwidth for top synthesizer
 - High PLL bandwidth possible since ref_1 is high

Alternate Dual-Loop Architecture

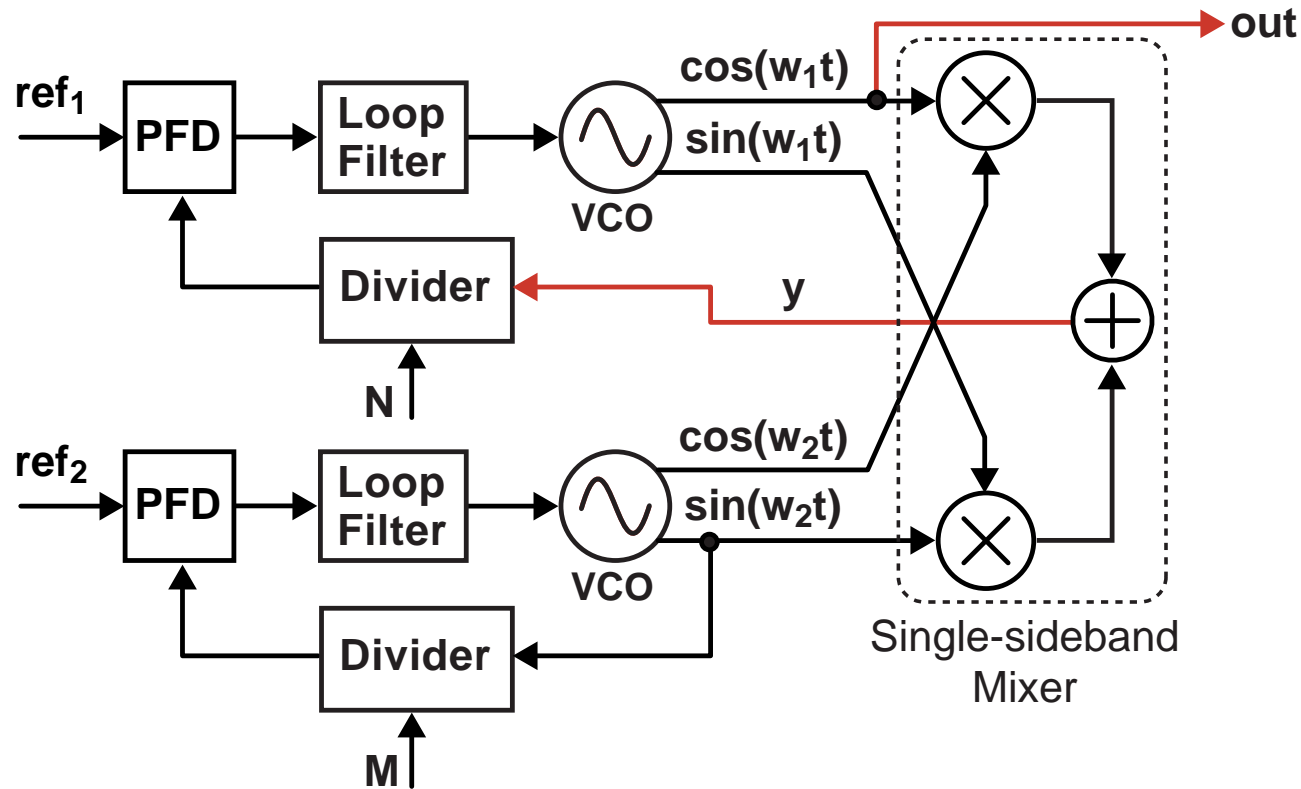


■ Calculation of output frequency

$$y(t) = \cos((w_1 - w_2)t)$$

$$\Rightarrow Nw_{ref_1} = w_1 - w_2$$


$$\Rightarrow \boxed{out(t) = \cos((Nw_{ref_1} + w_2)t)}$$

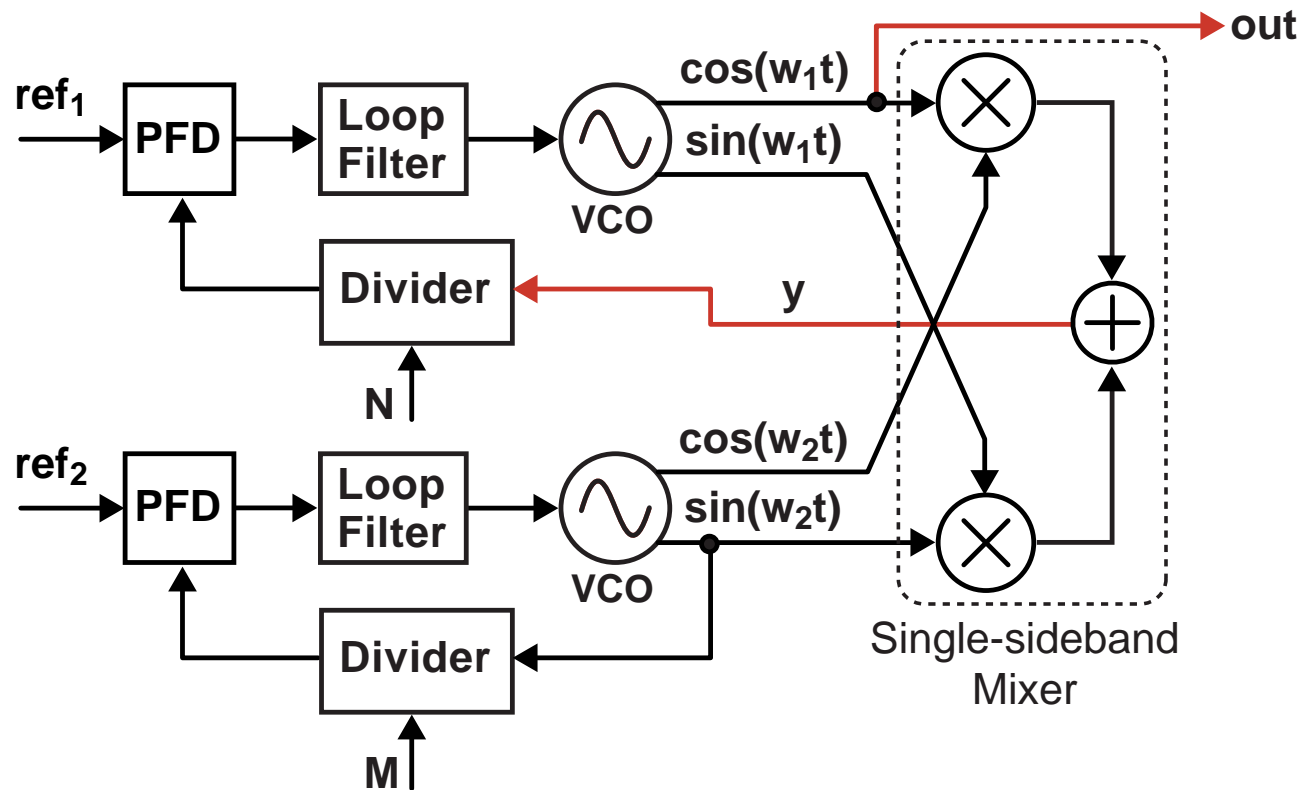Advantage of Alternate Dual-Loop Architecture




- Issue: a practical single-sideband mixer implementation will produce a spur at frequency $\omega_1 + \omega_2$
- PLL bandwidth of top synthesizer can be chosen low enough to suppress the single-sideband spur
 - Negative: lower suppression of top VCO noise

Direct Digital Synthesis (DDS)

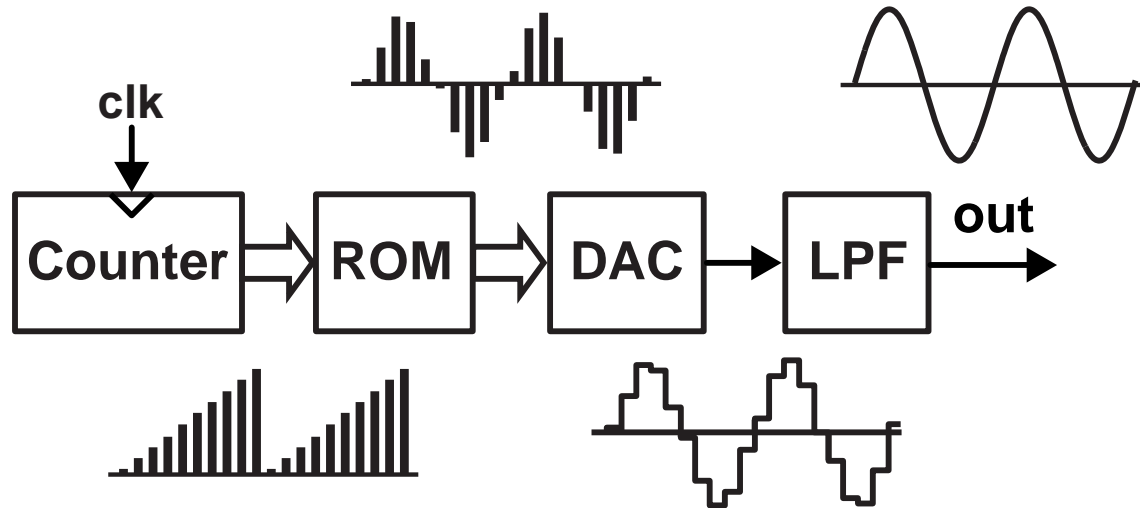

- **Encode sine-wave values in a ROM**
- **Create sine-wave output by indexing through ROM and feeding its output to a DAC and lowpass filter**
 - **Speed at which you index through ROM sets frequency of output sine-wave**
 - Speed of indexing is set by increment value on counter (which is easily adjustable in a digital manner)

 Pros and Cons of Direct Digital Synthesis




■ Advantages

- Very fast adjustment of frequency
- Very high resolution can be achieved
- Highly digital approach

■ Disadvantages


- Difficult to achieve high frequencies
- Difficult to achieve low noise
- Power hungry and complex

Hybrid Approach

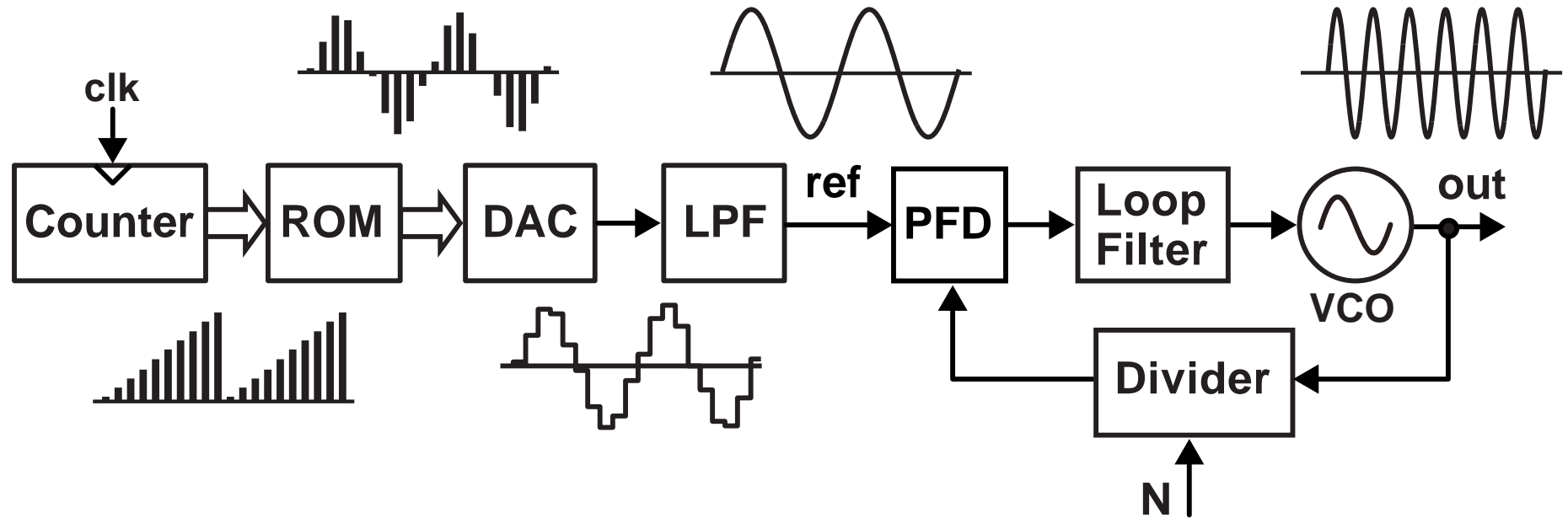


- Use DDS to create a finely adjustable reference frequency
- Use integer-N synthesizer to multiply the DDS output frequency to much higher values
- Issues
 - Noise of DDS is multiplied by N^2
 - Complex and power hungry

Fractional-N Frequency Synthesizers

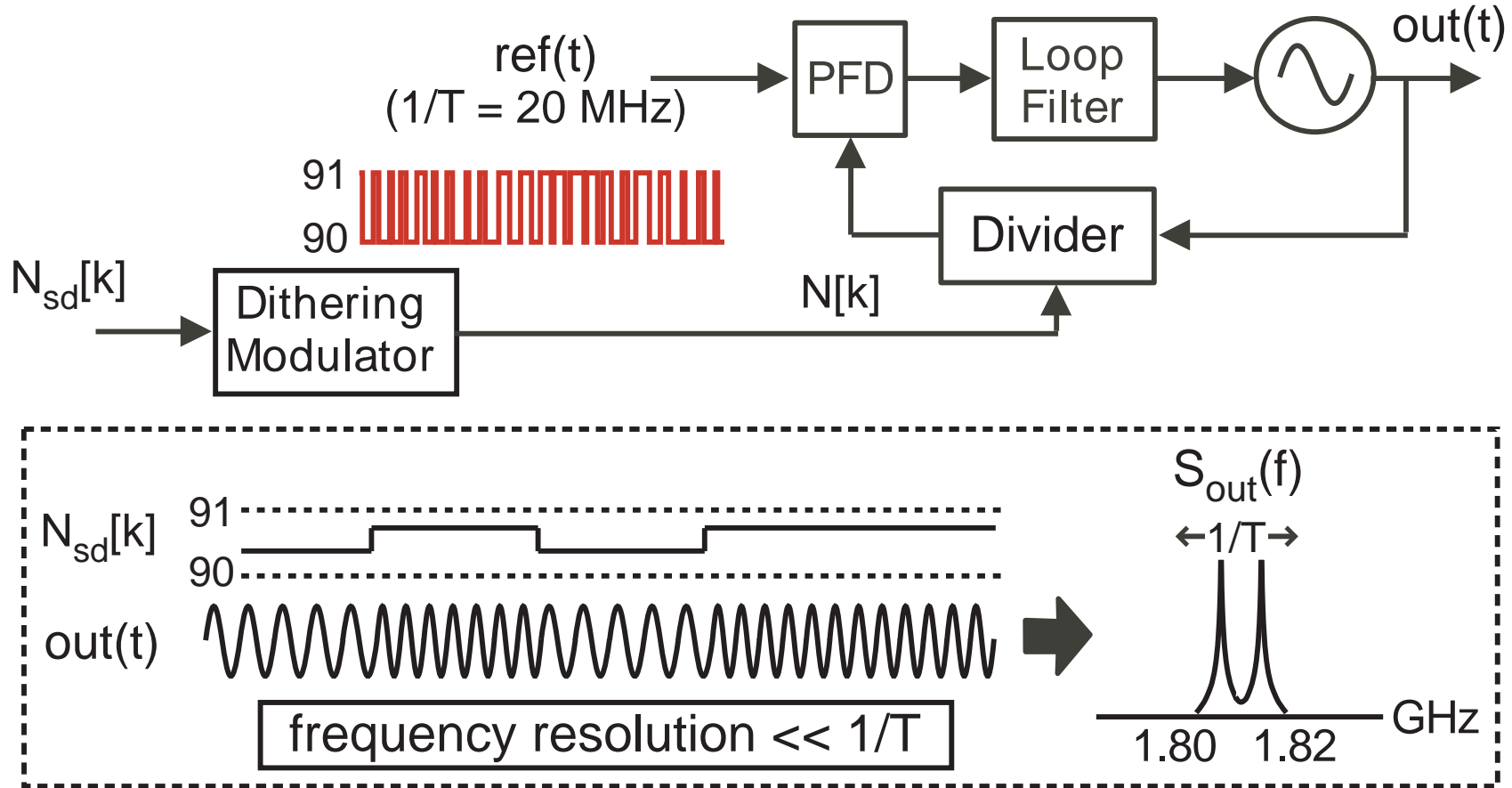


- **Break constraint that divide value be integer**
 - Dither divide value dynamically to achieve fractional values
 - Frequency resolution is now arbitrary regardless of $1/T$
- **Want high $1/T$ to allow a high PLL bandwidth**

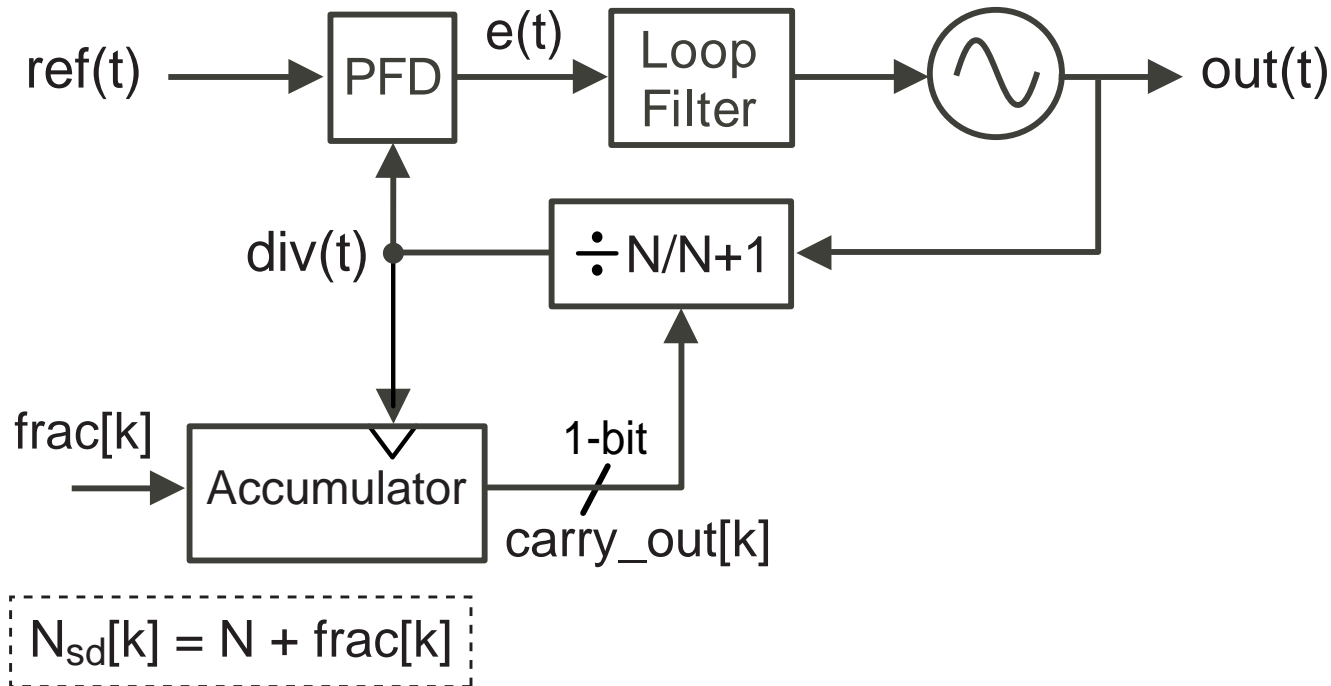Classical Fractional-N Synthesizer Architecture




- **Use an accumulator to perform dithering operation**
 - Fractional input value fed into accumulator
 - Carry out bit of accumulator fed into divider

Accumulator Operation

 


- Carry out bit is asserted when accumulator residue reaches or surpasses its full scale value
 - Accumulator residue increments by input fractional value each clock cycle

 Fractional-N Synthesizer Signals with $N = 4.25$




- **Divide value set at $N = 4$ most of the time**
 - Resulting frequency offset causes phase error to accumulate
 - Reset phase error by “swallowing” a VCO cycle
 - Achieved by dividing by 5 every 4 reference cycles

The Issue of Spurious Tones

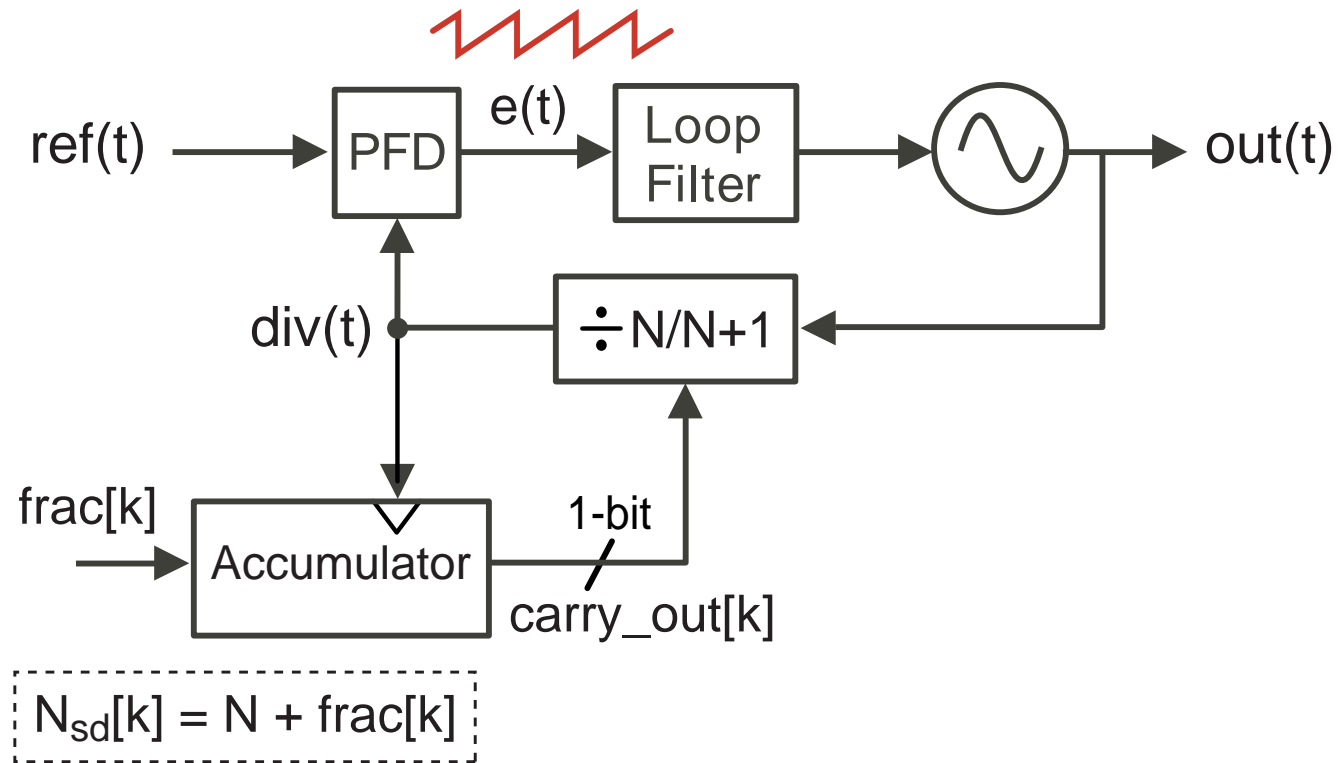


- **PFD error is periodic**
 - Note that actual PFD waveform is series of pulses – the sawtooth waveform represents pulse width values over time
- **Periodic error signal creates spurious tones in synthesizer output**
 - Ruins noise performance of synthesizer

The Phase Interpolation Technique

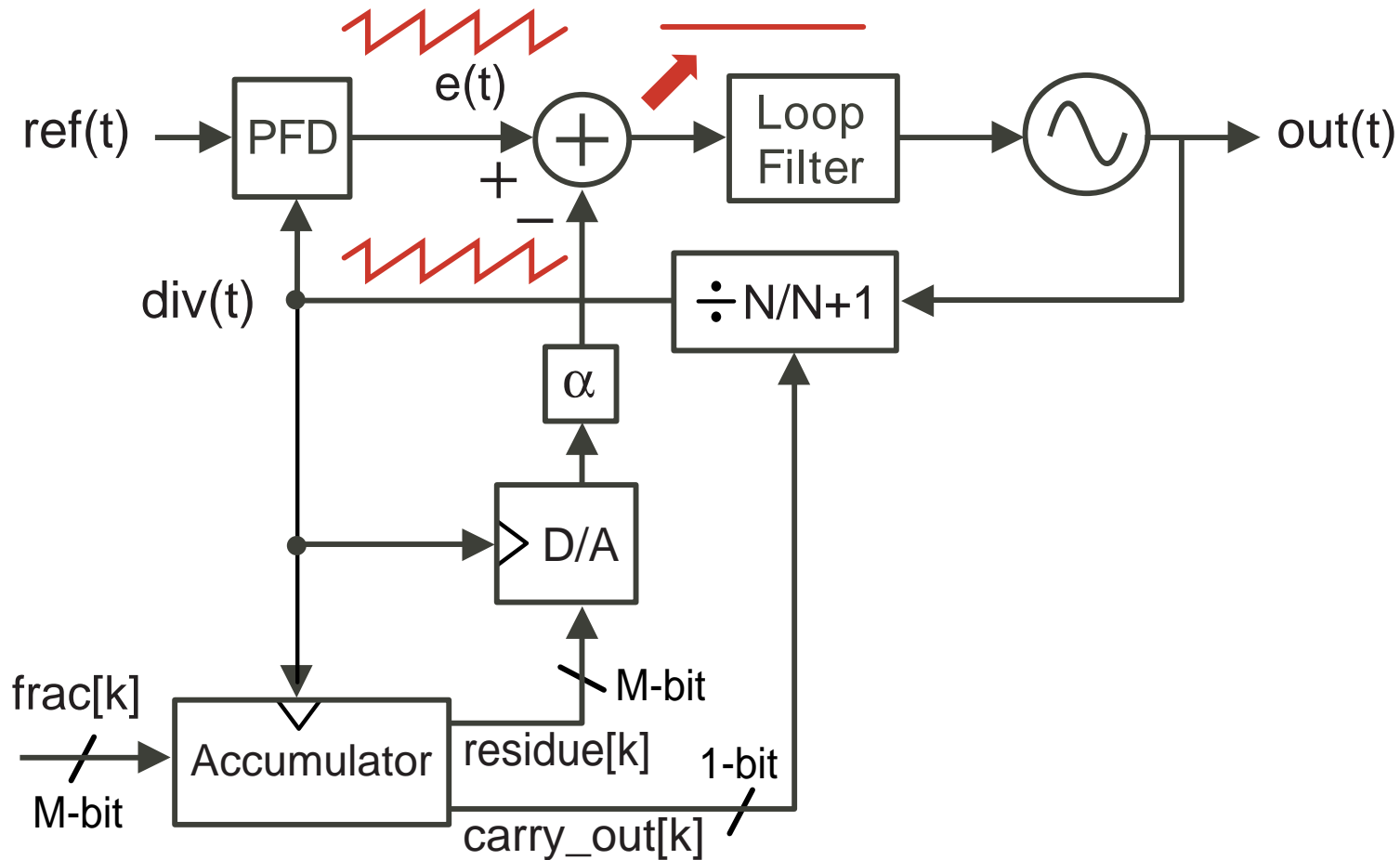

- Phase error due to fractional technique is predicted by the instantaneous residue of the accumulator
 - Cancel out phase error based on accumulator residue


The Problem With Phase Interpolation

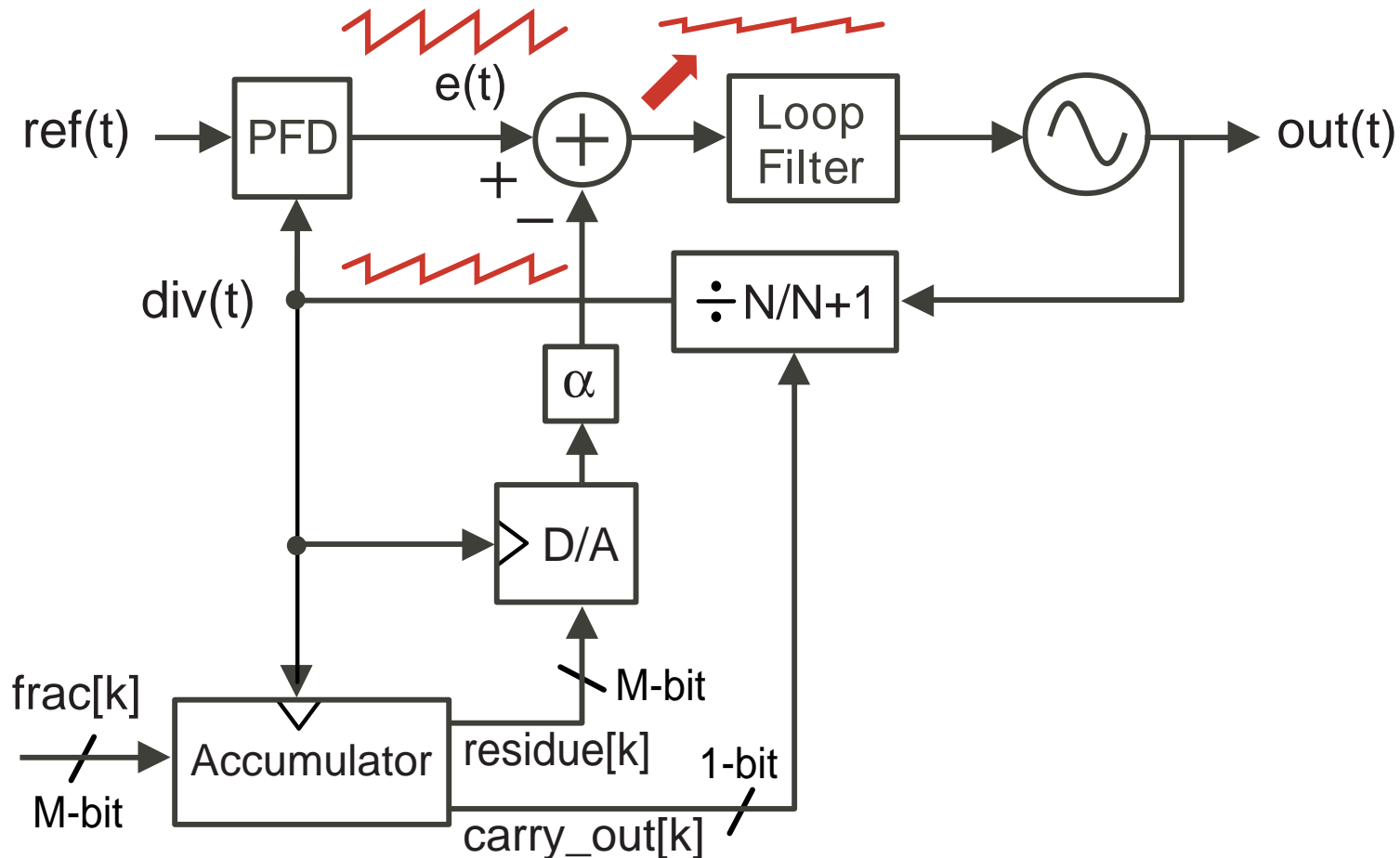

- **Gain matching between PFD error and scaled D/A output must be extremely precise**
 - Any mismatch will lead to spurious tones at PLL output


Is There a Better Way?

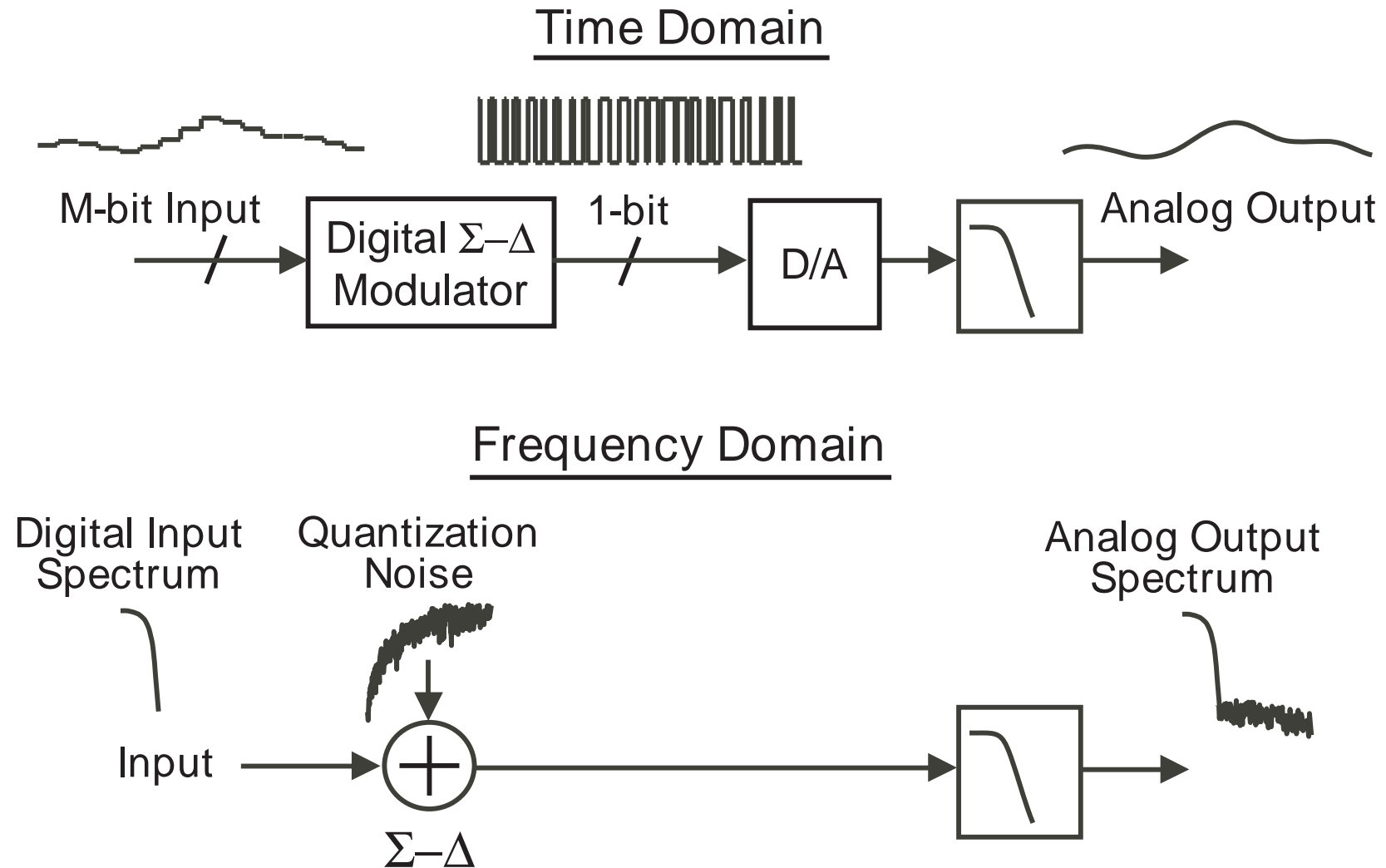A Better Dithering Method: Sigma-Delta Modulation




- **Sigma-Delta dithers in a manner such that resulting quantization noise is “shaped” to high frequencies**

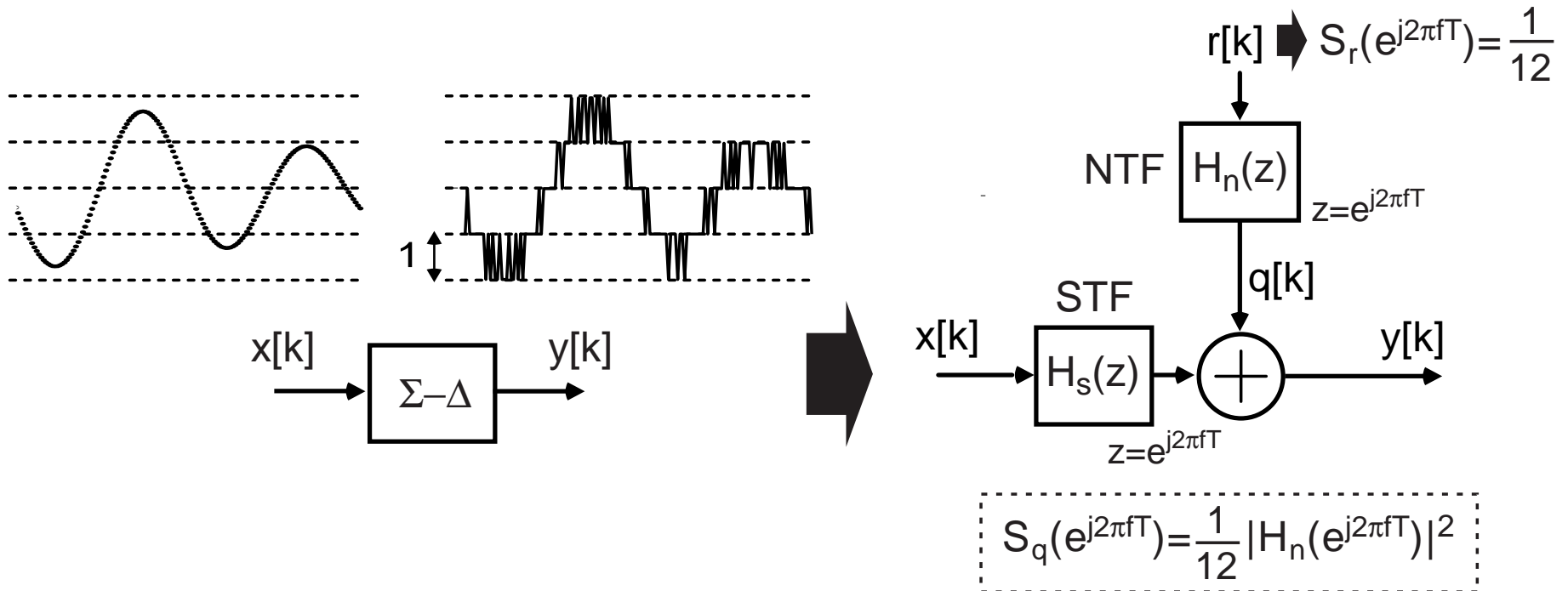Linearized Model of Sigma-Delta Modulator




- **Composed of two transfer functions relating input and noise to output**
 - **Signal transfer function (STF)**
 - Filters input (generally undesirable)
 - **Noise transfer function (NTF)**
 - Filters (i.e., shapes) noise that is assumed to be white

Example: Cutler Sigma-Delta Topology

 

- **Output is quantized in a multi-level fashion**
- **Error signal, $e[k]$, represents the quantization error**
- **Filtered version of quantization error is fed back to input**
 - **$H(z)$ is typically a highpass filter whose first tap value is 1**
 - i.e., $H(z) = 1 + a_1 z^{-1} + a_2 z^{-2} \dots$
 - **$H(z) - 1$ therefore has a first tap value of 0**
 - Feedback needs to have delay to be realizable

Linearized Model of Cutler Topology

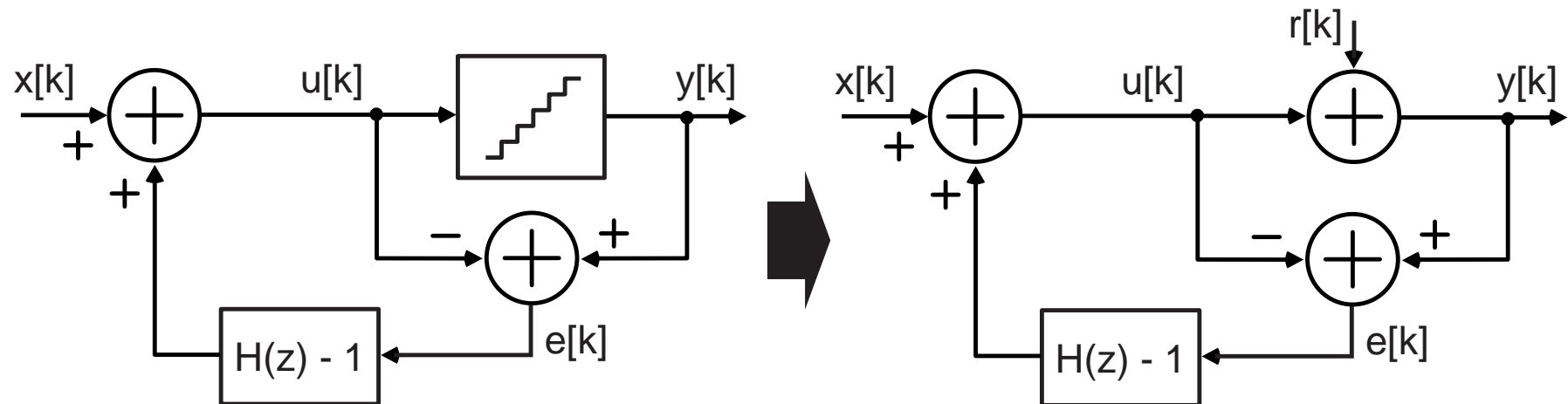


- Represent quantizer block as a summing junction in which $r[k]$ represents quantization error

- Note:

$$e[k] = y[k] - u[k] = (u[k] + r[k]) - u[k] = r[k]$$

- It is assumed that $r[k]$ has statistics similar to white noise
 - This is a key assumption for modeling – often not true!

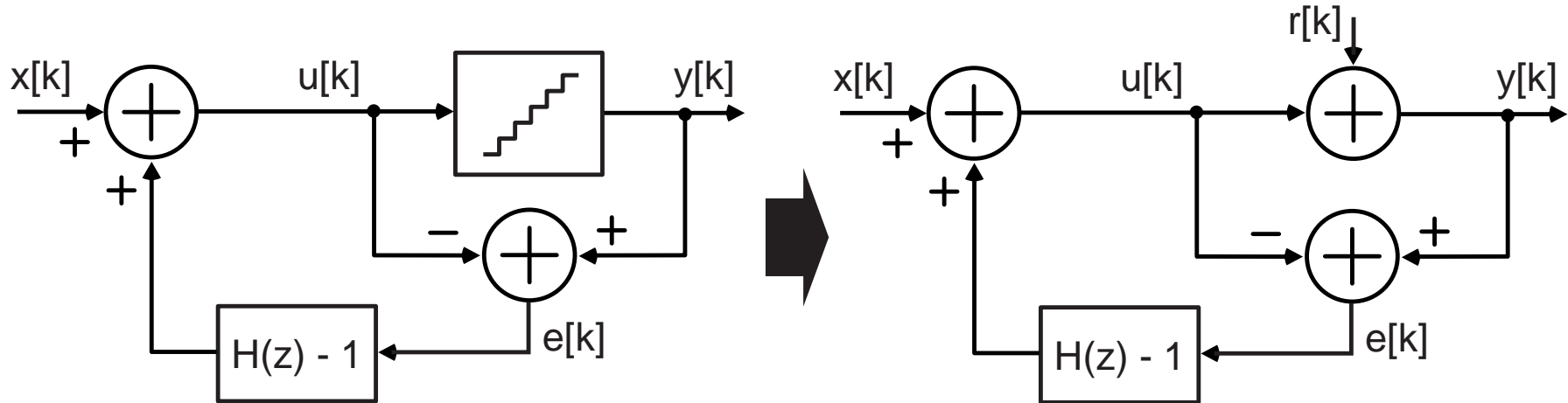Calculation of Signal and Noise Transfer Functions



- Calculate using Z-transform of signals in linearized model

$$Y(z) = U(z) + R(z)$$

$$= X(z) + (H(z) - 1)E(z) + R(z)$$


$$= X(z) + (H(z) - 1)R(z) + R(z)$$

$$= X(z) + H(z)R(z)$$

- NTF: $H_n(z) = H(z)$
- STF: $H_s(z) = 1$

A Common Choice for $H(z)$


$$H(z) = (1 - z^{-1})^m$$
$$\Rightarrow |H(e^{j2\pi fT})| = |(1 - e^{-j2\pi fT})^m|$$

 

Example: First Order Sigma-Delta Modulator



- Choose NTF to be

$$H_n(z) = H(z) = 1 - z^{-1}$$

 

- Plot of output in time and frequency domains with input of

  
$$x[k] = 0.5 + 0.25 \sin\left(\frac{2\pi}{100}k\right)$$



Example: Second Order Sigma-Delta Modulator



- Choose NTF to be

$$H_n(z) = H(z) = (1 - z^{-1})^2$$

 

- Plot of output in time and frequency domains with input of

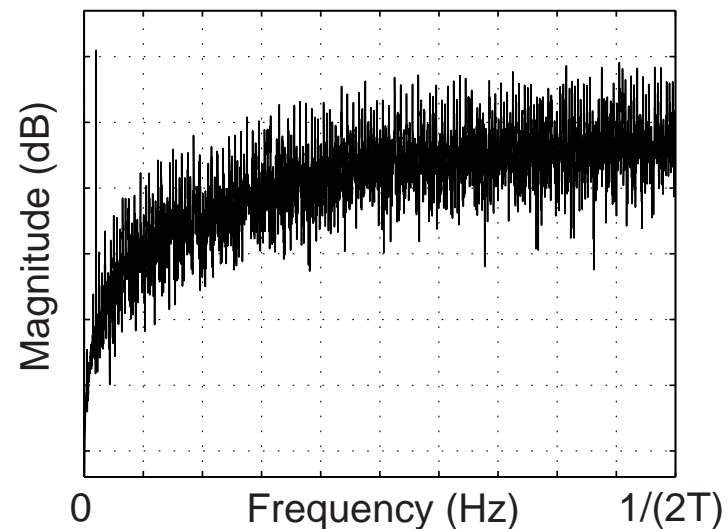 
$$x[k] = 0.5 + 0.25 \sin\left(\frac{2\pi}{100}k\right)$$



Example: Third Order Sigma-Delta Modulator



- Choose NTF to be

$$H_n(z) = H(z) = (1 - z^{-1})^3$$

 

- Plot of output in time and frequency domains with input of
  
$$x[k] = 0.5 + 0.25 \sin\left(\frac{2\pi}{100}k\right)$$




Observations


- **Low order Sigma-Delta modulators do not appear to produce “shaped” noise very well**
 - Reason: low order feedback does not properly “scramble” relationship between input and quantization noise
 - Quantization noise, $r[k]$, fails to be white
- **Higher order Sigma-Delta modulators provide much better noise shaping with fewer spurs**
 - Reason: higher order feedback filter provides a much more complex interaction between input and quantization noise

Warning: Higher Order Modulators May Still Have Tones

 - Quantization noise, $r[k]$, is best whitened when a “sufficiently exciting” input is applied to the modulator
 - Varying input and high order helps to “scramble” interaction between input and quantization noise
- Worst input for tone generation are DC signals that are rational with a low valued denominator
 - Examples (third order modulator):




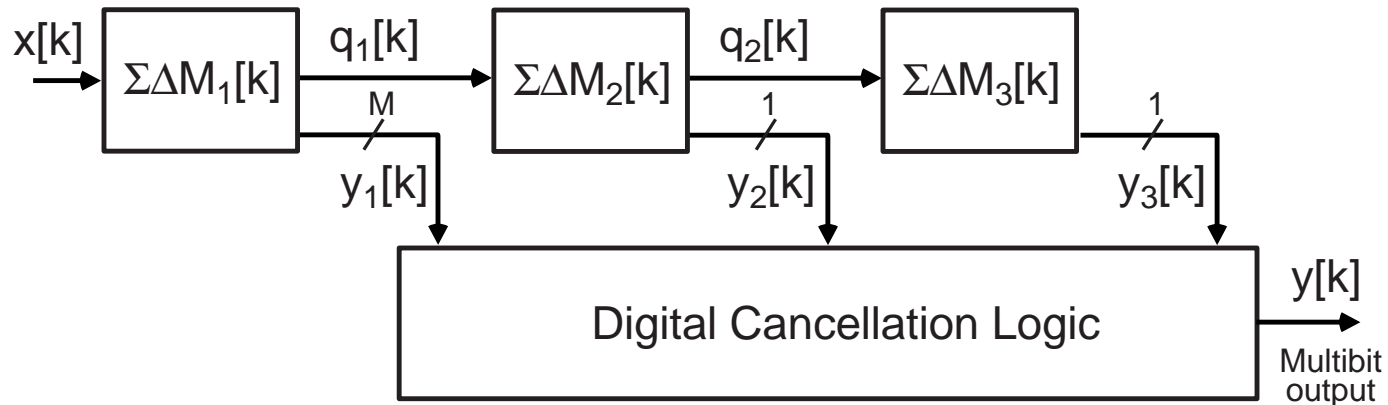Cascaded Sigma-Delta Modulator Topologies




- Achieve higher order shaping by cascading low order sections and properly combining their outputs
- Advantage over single loop approach
 - Allows pipelining to be applied to implementation
 - High speed or low power applications benefit
- Disadvantages
 - Relies on precise matching requirements when combining outputs (not a problem for digital implementations)
 - Requires multi-bit quantizer (single loop does not)

MASH topology

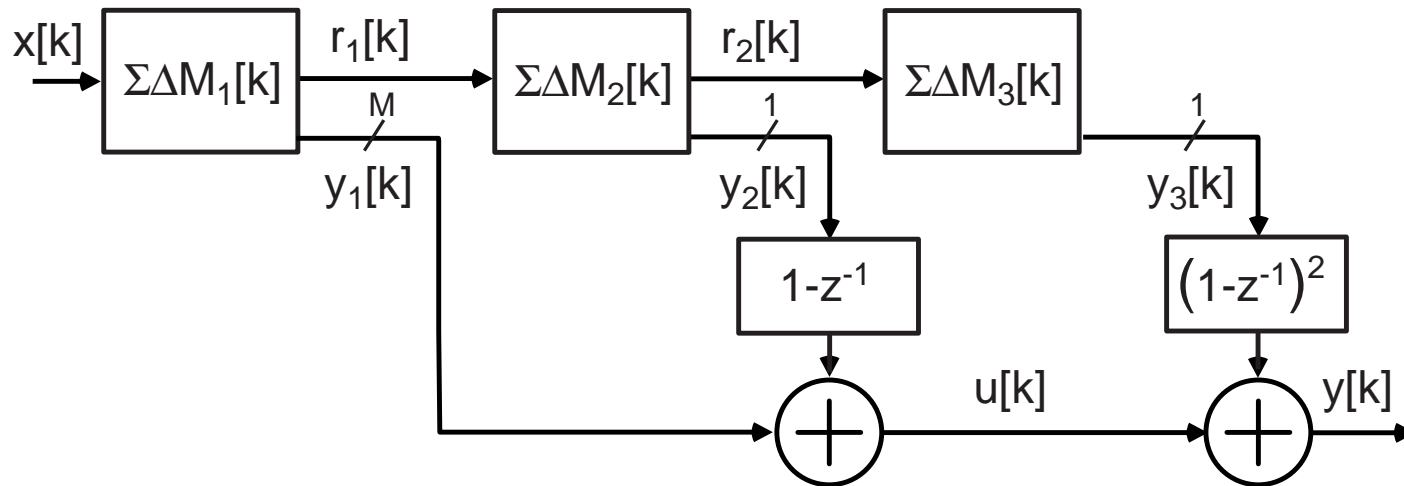

- Cascade first order sections
- Combine their outputs after they have passed through digital differentiators

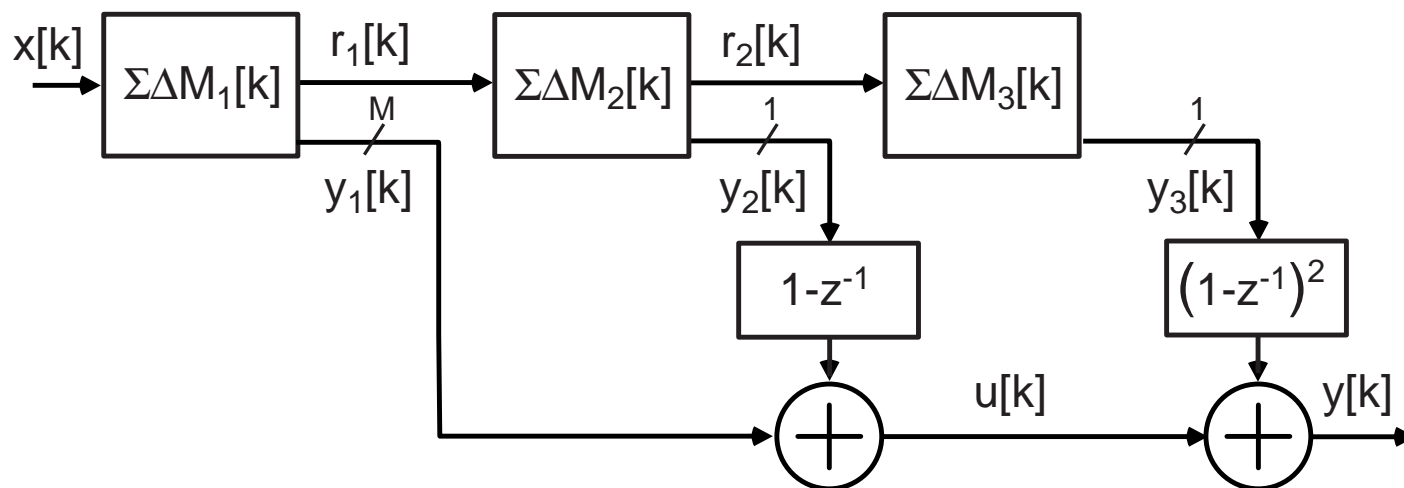Calculation of STF and NTF for MASH topology (Step 1)



Individual output signals of each first order modulator

$$y_1(z) = x(z) - (1 - z^{-1})r_1(z)$$


$$y_2(z) = r_1(z) - (1 - z^{-1})r_2(z)$$

$$y_3(z) = r_2(z) - (1 - z^{-1})r_3(z)$$

Addition of filtered outputs

$$\begin{aligned} & y_1(z) \\ + & (1 - z^{-1})y_2(z) \\ + & (1 - z^{-1})^2 y_2(z) \\ \hline = & x(z) - (1 - z^{-1})^3 r_3(z) \end{aligned}$$

 Calculation of STF and NTF for MASH topology (Step 1)




Overall modulator behavior

$$y(z) = x(z) - (1 - z^{-1})^3 r_3(z)$$


- STF: $H_s(z) = 1$
- NTF: $H_n(z) = (1 - z^{-1})^3$

Sigma-Delta Frequency Synthesizers

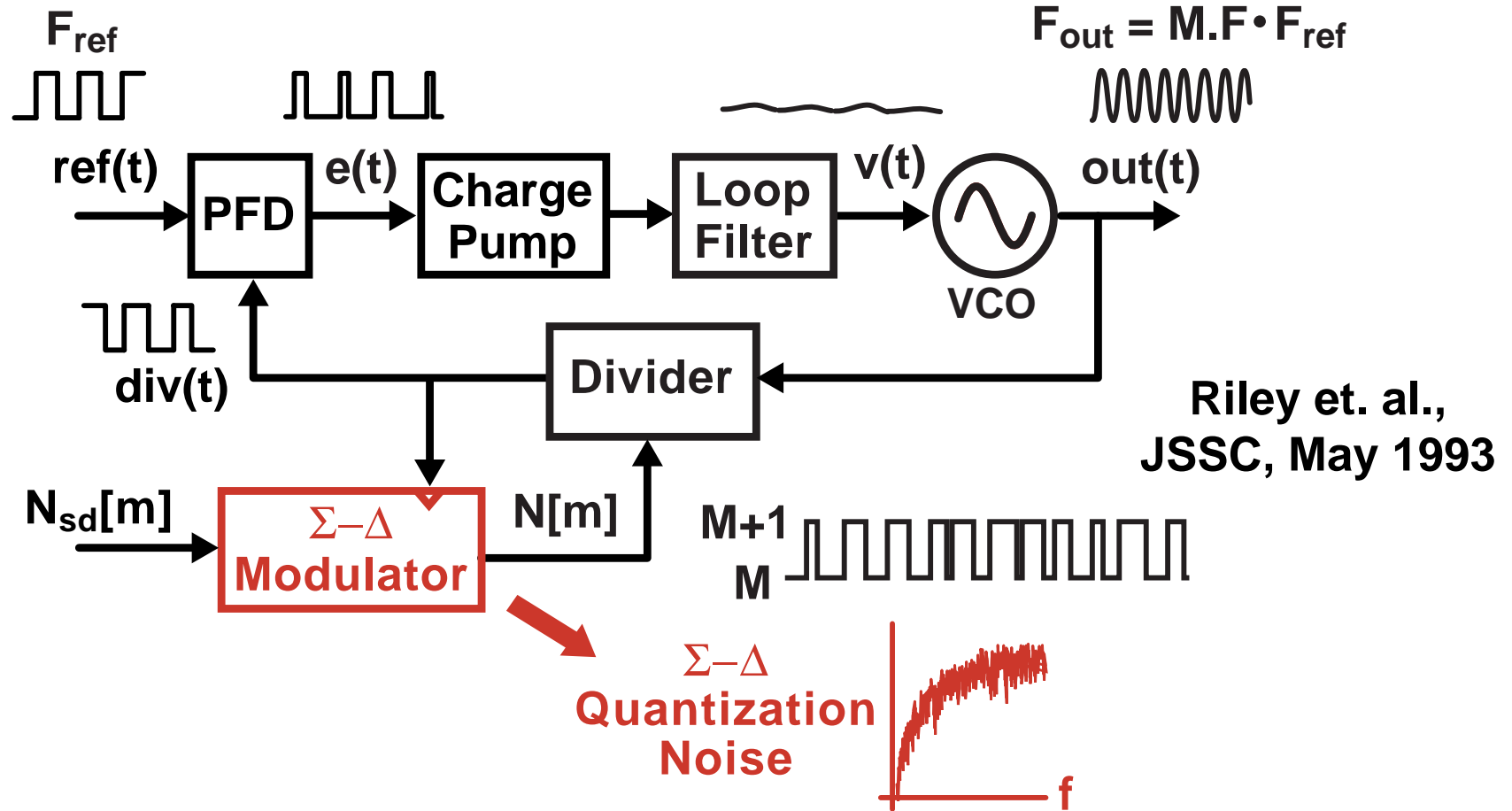

- Use Sigma-Delta modulator rather than accumulator to perform dithering operation
 - Achieves much better spurious performance than classical fractional-N approach

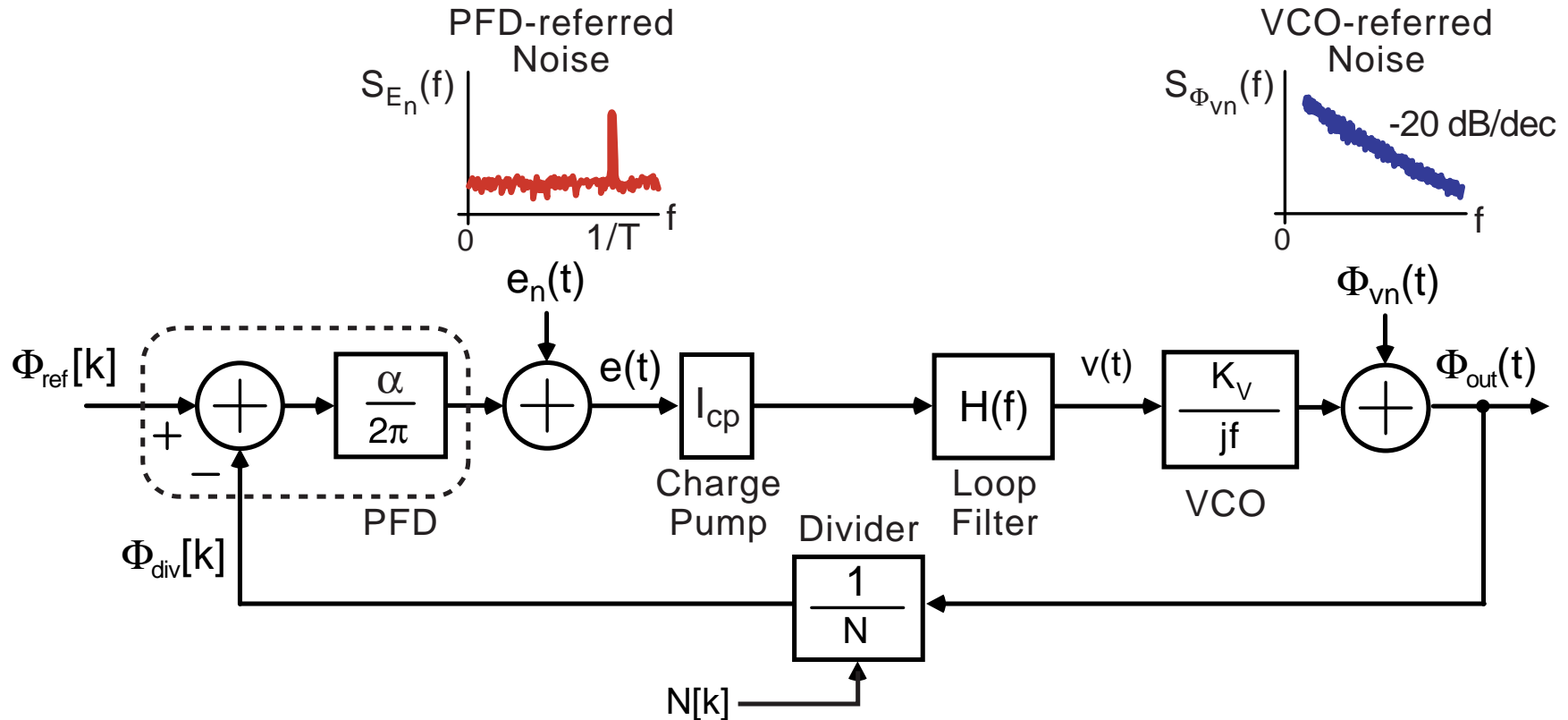
Background: The Need for A Better PLL Model



■ Classical PLL model


- Predicts impact of PFD and VCO referred noise sources
- Does not allow straightforward modeling of impact due to divide value variations
 - This is a problem when using fractional-N approach

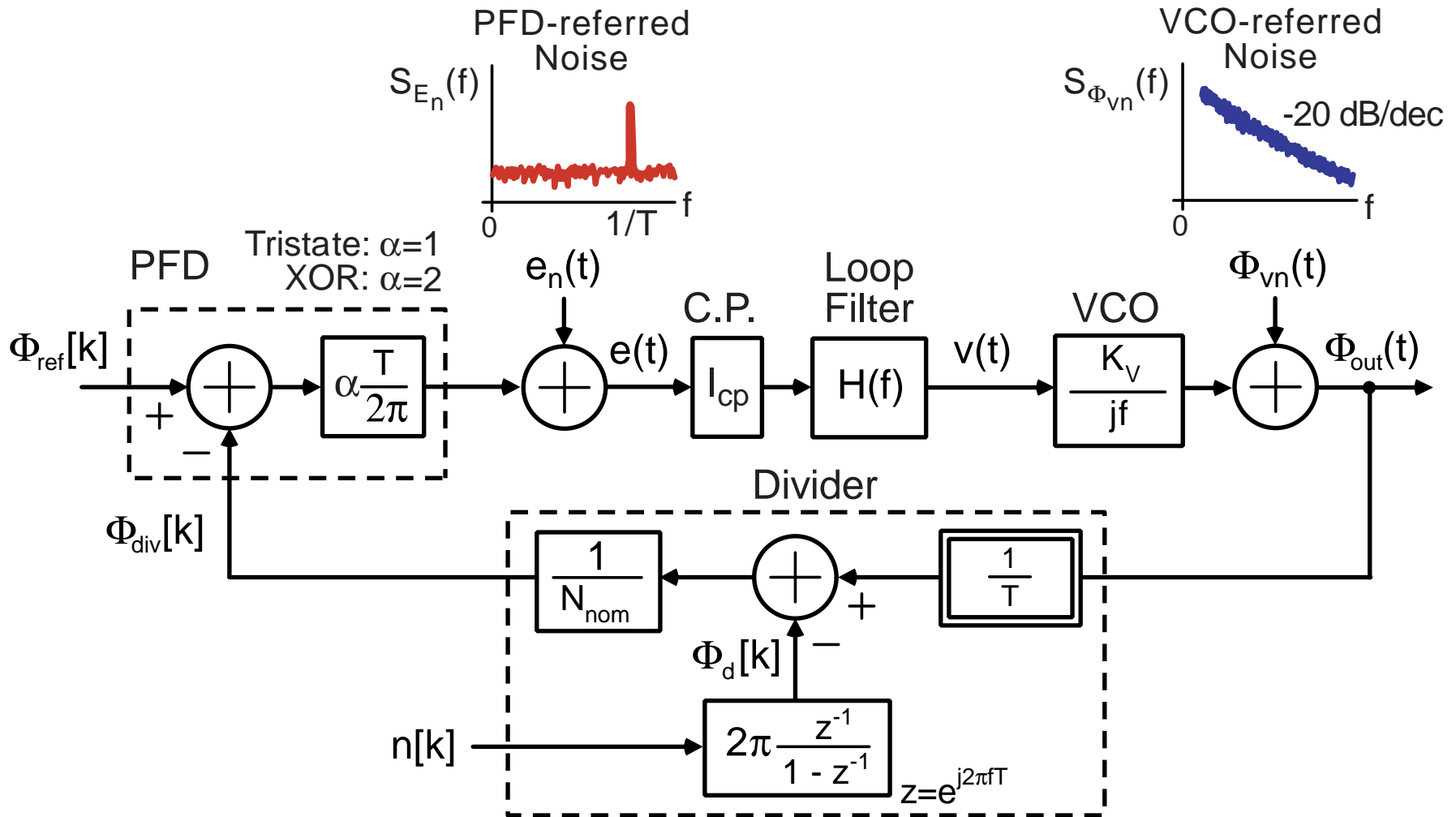A PLL Model Accommodating Divide Value Variations



- See derivation in Perrott et. al., "A Modeling Approach for Sigma-Delta Fractional-N Frequency Synthesizers ...", JSSC, Aug 2002

Parameterized Version of New Model


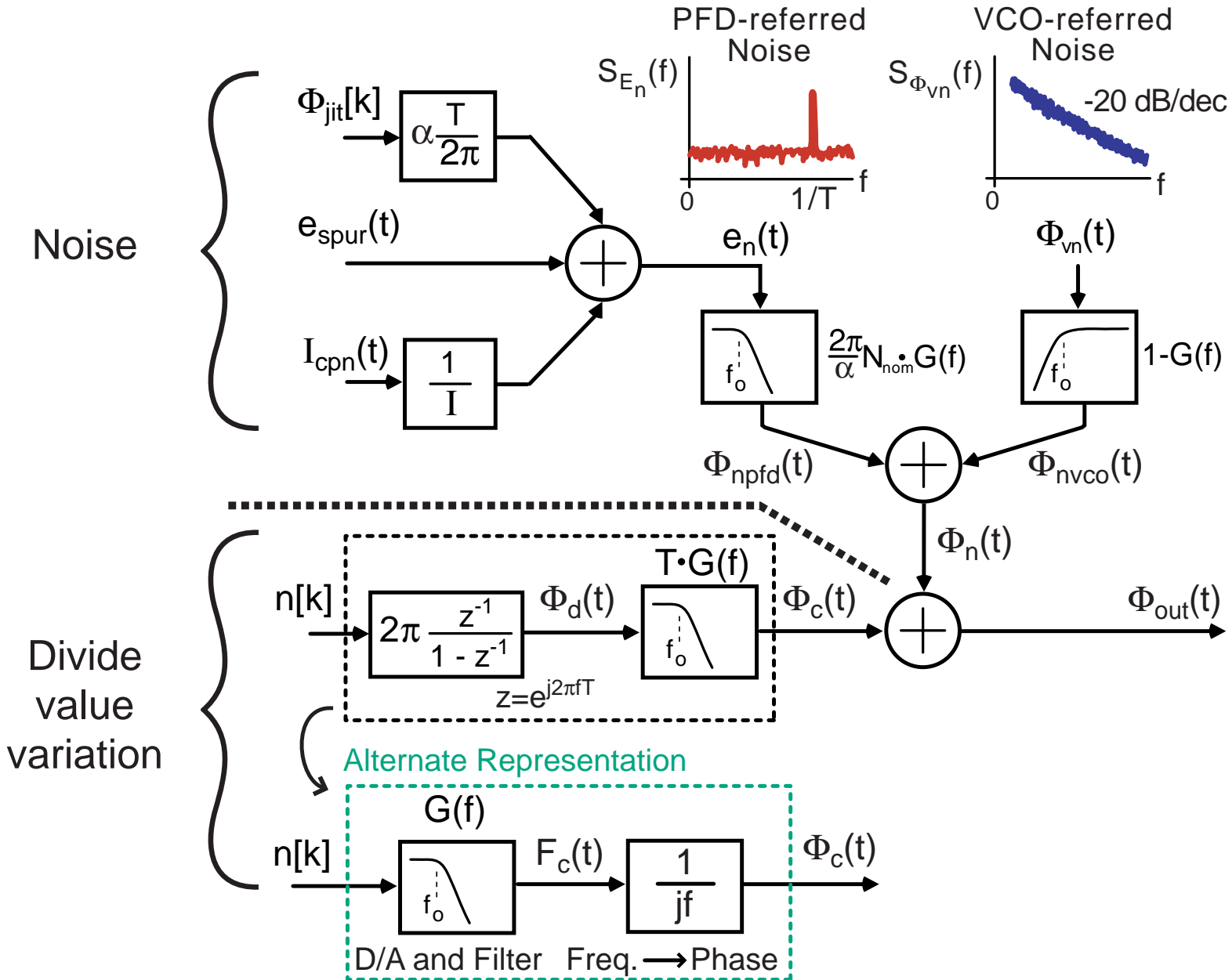


Spectral Density Calculations



- **Case (a):** $S_y(f) = |H(f)|^2 S_x(f)$
- **Case (b):** $S_y(e^{j2\pi fT}) = |H(e^{j2\pi fT})|^2 S_x(e^{j2\pi fT})$
- **Case (c):** $S_y(f) = \frac{1}{T} |H(f)|^2 S_x(e^{j2\pi fT})$

 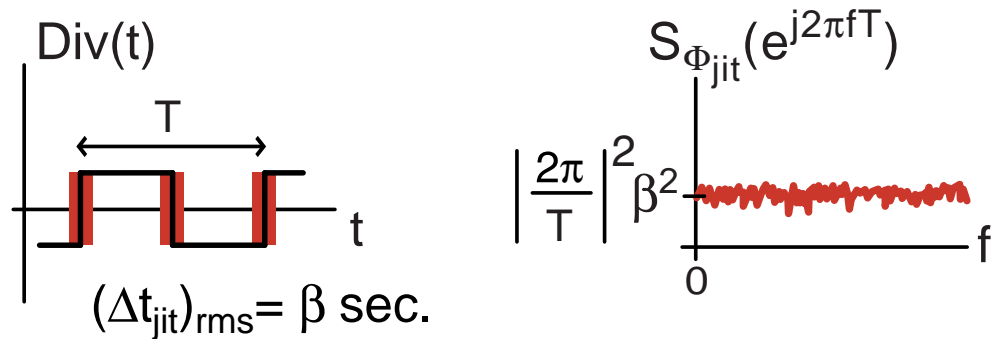
Example: Calculate Impact of Ref/Divider Jitter (Step 1)



- **Assume jitter is white**
 - i.e., each jitter value independent of values at other time instants
- **Calculate spectra for discrete-time input and output**
 - Apply case (b) calculation

$$S_{\Delta t_{jit}}(e^{j2\pi fT}) = \beta^2 \Rightarrow S_{\Phi_{jit}}(e^{j2\pi fT}) = \left|\frac{2\pi}{T}\right|^2 \beta^2$$

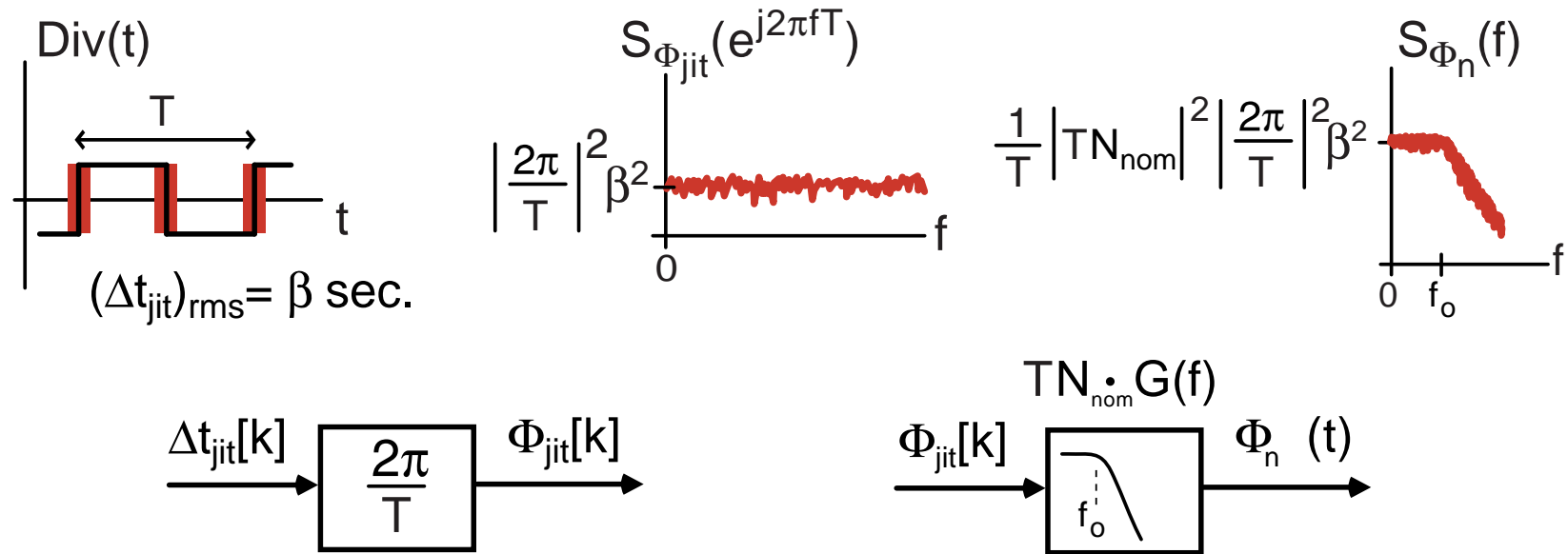Example: Calculate Impact of Ref/Divider Jitter (Step 2)




- **Compute impact on output phase noise of synthesizer**
 - We now apply case (c) calculation

$$\begin{aligned}
 S_{\Phi_n}(f) &= \frac{1}{T} |TN_{nom} G(f)|^2 S_{\Phi_{jit}}(e^{j2\pi fT}) \\
 &= \frac{1}{T} |TN_{nom} G(f)|^2 \left|\frac{2\pi}{T}\right|^2 \beta^2
 \end{aligned}$$


- Note that $G(f) = 1$ at DC

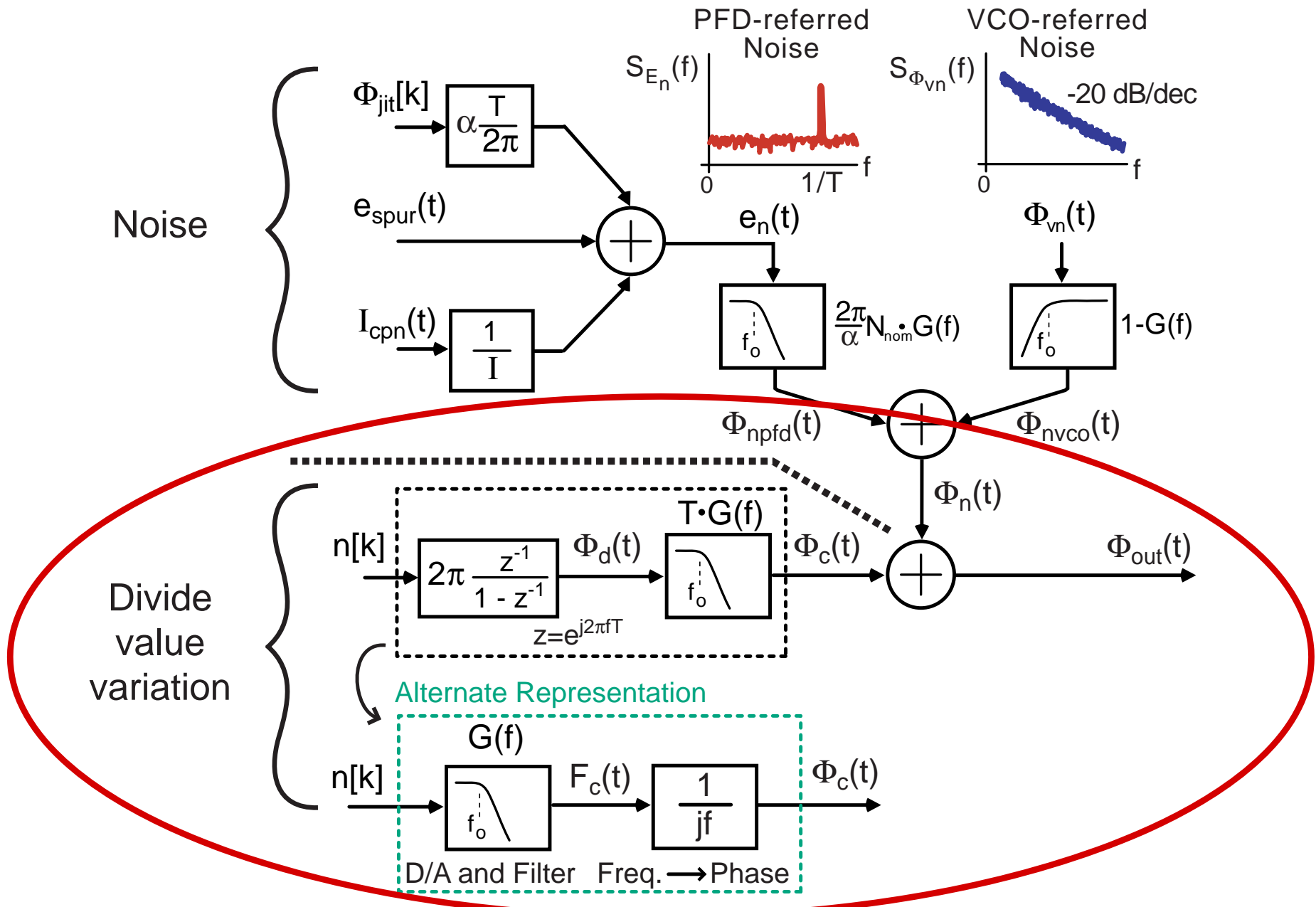Now Consider Impact of Divide Value Variations




Divider Impact For Classical Vs Fractional-N Approaches

Classical Synthesizer



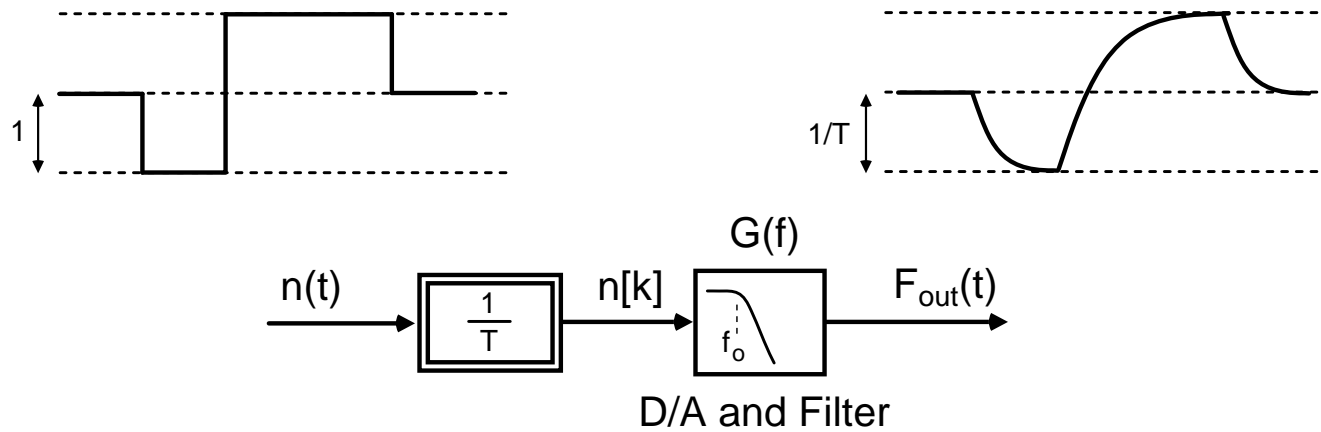


Fractional-N Synthesizer

 


■ Note: $1/T$ block represents sampler (to go from CT to DT)

   Focus on Sigma-Delta Frequency Synthesizer




- **Divide value can take on fractional values**
 - Virtually arbitrary resolution is possible
- **PLL dynamics act like lowpass filter to remove much of the quantization noise**

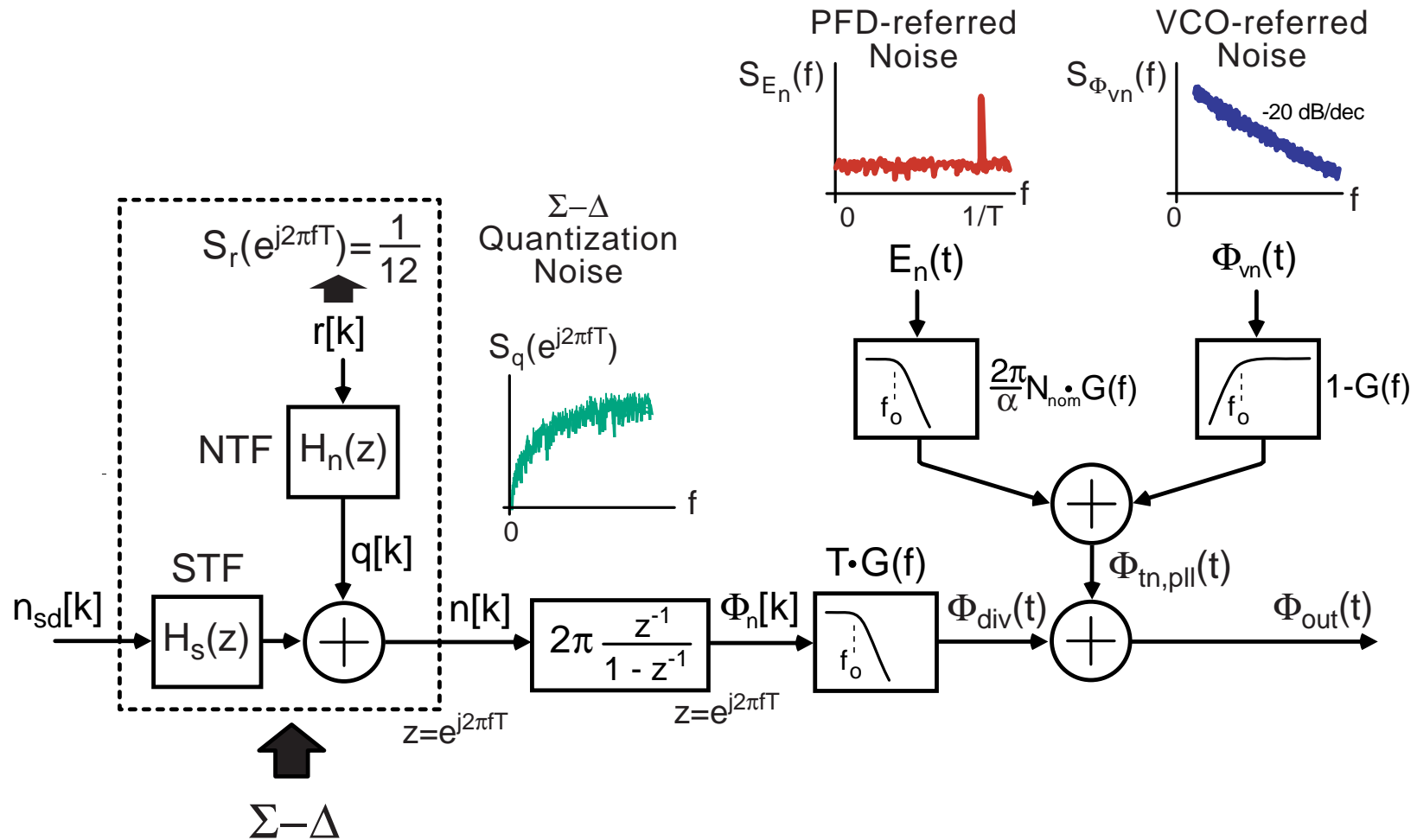Quantifying the Quantization Noise Impact




- Calculate by simply attaching Sigma-Delta model
 - We see that quantization noise is integrated and then lowpass filtered before impacting PLL output

A Well Designed Sigma-Delta Synthesizer

 


- Order of $G(f)$ is set to equal to the Sigma-Delta order
 - Sigma-Delta noise falls at -20 dB/dec above $G(f)$ bandwidth
- Bandwidth of $G(f)$ is set low enough such that synthesizer noise is dominated by intrinsic PFD and VCO noise

Impact of Increased PLL Bandwidth

 

- Allows more PFD noise to pass through
- Allows more Sigma-Delta noise to pass through
- Increases suppression of VCO noise

Impact of Increased Sigma-Delta Order

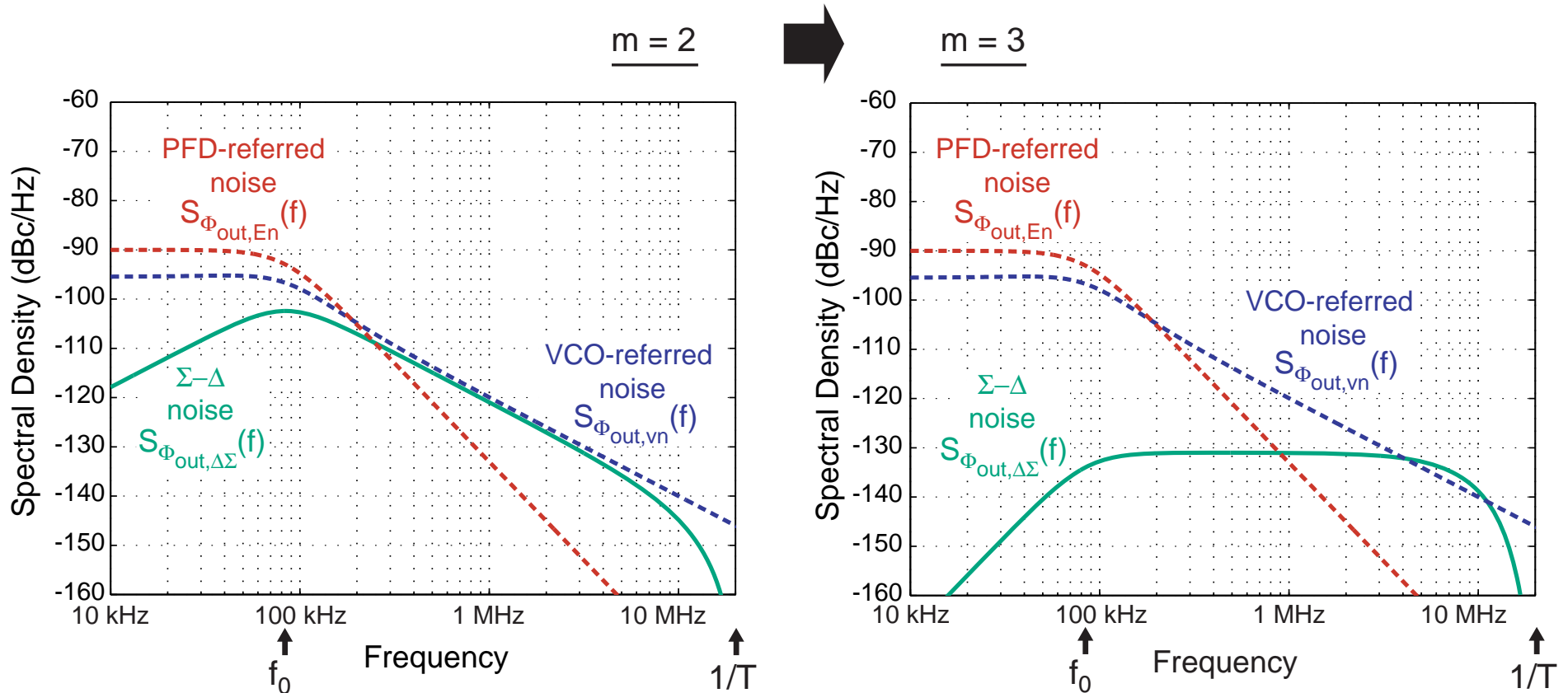

- PFD and VCO noise unaffected
- Sigma-Delta noise no longer attenuated by $G(f)$ such that a -20 dB/dec slope is achieved above its bandwidth